

EE204 : Analog Circuits
Dept of Electrical Engineering
IIT Bombay
Autumn Semester 2023

Assignment 2

Total Marks: 10

Submission Deadline: 11:59 p.m., 26-08-2023

Mode of Submission: Scan your assignment and upload on Moodle as a single pdf file.

1. For the circuit shown in Figure 1, $V_{dd} = 1.8\text{ V}$, $\mu_n C_{ox} = 260\mu\text{A/V}^2$, $V_t = 0.4\text{ V}$, $\frac{3\mu\text{m}}{0.5\mu\text{m}} < \left(\frac{W}{L}\right)_1 < \frac{5\mu\text{m}}{0.5\mu\text{m}}$ (Choose any aspect ratio in this range).

- (a) Find V_{GS} of transistor M1 for the Figure 1(a). (1.5 Marks)
- (b) The circuit in Figure 1(b) is 1:1 current mirror, Plot I_{out} v/s V_{DS} for two lengths of M2, $(L_2)_1 = 0.5\mu\text{m}$ and $(L_2)_2 = 1\mu\text{m}$ (keeping aspect ratio same as Q1(a)) and write the approximate value of slope in saturation and ohmic region, given that $\lambda = 0.025\text{ V}^{-1}$ for $L_2 = 1\mu\text{m}$ and $\frac{d\lambda}{dL} = -0.05\text{ V}^{-1}/\mu\text{m}$ for $L \leq 1\mu\text{m}$. (1.5 Marks)
- (c) The circuit in Figure 1(c) is 1:1 current mirror, Find the region of operation of M2 and I_{out} for $R = 20\text{ k}\Omega$ and $R = 40\text{ k}\Omega$. (2 Marks)

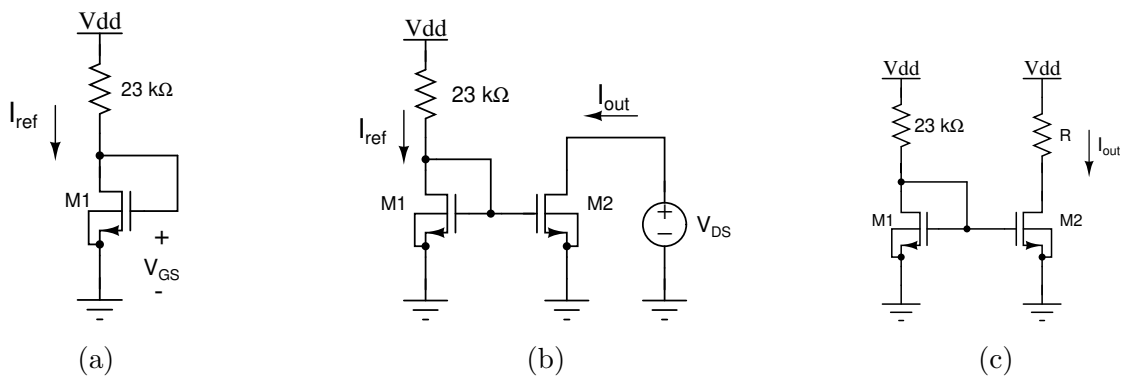


Figure 1: Circuits for Q1

2. Refer to Figure 2 and answer the following questions:

- (a) What should be the value of R_2 such that I_{load} is independent of R_1 . Given that $R_1 = 1\text{ k}\Omega$, $R_3 = 1\text{ k}\Omega$, $R_4 = 9\text{ k}\Omega$, $A = 100$? (1.5 Marks)
- (b) Derive the expression for the I_{load} , if R_3 reduces by $a\%$ ($0 < a \leq 5$) and R_2 increases by $b\%$ ($0 < a \leq 4$). Then specify the condition for worst-case error in the load current. (2.5 Marks)
- (c) Use the worst-case values you obtained in Q2(b) and calculate the numerical value of the error in the worst-case condition (Choose a reasonable value of V_{ctrl}). (1 Mark)

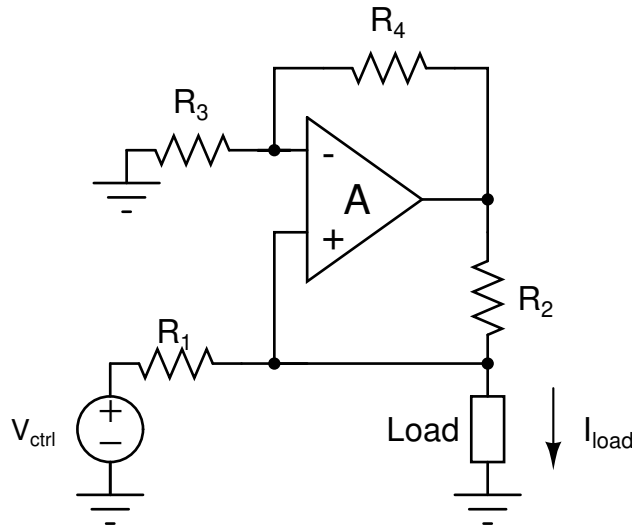


Figure 2: Circuit for Q2