


Tutorial 8 solutions

EE204: Analog Circuits

Dept of Electrical Engineering, IITB
Autumn Semester 2023

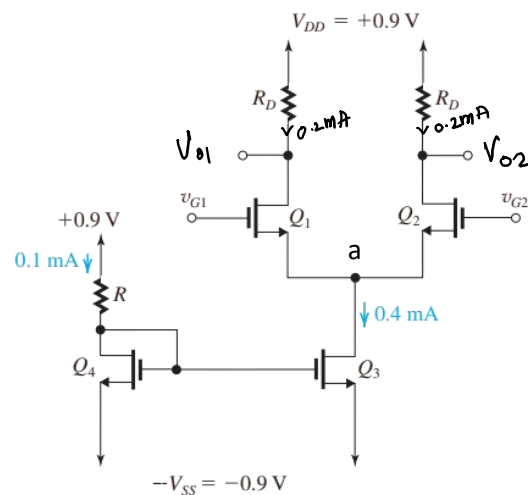Q1.

Design the diff pair circuit in Fig. 1 to obtain a dc voltage of +0.1 V at each of the drains of Q1 and Q2 when $v_{G1} = v_{G2} = 0$ V. Operate all transistors at $V_{OV} = 0.15$ V and assume that for the process technology in which the circuit is fabricated, $V_{Th} = 0.4$ V and $\mu_n C_{ox} = 400 \mu\text{A}/\text{V}^2$. Neglect channel-length modulation. Determine the values of R , R_D , and the W/L ratios of Q1, Q2, Q3, and Q4. What is the input common-mode voltage range for the design?



Given $v_{O1} = 0.1$ V then,

$$R_D = (V_{DD} - v_{O1}) / I_{DQ1} = 4 \text{ K ohm}.$$

$I_{DQ1} = I_{DQ2} = 0.2$ mA. The transistors should be in the saturation region for the diff pair operation, given all transistors are operated at $V_{OV} = 0.15$ V so, by using saturation current equation of the transistors,

$$\frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_{1,2} V_{ov}^2 = 0.2 \text{ mA}$$

$$\left(\frac{W}{L} \right)_{1,2} = \frac{400}{9}$$

$$\frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_3 V_{ov}^2 = 0.4 \text{ mA}$$

$$\left(\frac{W}{L} \right)_3 = \frac{800}{9}$$

$$\frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_4 V_{ov}^2 = 0.1 \text{ mA}$$

$$\left(\frac{W}{L} \right)_4 = \frac{200}{9}$$

$$V_{ovQ4}=0.15$$

$$V_{GSQ4}=0.15+V_{th}=0.55$$

$$V_{GQ4}= -V_{ss}+0.55=-0.35$$

$$R=(V_{dd}-V_{GQ4})/0.1mA = \mathbf{12.5K\ ohm}$$

As V_{cm} goes up the voltage at node a goes up to maintain the same current through Q1 and Q2 decreasing V_{DS} across them

For Q1,Q2 to be in saturation

$$V_{DS1,2} \geq V_{GS1,2} - V_{TH}$$

$$V_{D1,2} \geq V_{G1,2} - 0.4$$

$$0.1 \geq V_{G1,2} - 0.4$$

$$V_{G1,2} \leq 0.5V$$

$$V_{G1,2} = V_{CM} \leq 0.5V$$

As V_{cm} goes down the voltage at node a goes down to maintain the same current through Q1 and Q2 decreasing V_{DS} across Q4

$$V_{DS3} \geq V_{GS3} - V_{TH}$$

$$V_{DS3} = V_{G1,2} - V_{GS1,2} - V_{SS} \geq 0.15$$


$$V_{G1,2} \geq 0.15 + 0.55 - 0.9$$

$$V_{G1,2} = V_{CM} \geq -0.2$$

$$-0.2V \leq V_{CM} \leq 0.5V$$

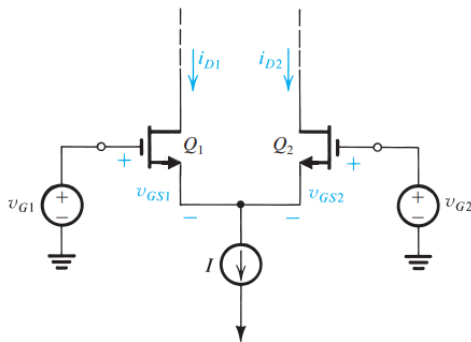Q2.

Design the MOS differential amplifier shown in the figure below to operate at $V_{ov}=0.25V$ and to provide a transconductance g_m of 1 mA/V. Specify the W/L ratios and the bias current. The technology available provides $V_{th}=0.5V$ and $\mu_n C_{ox}=400\ \mu A/V^2$.



Given $g_m=1mA/V$ then the bias current I_D is related to g_m as, $g_m=2I_D/V_{ov}$

$$1mA/V=2I_D/0.25$$

$$I_D=0.125mA$$


Also from the mosfet current equation ,

$$\frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_{1,2} V_{ov}^2 = 0.125mA$$

$$\left(\frac{W}{L} \right)_{1,2} = \mathbf{10}$$

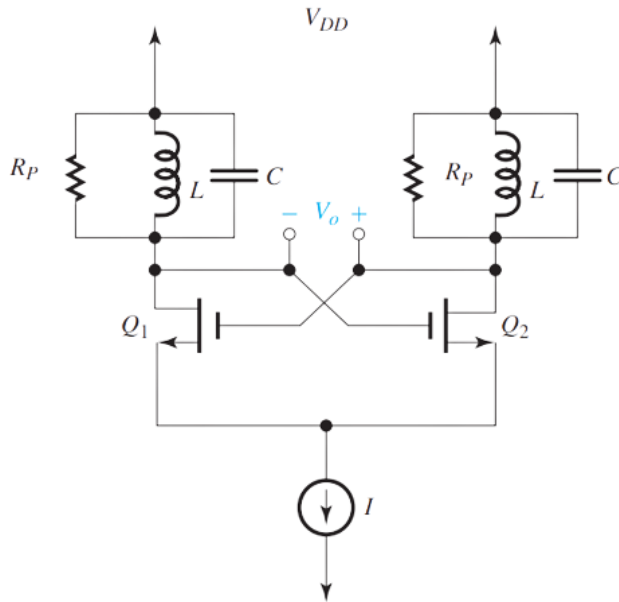Q3.

Design the cross-coupled oscillator to operate at $\omega_0 = 10 \text{ G rad/s}$. The IC inductors available have $L = 10 \text{ nH}$ and $Q = 10$. If the transistor $r_o = 10 \text{ k}$, find the required value of C and the minimum required value of g_m at which Q_1 and Q_2 are to be operated.



$$\text{frequency of oscillation of LC tank circuit} = \omega_0 = \frac{1}{\sqrt{LC}}$$

$$C = \omega_0^2 * L$$

$$C = 1 \text{ pF}$$

R_p can be evaluated from the Q factor of inductance

$$Q = R_p / (\omega_0 L)$$

$$R_p = 10 * 10 \text{ n} * 10 \text{ G} = 1000 = 1 \text{ K}$$


at ω_0 , the gains $A_1 = A_2 = -g_m (R_p || r_o)$

from barkhausen's criterion for sustained oscillations, $|A_1 * A_2| = 1$

$$\begin{aligned} A_1^2 &= 1 \\ -g_m (R_p || r_o) &= -1 \\ g_m (R_p || r_o) &= 1 \\ g_m &= 1.1 \text{ mA/V} \end{aligned}$$

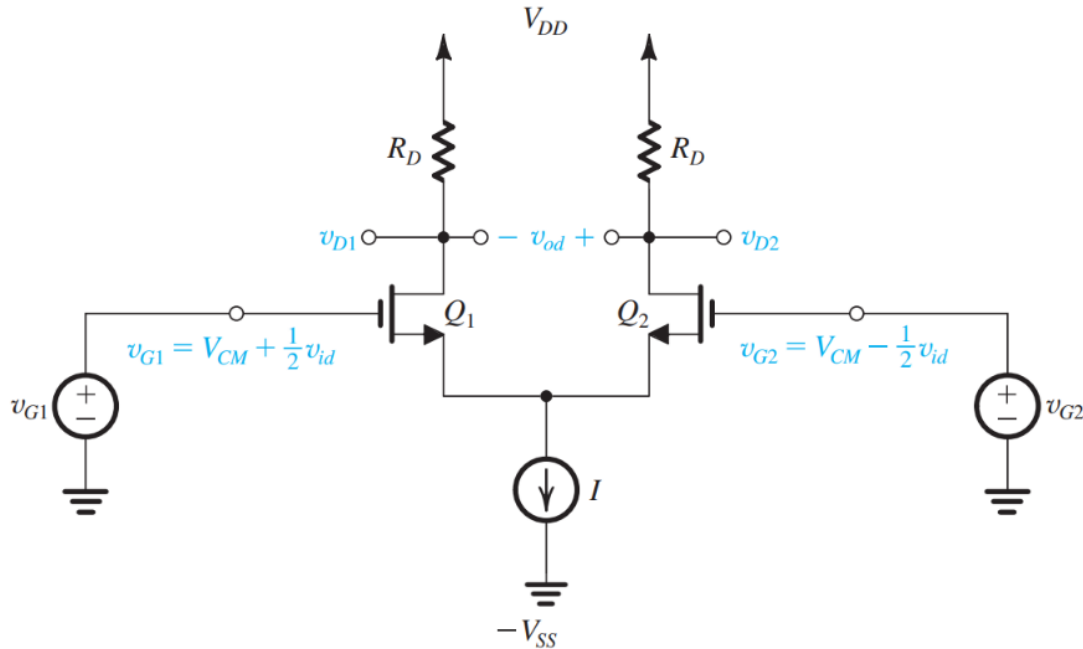Q4.

Design a MOS differential amplifier to operate from a 2V supply and dissipate no more than 1 mW in its equilibrium state. Select the value of V_{ov} so that the value of V_{id} that steers the current from one side of the pair to the other is 0.25 V. The differential voltage gain A_d is to be 10 V/V. Assume $k_n = 400 \mu\text{A/V}^2$ and neglect the Early effect. Specify the required values of I , R_D , and W/L .



The power consumed by the circuit = $2 \cdot I \cdot V_{DD} < 1\text{mW} \Rightarrow I < 0.5\text{mA}$

Given value of V_{id} that steers the current from one side to other is 0.25V this means for V_{id} of 0.25 v one branch carries 0 current while other carries all the current of the current source

Assume initial overdrive voltage = V_{ov1} , now a differential input of 0.25V is applied then, on positive side, $V_{ovQ1} = V_{ov1} + 0.125$
on the negative side $V_{ovQ2} = V_{ov1} - 0.125$

The negative branch has no current flowing through it so **$V_{ov1} = 0.125\text{V}$**

$I_D = I/2 < 0.25\text{mA}$

$$\frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_{1,2} V_{ov1}^2 < 0.25\text{mA}$$

$$\left(\frac{W}{L} \right)_{1,2} < 80$$

Also, given $A_d = 10\text{V/V} \Rightarrow g_m R_D = 10$

$g_m R_D = 2I_D R_D / V_{ov1} = I \cdot R_D / V_{ov1} = 10$

$I = 10 \cdot V_{ov1} / R_D < 0.5\text{mA}$

$10 \cdot 0.125 / 0.5 < R_D$

$R_D > 2.5\text{K ohm}$