

EE204 Autumn 2023

Tutorial I

Date 17 Aug 2023

Q1) The circuit in Fig. 1 utilizes an ideal op-amp.

- (a) Find I_1, I_2, I_3, I_L , and V_x .
- (b) If V_o is not to be lower than -13 V, find the maximum allowed value for RL .
- (c) If RL is varied in the range 100Ω to $1\text{ k}\Omega$, what is the corresponding change in I_L And in V_o ?

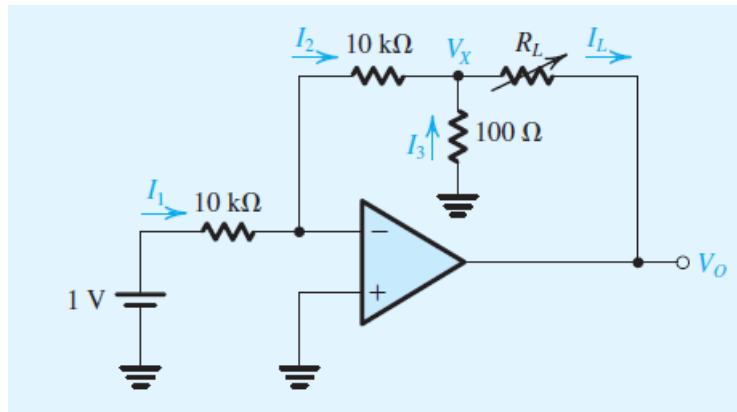


Figure 1

Q2) The circuit in Fig. 2 utilizes an ideal op-amp. Determine expression for v_o in terms of v_1, v_2, v_3 .

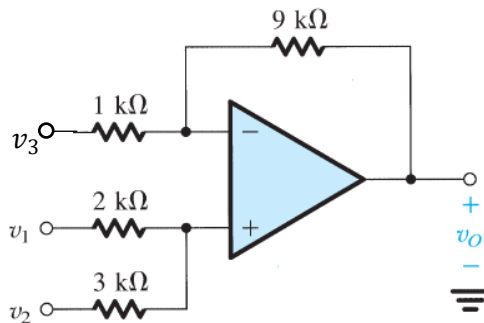



Figure 2

Q3) Consider a CMOS process for which $L_{min} = 0.25\text{ }\mu\text{m}$, $t_{ox} = 6\text{ nm}$, $\mu_n = 350\text{ cm}^2/\text{V.s}$, and $V_t = 0.5\text{ V}$.

- (a) Find C_{ox} .
- (b) For an NMOS transistor with $W/L = 20\text{ }\mu\text{m}/0.25\text{ }\mu\text{m}$, calculate the values of V_{OV} , V_{GS} , and V_{DSmin} needed to operate the transistor in the saturation region with a dc current $I_D = 0.5\text{ mA}$.
- (c) For an NMOS transistor with $L = 0.25\text{ }\mu\text{m}$, calculate the W/L ratio needed to operate the transistor in the saturation region with a dc current $I_D = 0.3\text{ mA}$ and $V_{GS} = 0.8\text{ V}$.

Solution

Q1) a)

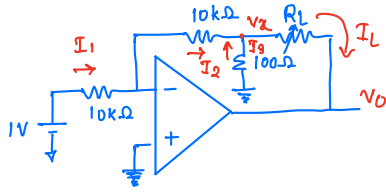

$$I_1 = \frac{1V}{10k\Omega} \quad (\text{Virtual ground})$$

$$= 0.1mA$$

$$I_1 = I_2 = 0.1mA$$

$$V_x = -I_2 \cdot 10k\Omega = -1V$$

$$I_3 = -\left(\frac{-1V}{100}\right) = 10mA$$

$$\therefore I_L = I_3 + I_2 = 10mA + 0.1mA = 10.1mA$$

b) $V_o > -13V$

$$V_o = V_x - I_L \cdot R_L$$

$$-13V = -1 - 10.1mA \times R_{L_{max}}$$


$$\therefore R_{L_{max}} = 1.19k\Omega$$

c) If R_L changes from 100Ω to $1k\Omega$, I_L will not change

$$V_o = -1 - 10.1mA \times 0.1k = -2.01V \quad \text{when } R = 100\Omega$$

$$V_o = -1 - 10.1mA \times 1k = -11.1V \quad \text{when } R = 1k\Omega$$

Q2)

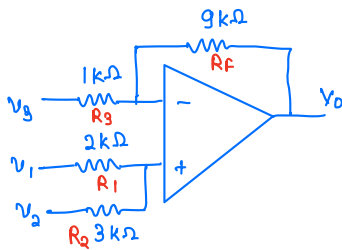

$$V_o = \left(1 + \frac{R_F}{R_3}\right) \left[\left(\frac{R_2}{R_1 + R_2}\right) V_1 + \left(\frac{R_1}{R_1 + R_2}\right) V_2 \right] - \frac{R_F}{R_1} V_3$$


$$= (1 + 9) \left[\frac{3}{5} V_1 + \frac{2}{5} V_2 \right] - 9 V_3$$

$$V_o = 6V_1 + 4V_2 - 9V_3$$

Q3) We have $C_{ox} = 8.6 \text{ fF}/(\mu\text{m})^2$ for $t_{ox} = 4 \text{ nm}$

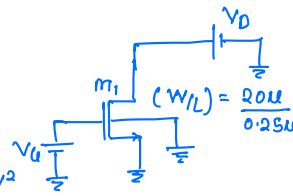a) Hence for $t_{ox} = 6 \text{ nm}$ $C_{ox} = 5.73 \text{ fF}/(\mu\text{m})^2$

$$\mu_n \cdot C_{ox} = 350 \text{ cm}^2/\text{V}\cdot\text{s} \times 5.73 \text{ fF}/(\mu\text{m})^2 = 200.5 \frac{\mu\text{A}}{\text{V}^2} \approx 200 \mu\text{A}/\text{V}^2$$



b) if M_1 is in saturation region then

$$I_D = \frac{\mu_n C_{ox}}{2} \times \left(\frac{W}{L}\right) [V_{GS} - V_T]^2$$

$$0.5 \text{ mA} = \frac{200 \mu}{2} \times \frac{20 \mu}{0.25 \mu} (V_{GS} - 0.5)^2$$

$$V_{GS} = 0.75 \text{ V}$$

$$V_{OV} = V_{GS} - V_T = V_{GS} - 0.5$$

$$= 0.75 - 0.5 = 0.25 \text{ V}$$

$$V_{DS_{min}} = V_{OV} = 0.25 \text{ V}$$

$$c) I_D = 0.3 \text{ mA} = \frac{200 \mu}{2} \times \left(\frac{W}{L}\right) [0.8 - 0.5]^2$$

$$0.3 \text{ m} = 100 \mu \left(\frac{W}{L}\right) (0.3)^2$$

$$\frac{W}{L} = 33.33$$