

Assignment 5

EE204 : Analog Circuits

Dept of Electrical Engineering, IITB
Autumn Semester 2023

TOTAL MARKS: 10

SUBMISSION DEADLINE: 11:59 P.M., 14-10-2023


MODE OF SUBMISSION: SCAN YOUR ASSIGNMENT AND UPLOAD ON MOODLE AS A SINGLE PDF FILE.

Q1. Design a Wein-Bridge Oscillator as shown with the following requirements:

- Frequency of Oscillation ω_0 should be **19/(1+x)** kHz, where x is the last digit of your roll number.
- Choose $R_s/R_p = 1+x$ and $C_p/C_s = 1+x$, where x is the last digit of your roll number.
- $R_s, R_p, R_1, R_2 > 1\text{ kohm}$, $C_p, C_s > 100\text{ pF}$.

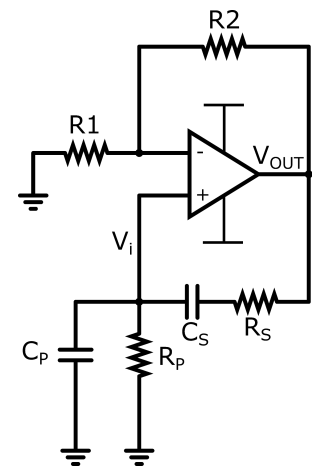A. Determine the following to design the oscillator, assuming the opamp is ideal

- A.1.** $\beta(s)$ - Transfer function of the feedback path as a function of R_s , R_p , C_p and C_s (2m)
- A.2.** Values of circuit elements - R_s , R_p , C_p and C_s (2m)
- A.3.** Using values from A.2, find $\beta(j\omega_0)$ - feedback Transfer Function at ω_0 (1m)
- A.4.** Using values from A.2, find the ratio R_2/R_1 for sustained oscillations (2m)



B. The following amplitude control is implemented with all other circuit elements being the same as before, except R_2 is now a potentiometer and two diodes are added across R_2 as shown :

- B.1.** Choose R_2/R_1 so that it is greater than the ratio obtained in A.4 . Determine the values of R_2 , R_1 . (1m)
- B.2.** Find the setting on the R_2 Potentiometer so that the output sine wave has an amplitude of 6V.
Given $V_{dd1} = -V_{ss1} = 15\text{V}$,
Diode current $I_D = I_s \cdot (\exp(V/V_T))$ where $V_T = 25\text{mV}$,
 $I_s = 100\text{nA}$, and V is the drop across the diode. (2m)

