
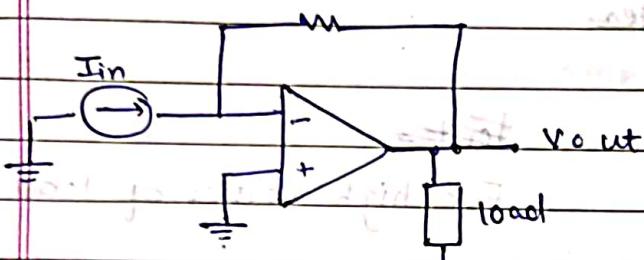



MORE OPAMP APPLICATION CIRCUITS

⇒ Current - To - Voltage - Converter

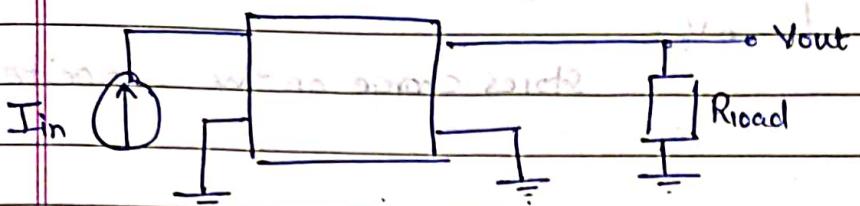

Problem: → Voltage across the current-source = 0
 $(R \rightarrow \infty)$
it may NOT work.


opamp can source/sink

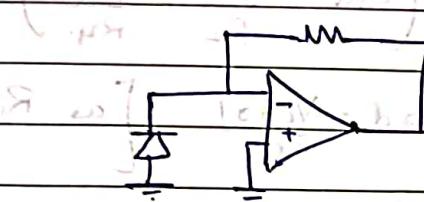

(Radiation detector)


The diode will be biased at 0
if the diode is photovoltaic diode (cell)
it will work

To solve this problem,

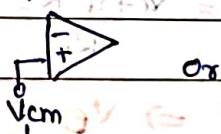

connect it to a -ve supply

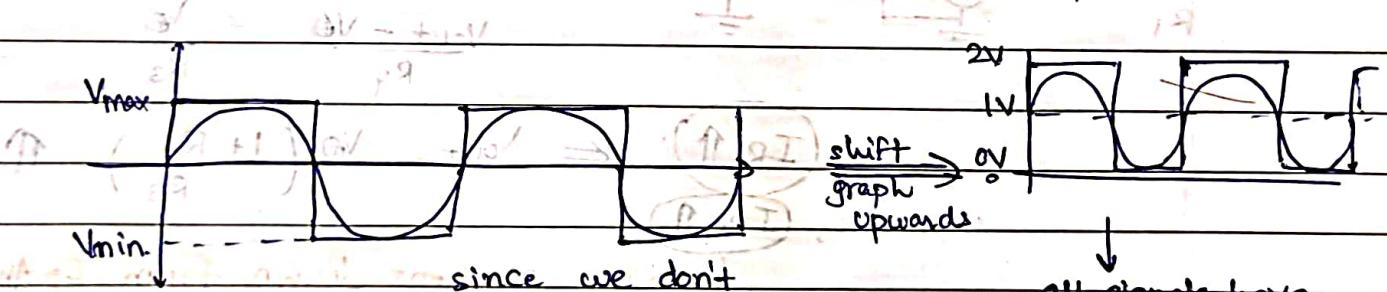
if external supply is -ve,
it is NOT a problem unless the voltage
is +ve at all other points



all signals have a DC value

used everywhere

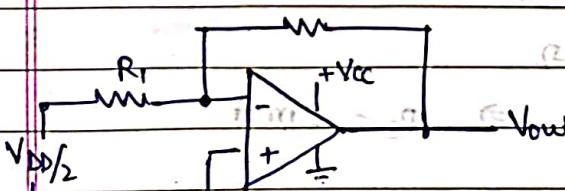ex. supply & $(V_{DD}/2)$ analog output also increases



$$I=0 \rightarrow V_{out} = V_{DD}/2$$


→ (DC does NOT change)

~~$V_{DD}/2$~~

$$+ V_m \sin \omega t \rightarrow \text{average doesn't change} \Rightarrow V_{out} = \frac{V_{DD}}{2} + \left(1 + \frac{R_2}{R_1}\right) V_m \sin \omega t$$


CHARGE SENSITIVE AMPLIFIER

Date _____
Page _____

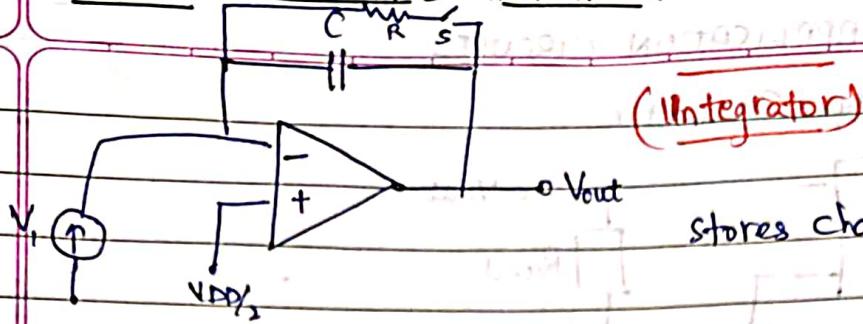

stores charge on the capacitor.

Voltage - To - Current Converter

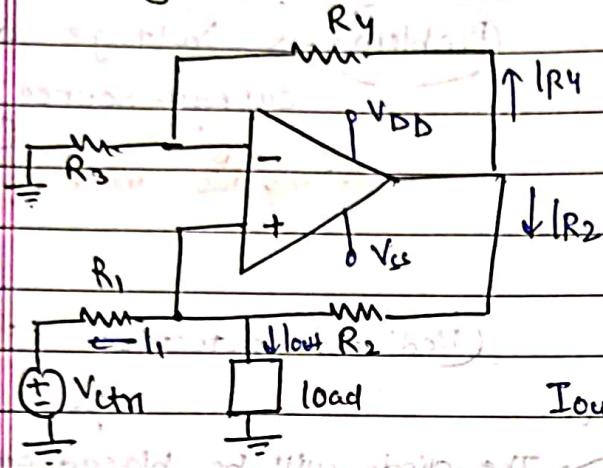

For high values of load,
 $I_{load} = \frac{V_{in}}{R_1}$

$$\left(\text{also: } R_1 = \frac{R_3}{R_4} \right)$$

$$I_{out} = I_{load} = \frac{V_{in}}{R_1} \quad [\text{as } R_{in} = -R_1]$$

$$V_\Theta = I_{out} \times R_L$$

$$V_\oplus = V_{in} \times R_L$$


$$R_1$$

$$R_L \uparrow \Rightarrow V_\Theta \uparrow$$

$$I_{R2} = I_{out} + I_1$$

as $V_\Theta \uparrow$ and
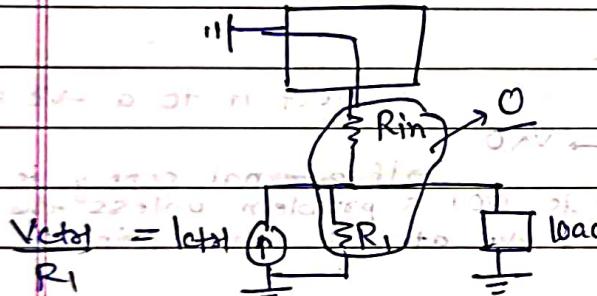
$$V_{out} - V_\Theta = \frac{V_\Theta}{R_3}$$



$$I_{R2} \uparrow$$

$$\text{also, } I_{R4} \uparrow$$

High current drawn from Op Amp supply

$$\text{if, } (I_{out})_{\max.} = 1 \text{ mA}$$

$$(\text{Load})_{\max.} = 3 \text{ k}\Omega \quad (V_\oplus)_{\max.} = 3 \text{ V}$$

$$V_{in} = 1.5 \text{ V} \Rightarrow R_1 = 1.5 \text{ k}\Omega$$

$$I_1 = \frac{3 - 1.5}{1.5 \text{ k}\Omega} = 1 \text{ mA} \Rightarrow I_{R2} = 2 \text{ mA}$$

$$\text{assume } (V_{out})_{\text{opamp, sat}} = 4 \text{ V} \quad \text{for } V_{DD} = 5 \text{ V}$$

$$R_2 < \frac{4 - 3}{2 \text{ mA}} = 0.5 \text{ k}\Omega$$

let's say $R_2 = 0.4 \text{ k}\Omega$ then $R_3 = \frac{R_1 R_2}{R_2} = \frac{1.5 \times 0.4}{0.4} = 3.75$

\Rightarrow If the load is increased: $3 \text{ k}\Omega \rightarrow 5 \text{ k}\Omega$

$$(V_{\text{out}})_{\text{max.}} = \frac{1.5 \times 5 \text{ k}\Omega}{1.5 \text{ k}\Omega} = 5 \text{ V} \quad (\text{V}_{\text{out}} \text{ can't be } 4 \text{ V})$$


$$I_1 = \frac{5 - 1.5}{1.5} = 2.3 \text{ mA} \Rightarrow I_{R_2} = 3.3 \text{ mA}$$

\Rightarrow Assume $(V_{\text{out}})_{\text{sat}} = 7 \text{ V}$ for $V_{DD} = 8 \text{ V}$


$$R_2 < \frac{7 - 5}{2.3 \text{ mA}} = 0.6 \text{ k}\Omega \quad R_2 = 0.5 \text{ k}\Omega \Rightarrow \frac{R_3}{R_4} = 3$$

MODIFIED HOWLAND CURRENT SOURCE

(High values of load)

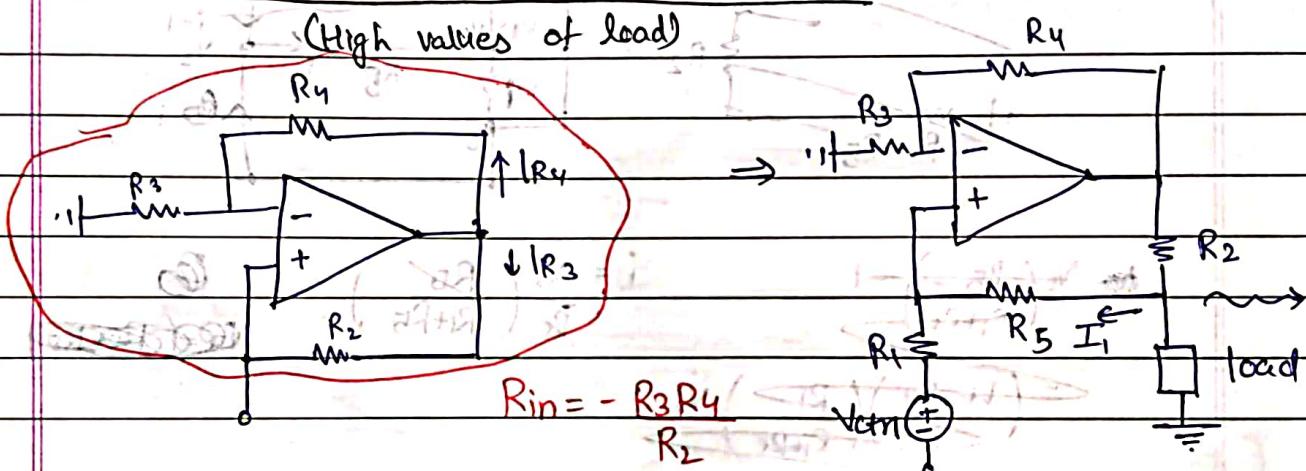


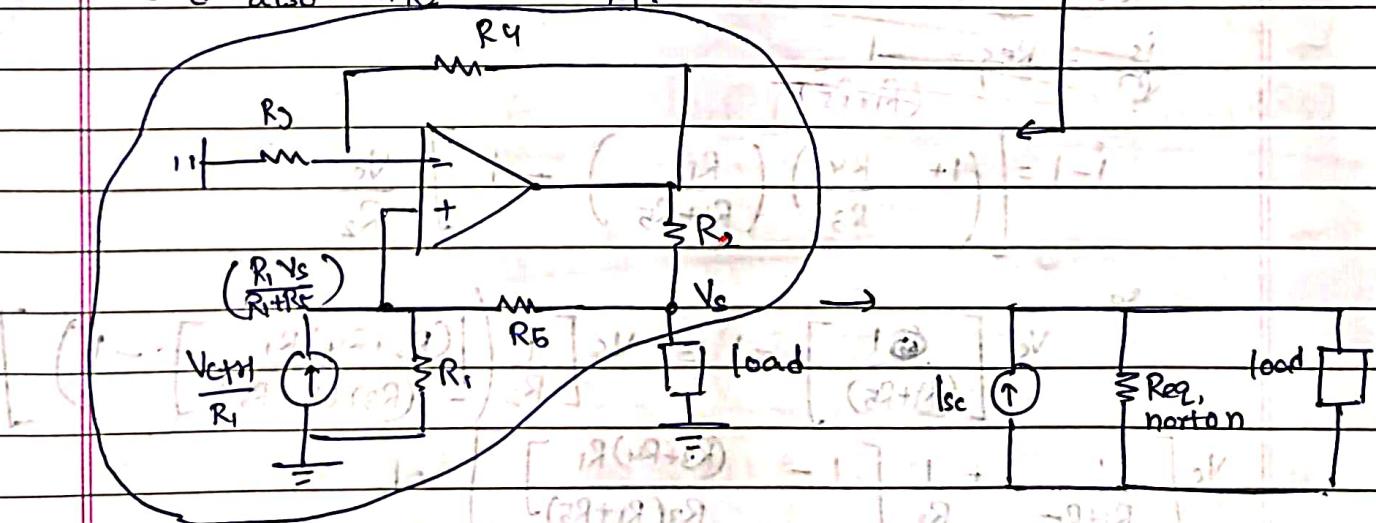Moving load away from \oplus terminal of OpAmp reduces V_T and also I_{R_2} and I_{R_4} .





OPEN-CIRCUIT \Rightarrow

(and remove voltage sources)

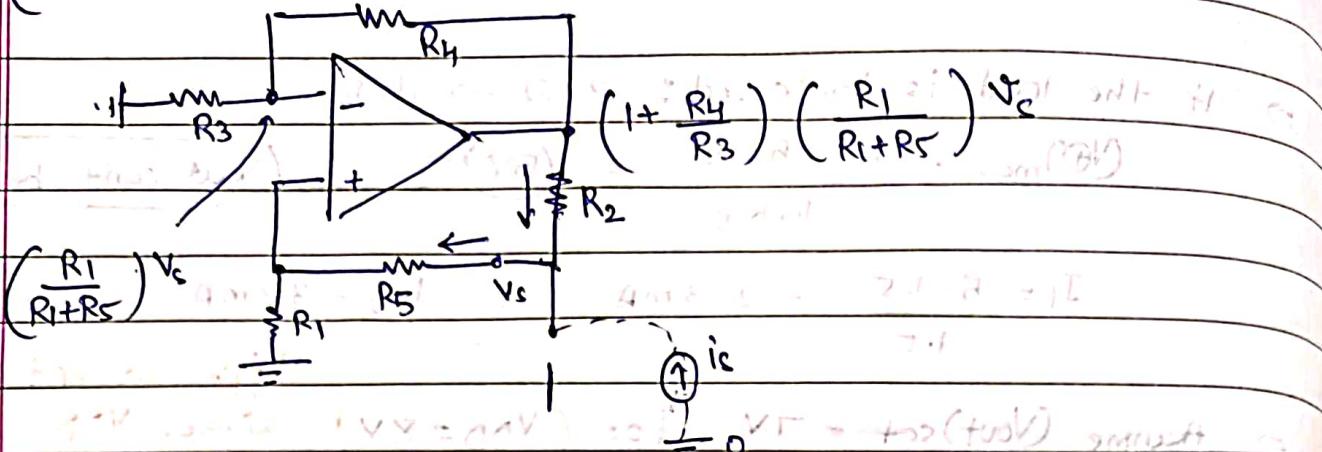

$$G_{eq} = 1 = 0$$

R_{eq}

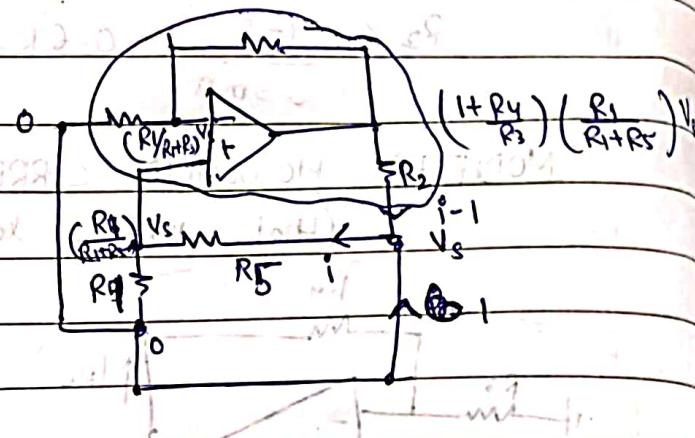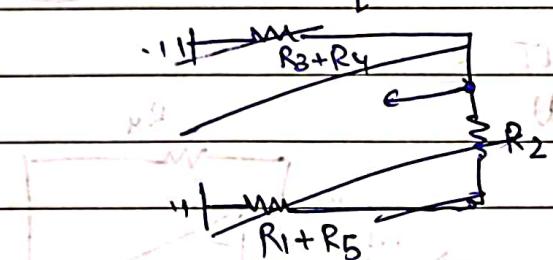

$$\textcircled{2} \quad V_s \left(\frac{R_5}{R_1 + R_5} \right) - 1$$

$$i = V_s \left(\frac{R_5}{R_1 + R_5} \right)$$

$$\textcircled{3} \quad \left(1 + \frac{R_4}{R_3}\right) \left(\frac{R_1}{R_1 + R_5}\right) V_s$$

$$\textcircled{4} \quad N_s \left(\frac{1}{\left(R_1 + R_5 \right)} \left(R_5 - R_1 \left(1 + \frac{R_4}{R_3} \right) \right) \right) = 1$$

$$\textcircled{5} \quad i_s = R_{eq} = \frac{1}{\left(R_1 + R_5 \right)}$$

$$i - 1 = \left[\left(1 + \frac{R_4}{R_3}\right) \left(\frac{R_1}{R_1 + R_5}\right) - 1 \right] \frac{V_s}{R_2}$$

so,

$$V_s \left[\frac{1}{\left(R_1 + R_5 \right)} - 1 \right] = V_s \left[\frac{1}{R_2} \left(\left[\frac{\left(R_3 + R_4 \right) R_1}{\left(R_3 \right) \left(R_1 + R_5 \right)} \right] - 1 \right) \right]$$

$$V_s \left[\frac{1}{R_1 + R_5} + \frac{1}{R_2} \left[1 - \frac{\left(R_3 + R_4 \right) R_1}{R_3 \left(R_1 + R_5 \right)} \right] \right] = 1$$

$$G_{eq} = \frac{1}{R_1 + R_5} + \frac{1}{R_2} \left[\frac{R_3 R_1 + R_3 R_5 - R_2 R_1 - R_4 R_1}{R_3 \left(R_1 + R_5 \right)} \right]$$

$$G_{eq} = \frac{1}{R_1 + R_5} + \frac{1}{R_2} \left[\frac{(R_5/R_1) - (R_4/R_3)}{(1+R_5/R_1)} \right] = 0$$

$$\text{So, } \frac{1}{R_1} + \frac{1}{R_2} \left(\frac{R_5}{R_1} \right) = \frac{1}{R_2} \left(\frac{R_4}{R_3} \right)$$

$$R_2 + R_5 = R_1 R_4$$


$$\frac{R_2 + R_5}{R_1} = \frac{R_4}{R_3}$$

$$R_4 = R_2 + R_5$$

$$R_3$$

$$R_3$$

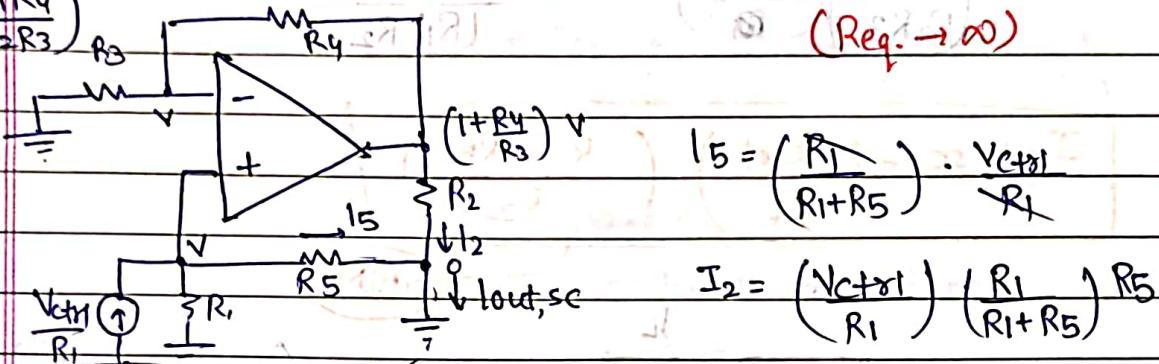
$$\frac{1+R_5}{R_2} = \frac{R_1 R_4}{R_2 R_3}$$



$$I_5 = \frac{R_1}{R_1 + R_5} \cdot V_{ctrl}$$

$$I_2 = \left(\frac{V_{ctrl}}{R_1} \right) \left(\frac{R_1}{R_1 + R_5} \right) R_5 \left(1 + \frac{R_4}{R_3} \right) \cdot \frac{1}{R_2}$$

$$I_2 = (R_1 || R_5) V_{ctrl} \left(1 + \frac{R_4}{R_3} \right) \left(\frac{1}{R_2} \right)$$

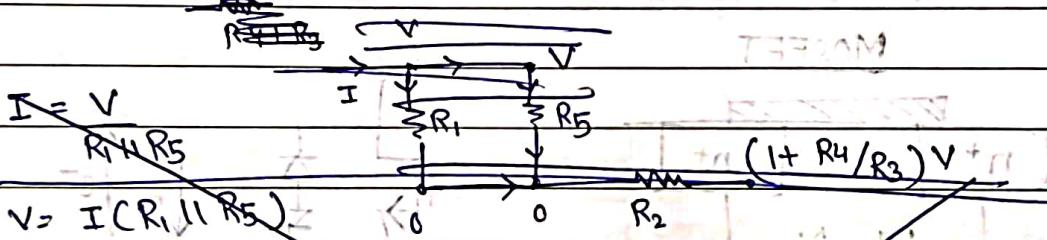

$$\text{and so } I_2 = \left(\frac{1+R_4}{R_3} \right) \frac{V}{R_2} = \left(\frac{1+R_4}{R_3} \right) \frac{V_{ctrl}}{R_1 R_2} (R_1 || R_5)$$

~~$$I_2 = \left(\frac{R_3 + R_4}{R_3} \right) \left(\frac{V_{ctrl}}{R_2} \right) \left(\frac{R_5}{R_1 + R_5} \right)$$~~

~~$$\text{So, } I_{SC} = \frac{V_{ctrl}}{R_1} \left(\frac{R_1}{R_1 + R_5} + \left(\frac{1+R_4}{R_3} \right) (R_1 || R_5) \cdot \frac{1}{R_2} \right)$$~~

~~$$R_4 = R_2 + R_5$$~~

~~$$V = I (R_1 || R_5) + \frac{R_1 + R_2 + R_5}{R_2} \left(\frac{R_1 R_5}{R_1 + R_5} \right) \cdot \frac{1}{R_2}$$~~

~~$$V = I (R_1 || R_5)$$~~

~~$$\left(\frac{1+R_4}{R_3} \right) (R_1 || R_5) \cdot \frac{1}{R_2} \left(\frac{V_{ctrl}}{R_1} \right)$$~~

~~$$+ \left(\frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{R_2 R_1} \right) \left(\frac{R_1 R_5}{R_1 + R_5} \right) \cdot \left(\frac{V_{ctrl}}{R_1} \right)$$~~

$$I_2 = \left(1 + \frac{R_4}{R_3}\right) \left(\frac{R_1 R_5}{R_1 + R_5}\right) \left(\frac{V_{ctrl}}{R_1}\right) \left(\frac{1}{R_2}\right).$$


$$I_{sc} = \frac{R_1}{R_1 + R_5} \cdot \frac{V_{ctrl}}{R_1} \left[\frac{R_5 \left(1 + \frac{R_4}{R_3}\right) + 1}{R_2} \right]$$

$$= \left(\frac{R_1}{R_1 + R_5}\right) \frac{V_{ctrl}}{R_1} \left[\frac{R_5 R_4 + R_1 R_4}{R_2 R_3} \right]$$

$$= \left(\frac{R_4}{R_2 R_3}\right) \left(\frac{V_{ctrl}}{R_1}\right) = \frac{R_2 + R_5}{(R_1) R_2} \cdot V_{ctrl}$$


$$I_{out, sc} = \left(\frac{V_{ctrl}}{R_1}\right) \left(\frac{R_2 + R_5}{R_2}\right)$$

(GAIN)

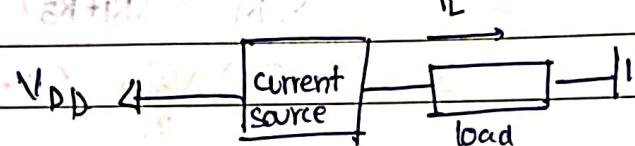

(equivalent circuit)

MOSFET

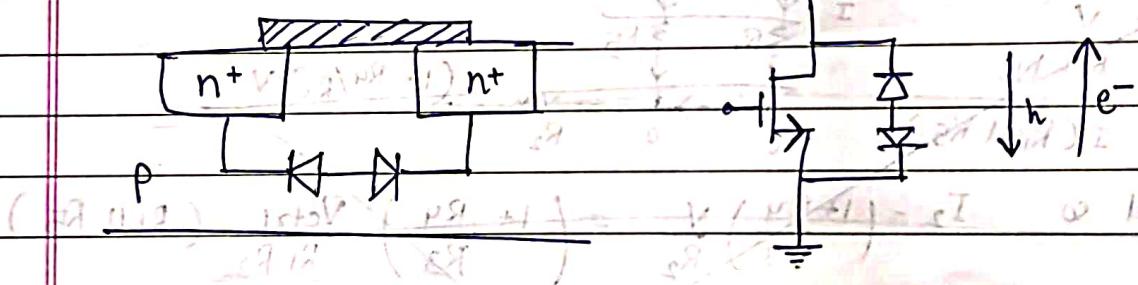 $\text{SiO}_2 \rightarrow \text{breakdown} \rightarrow T \text{ reaches a max}^m \text{ value}$ $\rightarrow \text{SiO}_2: E_{max} \approx 0.5 \text{ V nm}$ 4nm oxide $\rightarrow 2V \rightarrow \text{breakdown.} \Rightarrow$

Not reversible

 \rightarrow blw gate and any part of channel, voltage shouln't be more than?so, we have a $(V_{gs})_{max} = (V_{gd})_{max} = (V_{gb})_{max} = 1.8V$

for core devices in 180nm CMOS technology

I_D

saturation:

$$I_D = \frac{1}{2} nC_{ox} \frac{W}{L} (V_{GSt})^2 (1 + \lambda V_{DS})$$

 V_{GSt} $V_{GSt} < V_{GSc}$

$$V_{DC} > V_{GSt}$$

$$I_D = \frac{1}{2} nC_{ox} \frac{W}{L} (V_{GSt})^2 [1 + \lambda (V_{DS} - V_{GSt})]$$

 $(i=1/2\dots)$

saturation region


$$\frac{\Delta I_D}{\Delta V_{DS}} = I_D \cdot \lambda$$

$$so, R_{out} = \frac{1}{\lambda I_D}$$

CMOS OpAmp Specifications

- V_{DD} range → input capacitance
- open-loop gain (A_V) → output impedance
- unity gain frequency → input offset voltage
- input CM voltage range → output slew rate
- output voltage range

OpAmp Gain Limitation

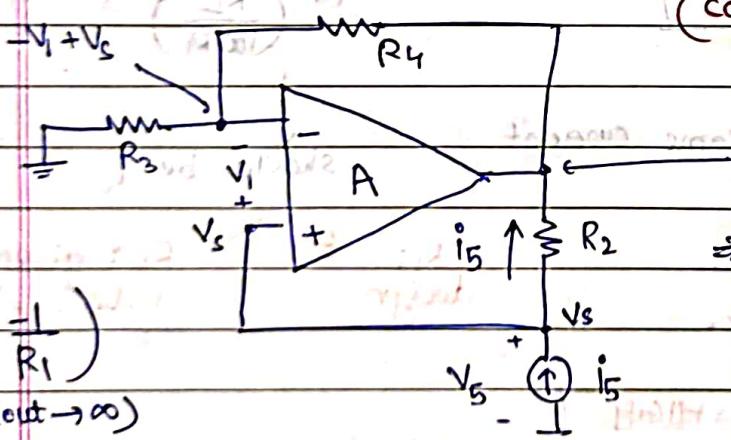(condition for R_i depends on A_V)

$$AV_1 = \left(1 + \frac{R_4}{R_3}\right) (V_s - V_1)$$

$$\Rightarrow AV_1 = A \left(1 + \frac{R_4}{R_3}\right) \cdot V_s$$

$$V_{R2} = V_s - AV_1 \Rightarrow i_s = \frac{V_s - AV_1}{R_2}$$

Req can be computed ← we get i_s as a function of V_s

$i \rightarrow$ function of a load

MISMATCH EFFECTS

$$eg.- \frac{R_4}{R_3} = \frac{R_2}{R_1} (1 - \epsilon) \quad \epsilon: \text{small no.}$$

in a Howland VCCS

Let $\epsilon = \pm 1\% \Rightarrow 0.99R_2 \leq R_4 \leq 1.01R_2$ $\frac{R_2}{R_1} \leq \frac{R_4}{R_3} \leq \frac{1.01R_2}{R_1}$ \rightarrow limited output resistance

$$\begin{aligned} G_{out} &= -\frac{R_4}{R_2 R_3} + \frac{1}{R_1} \\ &= \frac{1}{R_1} \left[1 - \frac{R_1 \cdot R_4}{R_2 \cdot R_3} \right] \\ &= \frac{1}{R_1} \left(1 - \frac{R_4/R_3}{R_2/R_1} \right) = \frac{1}{R_1} (\epsilon) \end{aligned}$$


$+0.01/R_1$
 $-0.01/R_1$

circuit may become unstable.

boundary values :-

$$\begin{aligned} G_{out} &\Rightarrow \begin{cases} \frac{0.01}{R_1} & R_{out} = 100R_1 \\ -\frac{0.01}{R_1} & R_{out} = -100R_1 \end{cases} \\ &\quad \text{stability output} \end{aligned}$$
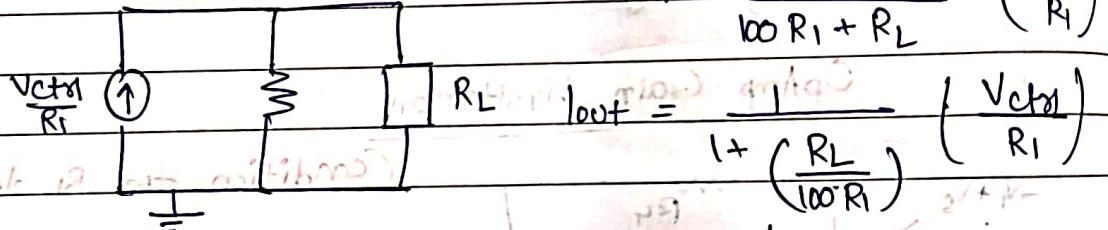
$$I_{out} = \frac{100R_1}{100R_1 + R_L} \cdot \left(\frac{V_{ctrl}}{R_1} \right)$$



$R_1 \uparrow \rightarrow V_{ctrl} \uparrow$ for same current


should be 1

worst case error: $\frac{(R_L)}{(100R_1)} \rightarrow \max.$

$R_1:$ design

$R_L:$ given
(change)

$R_L \rightarrow \text{HIGH}$

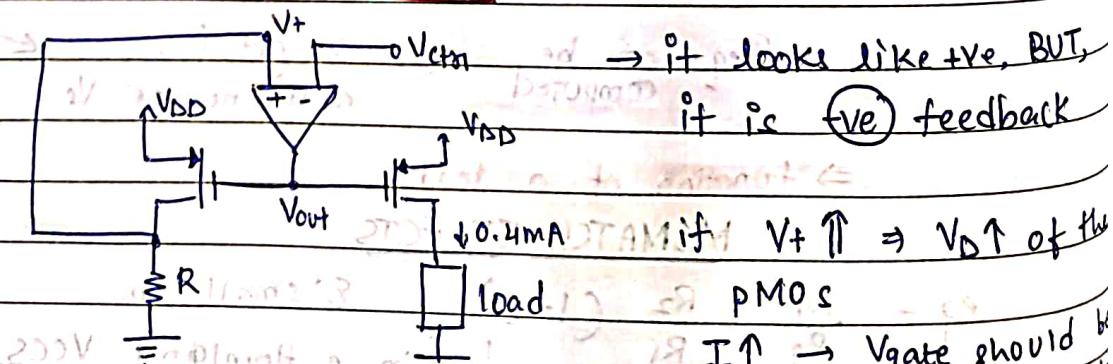

Hence, it is a
-ve feedback

so, V_{out}



$$V_{sg} = (V_{DD} - V_g)$$

$$I = K [V_{sg} - V_{g}]^2$$

$I \uparrow \rightarrow V_{gate}$ should be lesser for I to be higher

MODEL AND ANALYSIS FOR SIGNAL AMPLIFICATION

CIRCUIT inside CMOS OpAmp

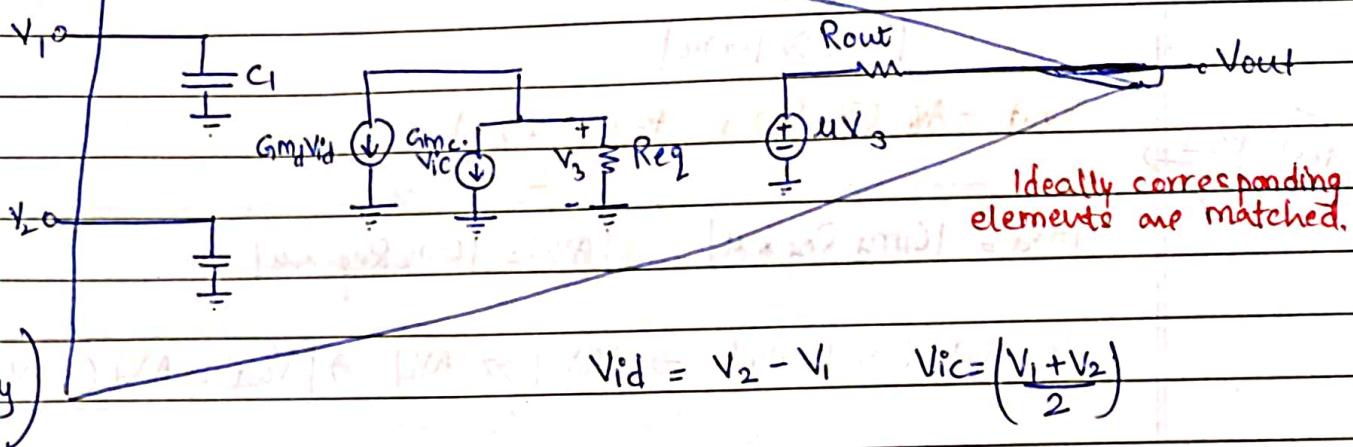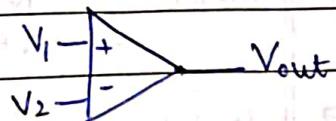

CMOS OpAmps are designed based on MOSFET's biased as signal amplifying elements and other analog operations.

$$V_{ic} = V_1 = V_2 ; V_{id} = 0$$

$$\text{if } V_1 = -V_2$$

$$V_{id} = 2V_1 ; V_{ic} = 0$$

2 VCC → respond to V_{id}, V_{ic} → currents added

↓
amplify the voltage.

$$\textcircled{1} |G_{md}| \ll |G_{mc}|$$

$$\textcircled{2} \text{ Req : High , Rout : Low/Medium}$$

⇒ 0° phase difference, $V_{ic} \approx \text{average}$; 180° phase difference, $V_{ic} \approx 0$.

$$\textcircled{3} G_{mc} : \text{very small}$$

$$\text{eg. } G_{md} = 1 \text{ mA/V} \quad \text{Req} = 500 \text{ k}\Omega \quad ; \quad G_{mc} = 0.1 \mu\text{A/V}$$

$$\text{so, } |G_{md} \text{ Req}| = 500$$

diff. mode gain

$$|G_{mc} \text{ Req}| = 0.05$$

common mode gain

$$\text{CMRR (common-mode rejection ratio)} = \left| \frac{G_{md} \cdot \text{Req}}{G_{mc} \cdot \text{Req}} \right|$$

$$\text{CMRR} = \left(\frac{500}{500 \times 10^{-4}} \right) \rightarrow 20 \log \left(\frac{500}{500 \times 10^{-4}} \right)$$

$$\boxed{\text{CMRR} = 80 \text{ dB}}$$

both the currents are added & flowing together.

⇒ MOSFET is a non-linear element → how to get a linear OpAmp behavior from the MOSFET

⇒ Special model doesn't have $V_{out} = A_v(V_1 - V_2)$ except in special condition
 $|G_{md}| \gg |G_{mc}|$.

$$V_{out} = A_v (V_1 - V_2) + A_v \left(\frac{V_1 + V_2}{2} \right)$$



realistic model

$$|AV_d| = |G_{md} \text{Req} \times u| \quad |AV_c| = |G_{mc} \text{Req} \times u|$$

$$\text{If } |G_{md}| \gg |G_{mc}| \Rightarrow |AV_d| \gg |AV_c| \Rightarrow V_{out} = A_v V_d (V_1 - V_2)$$

Approximate Linear Amplification from a Transistor circuit

where to put \ominus ?

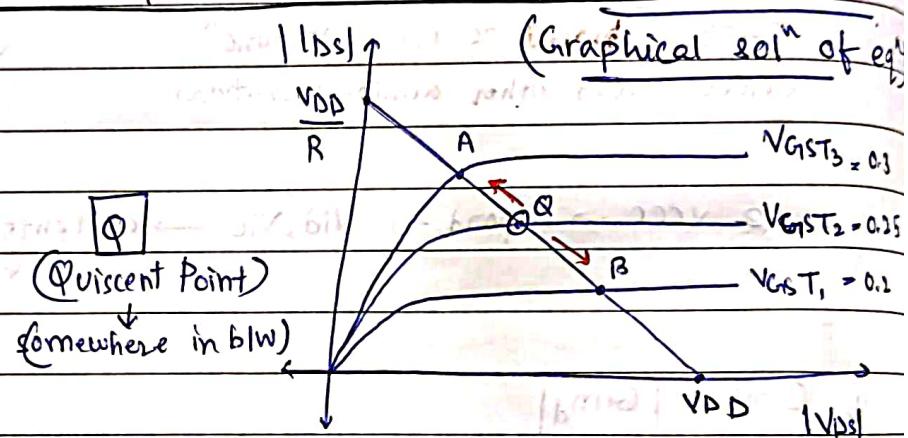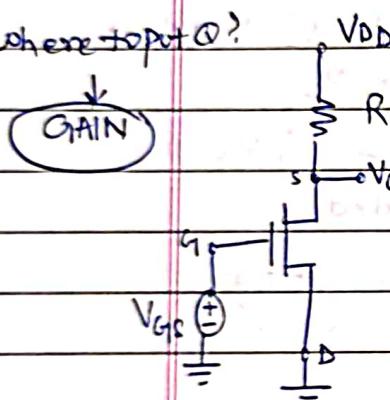

$$|V_{ds}| > |V_{gs} - V_T|$$

$$\text{i.e. } |V_{ds}| > |V_{gst}|$$

$$V_{DD} = R I_D + V_{DS}$$

$$I_D = \frac{V_{DD} - V_{DS}}{R}$$

$$V_{gs} = 0.25 \pm \Delta V_{gs}$$

$$\Delta V_{gs} = \begin{cases} +50\text{mV (A)} \\ 0 \\ -50\text{mV (B)} \end{cases}$$

as we ↑ V_{gst} , threshold moves to Right [Don't consider linear region]

⇒ As, $V_{gst} \downarrow \Rightarrow I_D \downarrow$ as $V_{ds} \uparrow$ or $[V_{ds} \downarrow \Rightarrow I_D \uparrow]$

(on changing V_{gst} also)

e.g. $R = 10\text{k}\Omega$ λ : negligible, $\mu n C_{ox} = 400 \frac{\text{nF}}{\text{V}}$, $w/L = 10$, $V_{DD} = 3\text{V}$

$$\begin{aligned} V_{gstA} &= 0.3 \\ V_{gstB} &= 0.25 \\ V_{gstC} &= 0.2 \end{aligned} \rightarrow \begin{cases} I_D = 180\text{mA} \\ I_D = 125\text{mA} \\ I_D = 80\text{mA} \end{cases} \Rightarrow \begin{cases} V_{ds} = 1.2\text{V} \\ V_{ds} = 1.78\text{V} \\ V_{ds} = 2.2\text{V} \end{cases}$$

(using line eqn)

Date _____
 Page _____

NOT THE SAME \rightarrow limit or more than 50mV,
 ΔV_{GST} the diff. is lesser.

$$\frac{\Delta V_{DSA}}{\Delta V_{GST}} = \frac{-0.58}{0.05} = -11.6$$

$$\frac{\Delta V_{DSB}}{\Delta V_{GST}} = \frac{0.42}{0.05} = +8.4$$


$$\Delta V_{DST} \approx (10 \text{ times}) \Delta V_{GST}$$

(Amplification of incremental values.)

- we get an almost linear behavior for incremental values from MOSFET.
- all the variables in V_{out} are incremental variables.
 e.g. - voice - incremental change in the signal.
 ↳ amplifier → increases the incremental values.

$$\Rightarrow \Delta V_{GST} = 10 \text{ mV} / 20 \text{ mV} / 30 \text{ mV} \quad (\text{linear} \rightarrow \text{nonlinear})$$

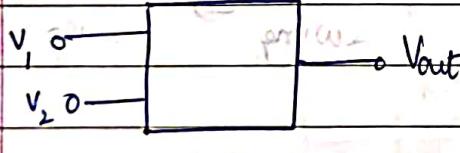- Voltage and current compliance
- Voltage and current rating



NOISE \otimes

$$V_{out} = A(V_1 - V_2)$$

$$(V_{id} = 0) \quad \hookrightarrow V_{out} = 0 \quad (\text{Difference Amplifier})$$

$$V_1 = -V_2 \Rightarrow V_1 - V_2 = 2V_1 = -2V_2 \Rightarrow$$

$$V_1 = \frac{V_{id}}{2} \quad V_2 = \frac{-V_{id}}{2}$$

entire info. is passed

ideal condition

$$\text{reality) } V_1 = \frac{V_{id}}{2} + x \quad V_2 = \frac{-V_{id}}{2} + y \rightarrow$$

$$x = y = \frac{V_1 + V_2}{2}$$

and

$$V_1 = -V_2$$

$$(V_1 - x = y - V_2)$$

$$x + y = V_1 + V_2$$

(common-mode)
 (shows up)



$$V_{id} = V_1 - V_2$$

$$V_{ic} = \frac{V_1 + V_2}{2}$$

$$V_1 = \frac{V_{id} + V_{ic}}{2}$$

$$V_2 = \frac{-V_{id} + V_{ic}}{2}$$

as long as the circuit \Rightarrow superposition
is linear

see effect of V_{id} $+$ see effect of V_{ic}

For some linear circuit, $y = aV_{id} + bV_{ic}$,


$$a = \frac{y}{V_{id}} \quad |_{V_{ic}=0}$$

$$b = \frac{y}{V_{ic}} \quad |_{V_{id}=0}$$

superposition principle

Also note:- $|bV_{ic}| \ll |aV_{id}|$

in real conditions $\rightarrow |V_{ic}| \gg |V_{id}| \rightarrow$ ImV signal and
|V noise is NOT

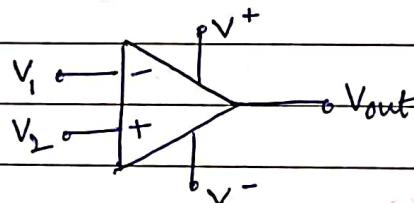

$$\text{CMRR} > 100 \text{ dB}$$

$$\text{i.e. } \left| \frac{A_d}{A_c} \right| > 100 \text{ dB}$$

\Rightarrow if the signal has a \Rightarrow pull Q. down; $-ve$ swing \Rightarrow pull Q. up;
+ve swing only

$$V_{GSI} = V_{GSI,Q} + \Delta V_{GSI}$$

$$\Delta I_D = \left(\frac{\partial I_D}{\partial V_{GS}} \right) \Delta V_{GSI} + \left(\frac{\partial I_D}{\partial V_{DS}} \right) \Delta V_{DS}$$

find (ΔI_D) at Q

TWO-PORT

$$V_{GS} = V_{GSQ} + \Delta V_{GS}$$

$$I_D = f(V_{GS}, V_{DS})$$

$$\Delta I_D = \frac{\partial f}{\partial V_{GS}}$$

$$V_{GS} = V_{GSQ}$$

$$V_{DS} = V_{DSQ}$$

$$\Delta V_{GS}$$


$$\Delta V_{DS}$$

$$(V_{GS} - V_{GSQ}) + \frac{\partial f}{\partial V_{DS}} \Delta V_{DS}$$

$$(V_{DS} - V_{DSQ})$$

$$V_{GS} = V_{GSQ}$$


$$V_{DS} = V_{DSQ}$$

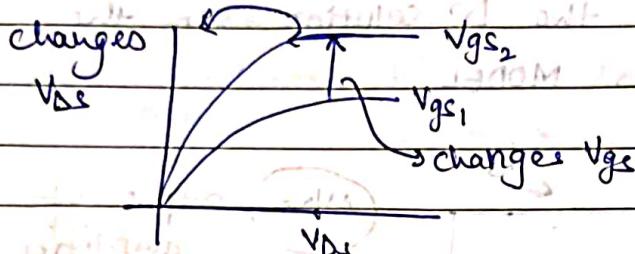

$$\text{So, } \Delta I_D = G_m \Delta V_{GS}$$


V_{DS} : constant

V_{GS} : constant.

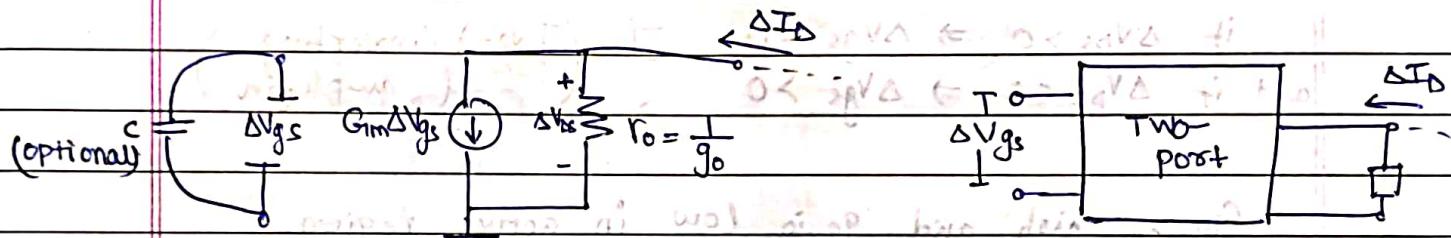

Assumptions:- $\Rightarrow \Delta V_{GS}$ is small

$$\Rightarrow Ig = 0$$

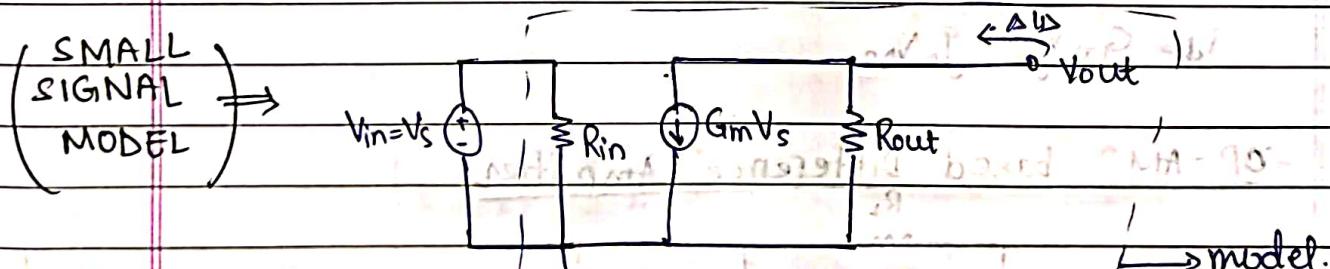


$$V_{GS} = V_{GSQ} + \Delta V_{GS}$$



$$\Delta I_D = G_m \Delta V_{GS} + g_o \Delta V_{DS}$$


DC value of V_{GS} i.e. V_{GSQ} won't appear here

(Model only for small signals)

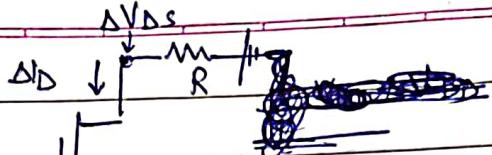

$$\Delta V_{GS} = \frac{\Delta ID}{g_m}$$

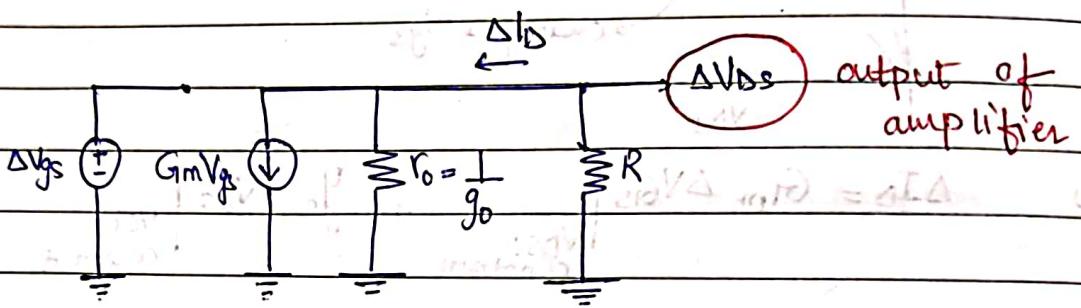→ We are decoupling the DC solution from the incremental changes MODEL.



if $\Delta V_{DS} > 0 \Rightarrow \Delta V_{GS} < 0$
and, if $\Delta V_{DS} < 0 \Rightarrow \Delta V_{GS} > 0$

Two-port (inverting amplifier)

Gm is high and g_o is low in active region.


$$\text{e.g. } G_m = 0.5 \text{ mA/V} \quad R_{out} = \frac{1}{g_o} = 100 \text{ k}\Omega$$

$$G_m R_{out} = 50$$

Intrinsic gain of transistor

$$i_d = G_m V_{GS} + g_o V_{DS}$$

OP-AMP based Difference - Amplifier

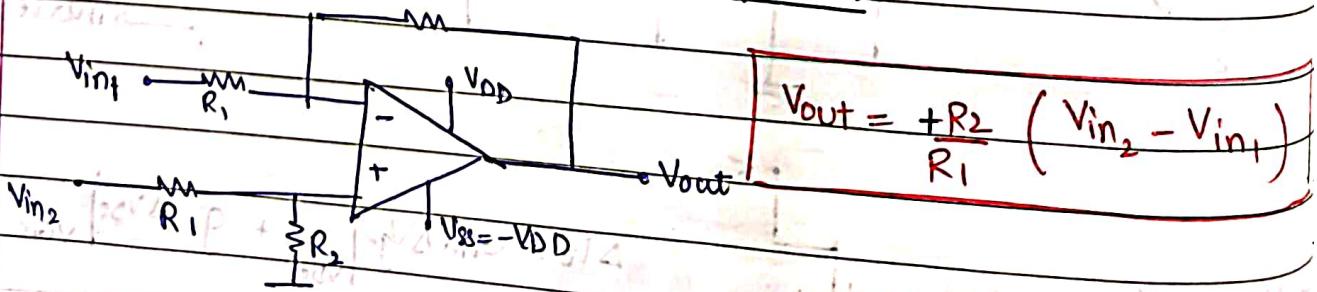

$$V_{out} = +\frac{R_2}{R_1} (V_{in_2} - V_{in_1})$$

Input impedance \rightarrow Differential mode input impedance
 \rightarrow Common mode input impedance.

$$V_{in1} = \frac{V_{id}}{2} + V_{ic}$$



$$V_{in2} = -\frac{V_{id}}{2} + V_{ic}$$

\Rightarrow superposition (linear)


$$V_{id} = V_{in1} - V_{in2} \quad V_{ic} = \frac{V_{in1} + V_{in2}}{2}$$

(Solve in differential mode) + (Solve in common-mode)

$$R_d = \frac{V_{id}}{i_{m,d}}$$

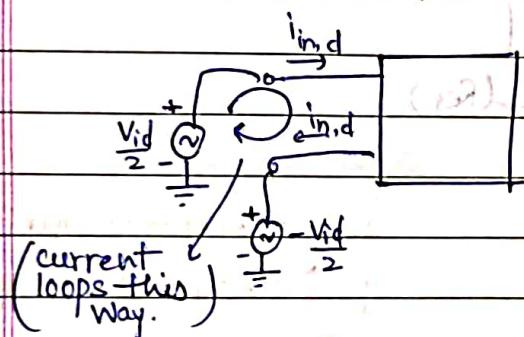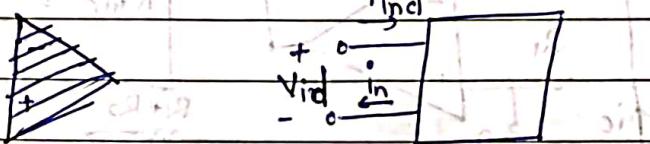

$$R_{ind} = \frac{V_{id}}{i_{ind}}$$

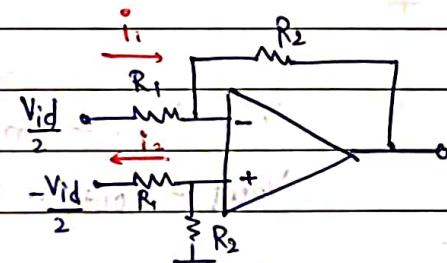

(\ominus \oplus terminals are virtually shorted)


$$i_2 = \frac{V_{id}/2}{R_1 + R_2}$$

$$V_+ = \left(\frac{R_2}{R_1 + R_2} \right) \left(-\frac{V_{id}}{2} \right)$$

$$i_1 = \frac{V_{id}/2}{R_1} + \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{V_{id}}{2} \right) = \frac{\left(\frac{V_{id}}{2} \right)}{R_1} \left[\frac{R_1 + 2R_2}{(R_1 + R_2)R_1} \right]$$


$$R_{ind} \Big|_{V_{id}/2} = \frac{V_{id}/2}{i_1} = \frac{R_1(R_1 + R_2)}{R_1 + 2R_2}$$

$$R_{in} \Big|_{-\frac{V_{id}}{2}} = (R_1 + R_2)$$

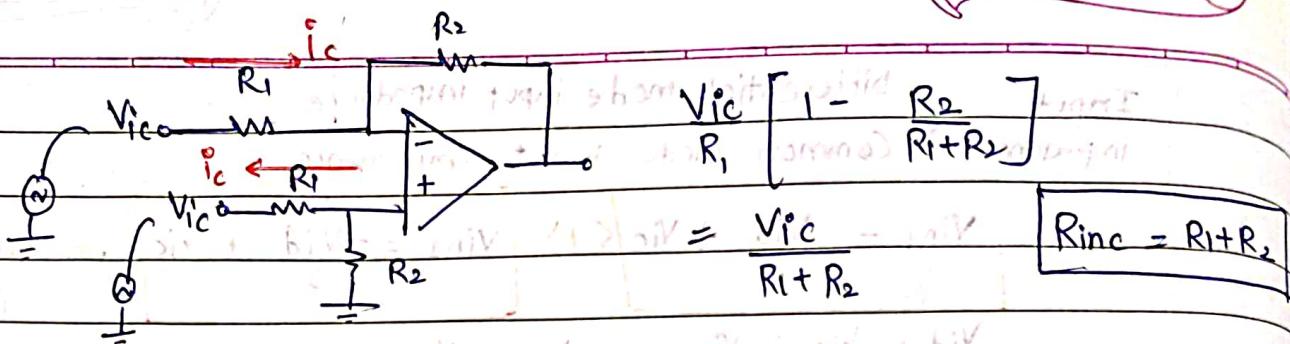


So, we can say that $V_{out} = 0$ as $i_C = \frac{V_{in}}{R_1 + R_2}$

R_1 & R_2 are in series.

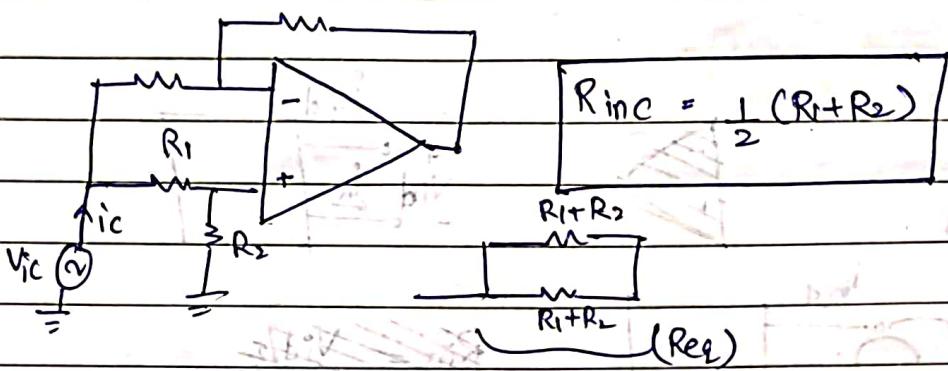

CONFIGURATION - II

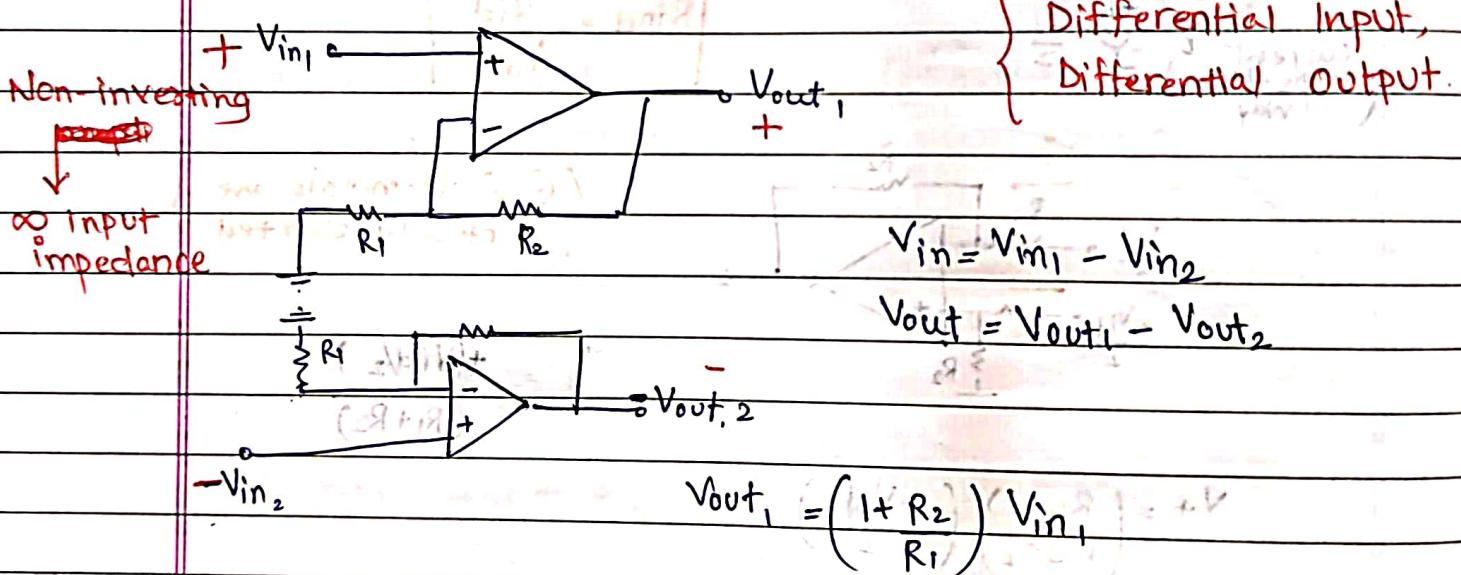


$$+ V_{out2} = \left(1 + \frac{R_2}{R_1}\right) (+ V_{in_2})$$

$$V_{out1} - V_{out2} = \left(1 + \frac{R_2}{R_1}\right) [V_{in_1} - V_{in_2}]$$

differential output differential input


INSTRUMENTATION AMPLIFIER

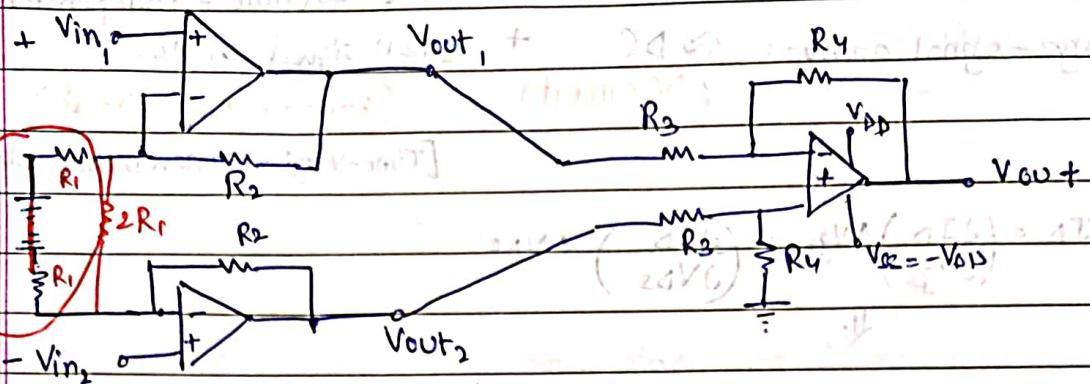


(NOTE :- We practically analyze opAmp circuits in small-signal mode)

⇒ Common-mode gain $\Rightarrow \frac{V_{out}}{V_{ic}} = ?$ $V_{in_1} = V_{in_2} = V_{ic}$
 $V_{out_1} = V_{out_2} = V_{ic}$

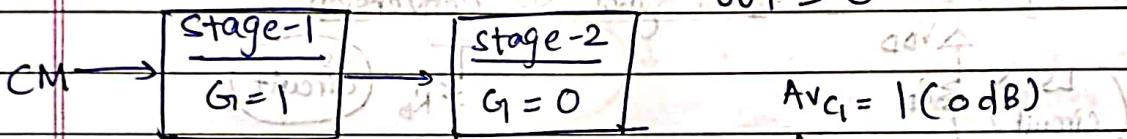
$$V_{out} = 0 \text{ (2J) (ideal)} \quad \text{small signal}$$



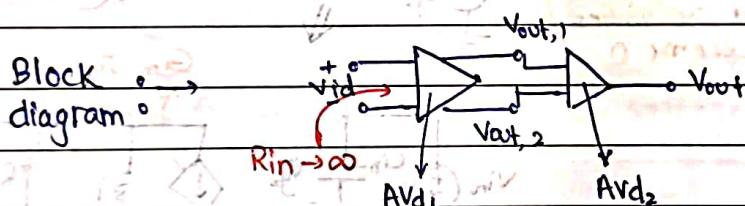⇒ CMRR : High, Rin : High (inverting amplifier), Avd : High → (Ideal)



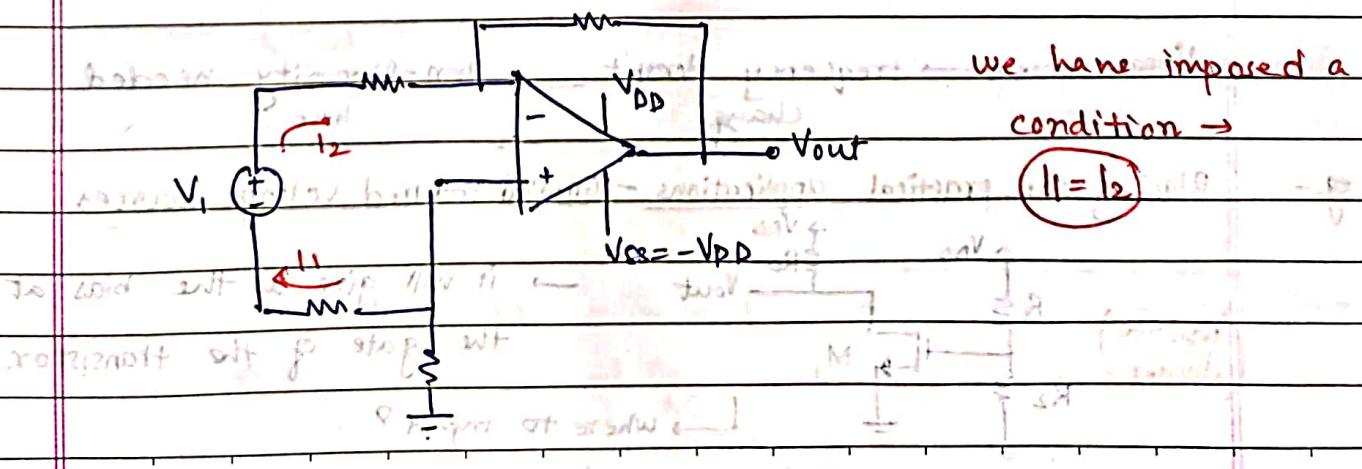
(Signal) S → mv → $\frac{V}{\mu V}$ at the output
 (noise) N_{CM} → v → $\frac{V}{V}$ (rejected)
 $(10^{-3}) \sim (10^6)$



- ⇒ Input-Output Transfer characteristics \Rightarrow (time-independent)
- ⇒ large-signal analysis \approx DC + small signal analysis's
 (DC circuit) (small-signal circuit)
 [Time-varying/incremental change]

$$\Delta I_D = \left(\frac{dI_D}{dV_{GS}} \right) \Delta V_{GS} + \left(\frac{dI_D}{dV_{DS}} \right) \Delta V_{DS}$$


$$I_D = G_m V_{GS} + G_o V_{DS}$$

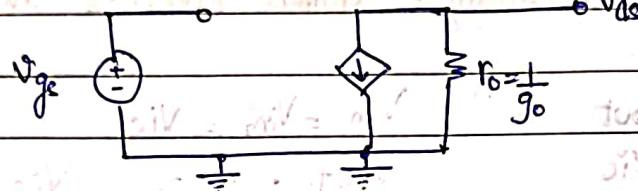

⇒ UNIVERSAL
model


[NMOS/PMOS]

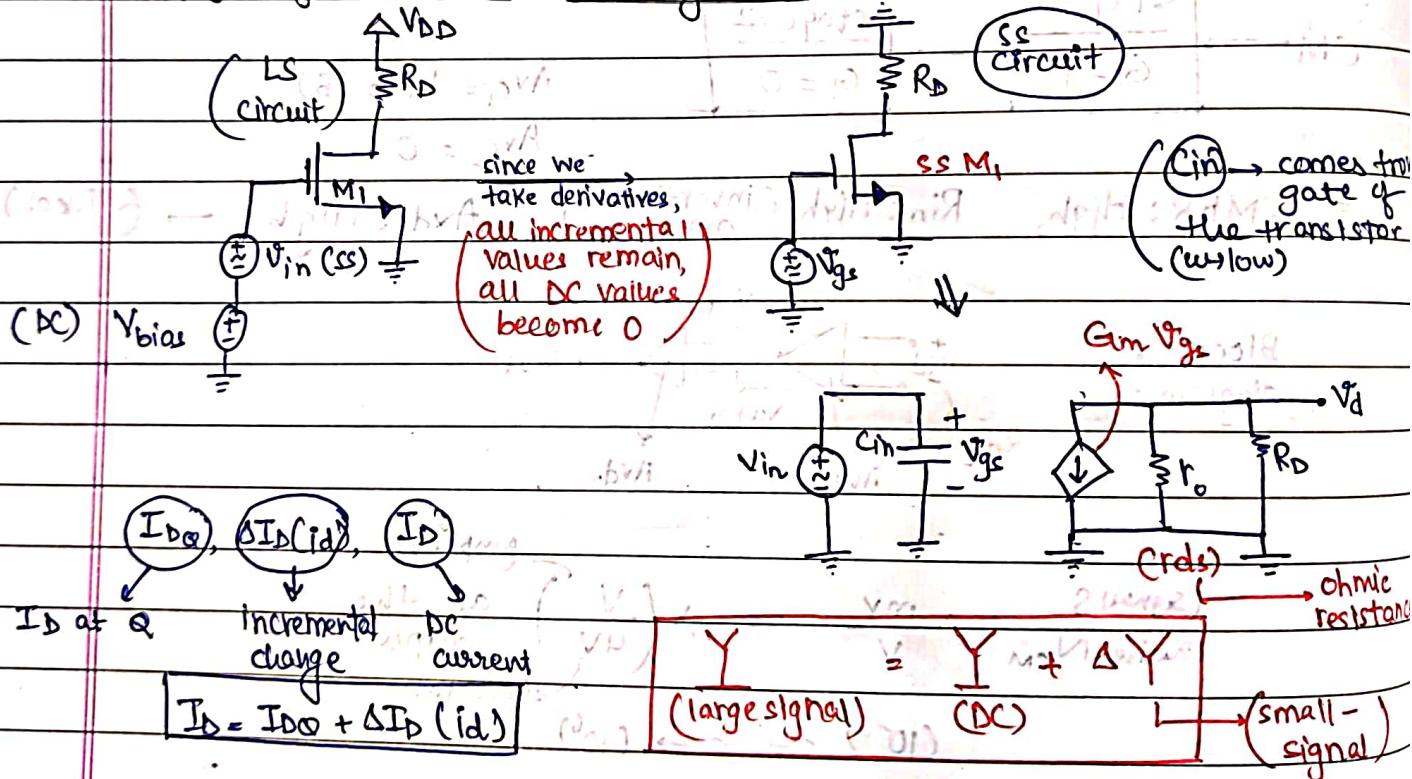Large Signal (LS) to small Signal (SS) conversion




linear system \rightarrow frequency doesn't change \rightarrow non-linearity needed here.

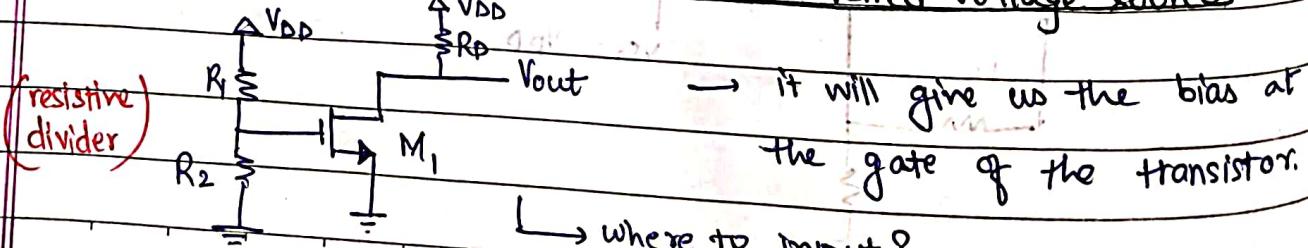e.g. - Biasing for practical applications - Ground-referred voltage sources




Where to connect?

Opt.-1

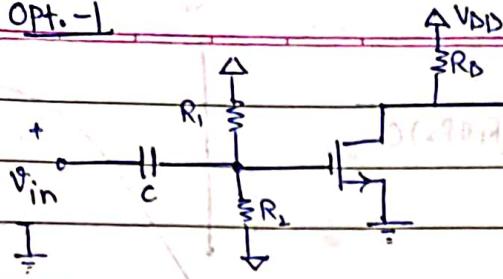

→ Capacitor is high enough to be considered shorted at frequencies of signal V_{in}

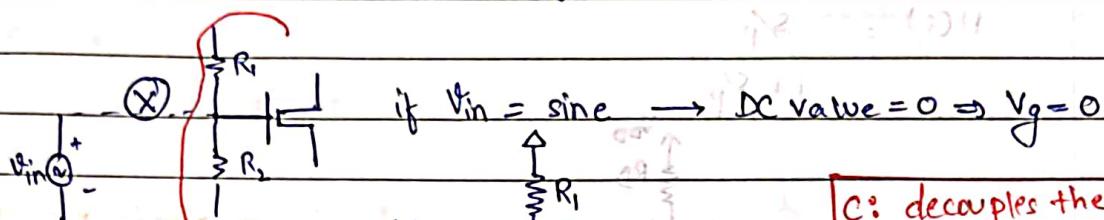(Assume V_{in} does NOT have DC signal information)



C: decouples the DC signal on both of its sides

$$(V_{GS})_S = V_g = \frac{V_{DD}}{R_1 + R_2}$$

($C \approx 100\mu F$)

Small signal part

$Z = \frac{1}{j\omega C} \downarrow \rightarrow$ acts like a short even at low frequencies.

$\frac{1}{C}$ \Rightarrow reactance \uparrow as capacitance \uparrow


$i_{max \sin \omega t}$

$$V_C = \frac{i_{max} (\cos \omega t)}{\omega C}$$

$$V = \int i \cdot dt$$

capacitance $\uparrow \rightarrow$ can't change its voltage as fast as the current.

⇒ equivalent circuit

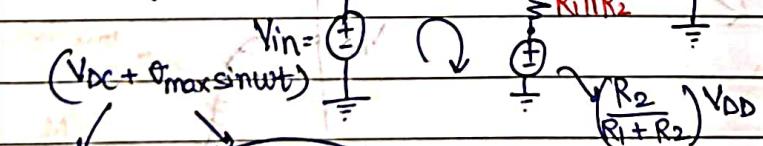

[C: high]

DC component
AC component

creates a current i_{in} in the capacitor


$$V_C = V_{in} - R_2 \frac{V_{DD}}{R_1 + R_2} - V_m \sin \omega t$$

Small signal \rightarrow short the capacitor and block DC


$$V_C = V_{in} - \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} - V_m \sin \omega t \Rightarrow V_C = (V_{in})_{DC} - \left(\frac{R_2}{R_1 + R_2} \right) V_{DD}$$

DC signal part
($i=0$ as $w \rightarrow 0$)

AC signal part → Voltage across
($i \rightarrow ciss.c.$) $R_1 || R_2$

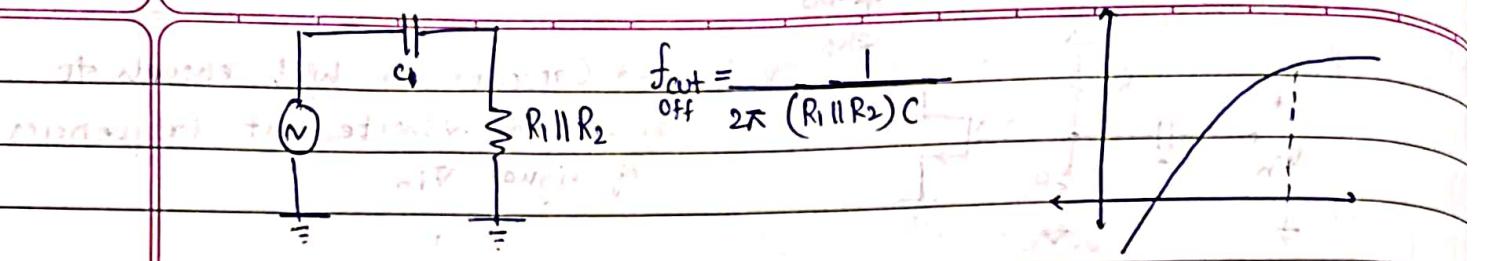

$$H(s) = \frac{s/p}{1 + s/p}$$

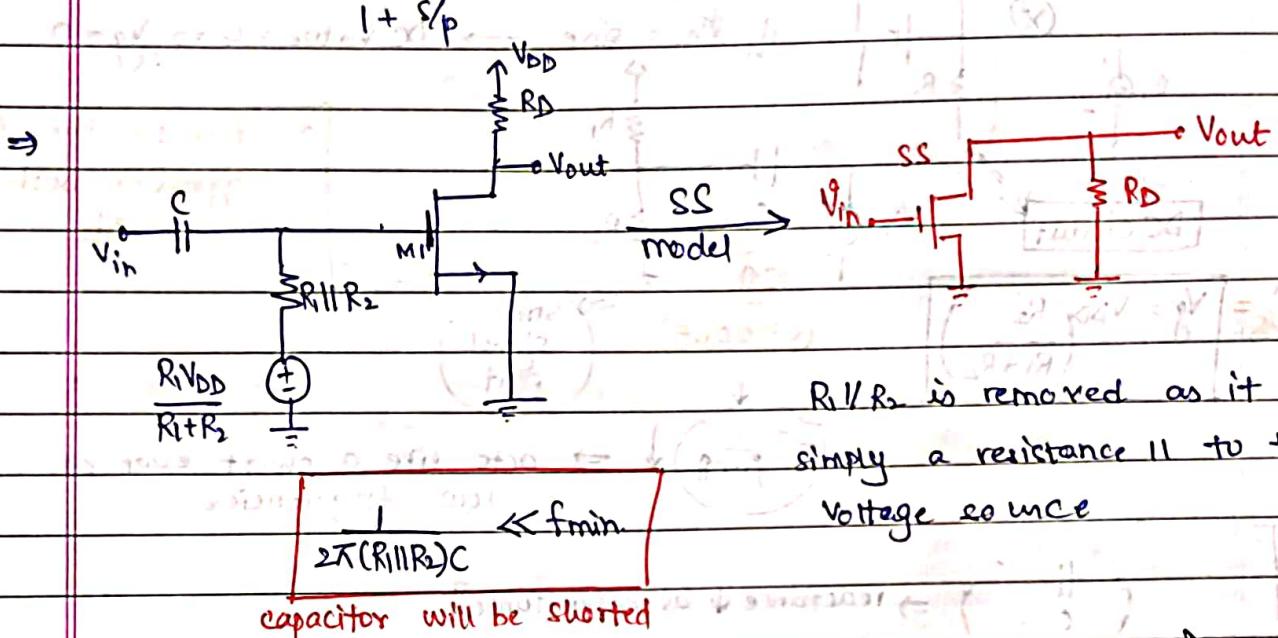

$$V_{\text{out}} = -g_m(R \parallel r_o) V_{\text{in}}$$

$$\text{slope} = \frac{dV_{\text{out}}}{dV_{\text{in}}} = -g_m(R \parallel r_o)$$

low frequency transfer function

Note :- The relⁿ blw parameters are

$$I_{DQ} = \frac{4n}{2} C_{\text{ox}} \left(\frac{W}{L} \right) \left[(V_{GST})^2 \right] \left[1 + \lambda (V_{DS} - V_{GSQ}) \right] \quad \text{corresponds to active region}$$


For active region ONLY,

$$V_{DS,Q} = V_{GST}$$



$$r_o = \left(\frac{\partial I_D}{\partial V_{DS}} \right)_{\text{const } V_{GS}} \quad \Rightarrow \quad r_o = \frac{1}{\lambda I_D}$$

$$g_m = \left(\frac{\partial I_D}{\partial V_{GS}} \right)_{\text{const } V_{DS}} = \frac{2 I_{DQ}}{V_{GST,0}}$$

$$I_D = \frac{4n}{2} C_{\text{ox}} \left(\frac{W}{L} \right) \left[V_{GST,Q}^2 \right]$$

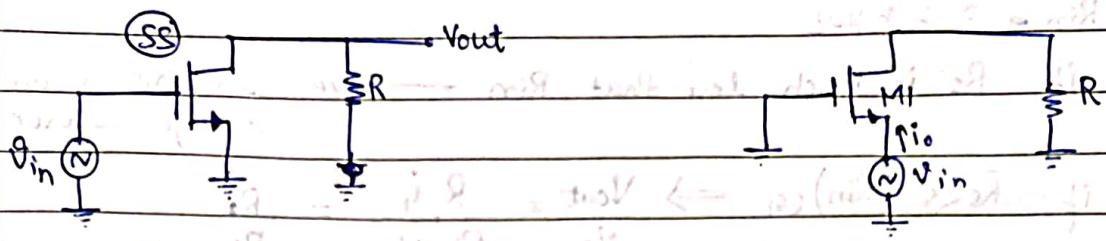CONFIGURATIONSCS Amplifier

$$R_{in} \rightarrow \infty$$

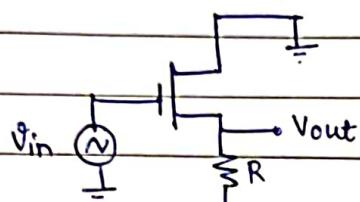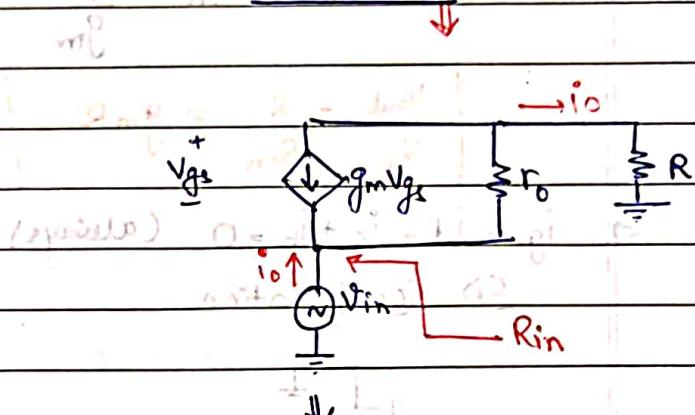CG config.CG₁ Amplifier

CG₁ MODE is NOT good as a Voltage amplifier.

attenuates
Voltage at
input itself


voltage at the
input drops, not
V_s anymore

r_o, R_s : resistive
division of
voltage

output resistance
of V_s

$$V_s = \left(\frac{R_{in}}{R_{in} + R_s} \right) V_s$$

$$N_s = R_{in} i_i$$

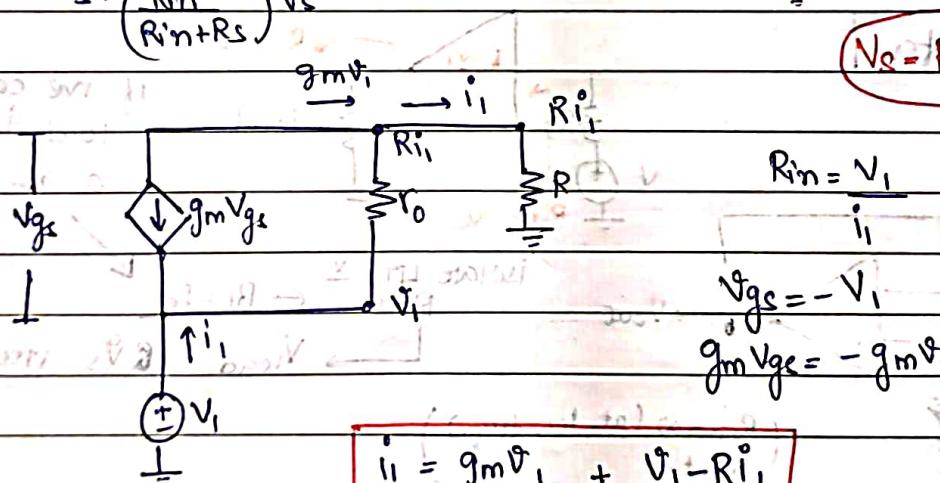

$$R_{in} = V_i / i_i$$

$$V_{g_s} = -V_i$$

$$g_m V_{g_s} = -g_m V_i$$

$$i_i = g_m V_i + V_i / R_o$$

$$R_o$$

$$\left(1 + \frac{R}{R_o} \right) i_i = \left(g_m + \frac{1}{R_o} \right) V_i$$

$$g_m \gg \frac{1}{R_o}$$

$$1/R_{in} = \left(\frac{V_i}{i_i} \right)^{-1} =$$

$$g_m + \frac{1}{R_o}$$

$$1/R_{in} = \frac{g_m + 1/R_o}{1 + R/R_o} = \frac{g_m}{1 + R/R_o}$$

$$Eg.: - g_m = 0.4 \text{ mA/V} \quad R = 10 \text{ k}\Omega \quad R_o = 200 \text{ k}\Omega$$

$$R/R_o \rightarrow 0 \quad 1/R_{in} = g_m \Rightarrow R_{in} = \frac{1}{g_m}$$

$$R_{in} \approx 2.5 k\Omega$$

if R_s is much less than R_{in} \rightarrow we can use it as a voltage source.


$$\text{if } R_s \ll (R_{in})_{CG} \Rightarrow V_{out} = \frac{R \cdot i_1}{V_s} = \frac{R}{R_{in}} \cdot i_1$$

$$\text{as } R_{in} \approx \frac{1}{g_m}$$

$$\boxed{\frac{V_{out}}{V_s} = \frac{R}{R_{in}} = g_m R}$$

$$\Rightarrow i_g + i_d + i_c + i_b = 0 \quad (\text{always})$$

CD Configuration

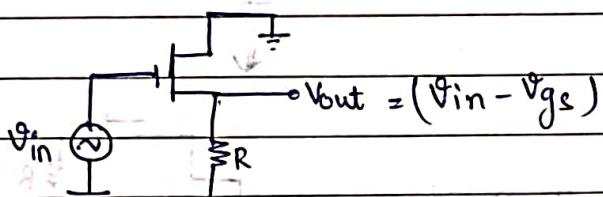


Source follower

V_{in} and V_{ge} have the same sign $\Rightarrow V_{in} - V_{ge} < V_i$

V_{out} can't be more than V_{in} \Rightarrow can't be used as a voltage amplifier.

Buffer

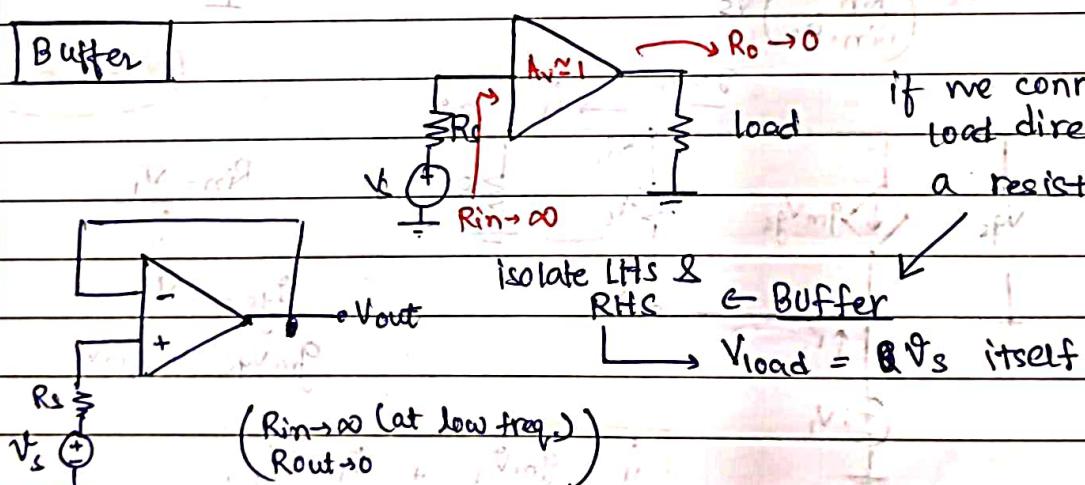

$$V_{out} = V_s \text{ (buffer)}$$

(CD Amplifier): $V_{in} > 0 \Rightarrow V_{ge} > 0$ and $V_{in} < 0 \Rightarrow V_{ge} < 0$

R_{out}

$A_v V_{in}$

load

R_{out}

(MOSFET is symmetric)
about D and S

Date _____
Page _____

Input resistance of CG \leftrightarrow Output resistance of CD

SAME

$(R_{out})_{CD} = \frac{1}{gm}$ we want $R_{out} \rightarrow 0$ as we want it to be a current follower.
so, ($gm \rightarrow$ as high as possible)

$\left| \frac{V_{GS}}{I_D} \right| = \text{constant}$ for constant V_{DS}

$$\frac{V_{GS}}{I_D} = (w/l)H \quad \frac{V_{GS}}{I_D} = (w/l)H$$

$$(\frac{V_{GS}}{I_D})_{\text{parallel}} = (\frac{V_{GS}}{I_D})_{\text{parallel}} = (\frac{V_{GS}}{I_D})_{\text{parallel}}$$

current source equivalent circuit

$(w/l)_{\text{parallel}} = \frac{V_{GS}}{I_D}$

$$(w/l)_{\text{parallel}} = \frac{V_{GS}}{I_D}$$

$$\frac{V_{GS}}{I_D} = (w/l)H \quad \frac{V_{GS}}{I_D} = (w/l)H$$

$$(\frac{V_{GS}}{I_D})_{\text{parallel}} + \cancel{\text{parallel}} = (\frac{V_{GS}}{I_D})_{\text{parallel}} = (w/l)H$$

$$(\frac{V_{GS}}{I_D})_{\text{parallel}}$$

dependence of w/l on I_D

$$I_D = (w/l)C_s V_D$$

current density J_D
 $J_D = w/l C_s V_D$

$$J_D = \frac{I_D}{l} = \frac{I_D}{l} (w/l) C_s V_D$$

$$J_D = \frac{I_D}{l} (w/l) C_s V_D \quad (J_D = \text{constant})$$