

Total Marks: 10**Submission Deadline: 11:59 p.m., 07-10-2023****Mode of submission: Scan your assignment and upload on Moodle as a single pdf file.**

Consider ideal op-amps for both questions.

Q1: The Circuit shown in Figure 1(a) uses a thermistor to indicate

- If temperature(T) is already below T_{MIN} or above T_{MAX} and
- will generate a falling edge or rising edge when temperature is going below T_{MIN} or going above T_{MAX} .

D_1 and D_2 are LEDs (light emitting diodes). R_{TH} is the resistance of the thermistor of which the thermal characteristic is expressed as $R_{TH}(T) = R_{TH}(T_0)e^{B(\frac{1}{T} - \frac{1}{T_0})}$, where T is absolute temperature in Kelvin (K). $T_0 = 298$ K (25°C), $R_{TH}(T_0) = 25\text{k}\Omega$, $B = 4000$ K.


- When the temperature rises above T_{MAX} then V_{IN} exceeds V_{TH} i.e. $V_{IN} > V_{TH}$ D_2 should turn on(emitting light).
- When the temperature falls below T_{MIN} and V_{IN} is lower than V_{TL} i.e. $V_{IN} < V_{TL}$ D_1 should turn on(emitting light).
- Op-Amp output saturates at $\pm 13\text{V}$.

Figure 1(b) shows the V_{OUT} vs V_{IN} hysteresis transfer characteristic for the circuit in Figure 1(a).

You will design the schmitt trigger as per following requirements

- (1) Choose R_1 and R_2 for your design according to limits: $1\text{k}\Omega \leq R_1, R_2 \leq 25\text{k}\Omega$.
- (2) $V_{TH} = 1.x$ and $V_{TL} = -1.x$, where x is last digit of your roll number.
- (3) LED D_1 has safe forward current between 1 mA and 5 mA and forward drop is 1V.
- (4) LED D_2 has safe forward current between 1 mA and 5 mA and forward drop is 2V.

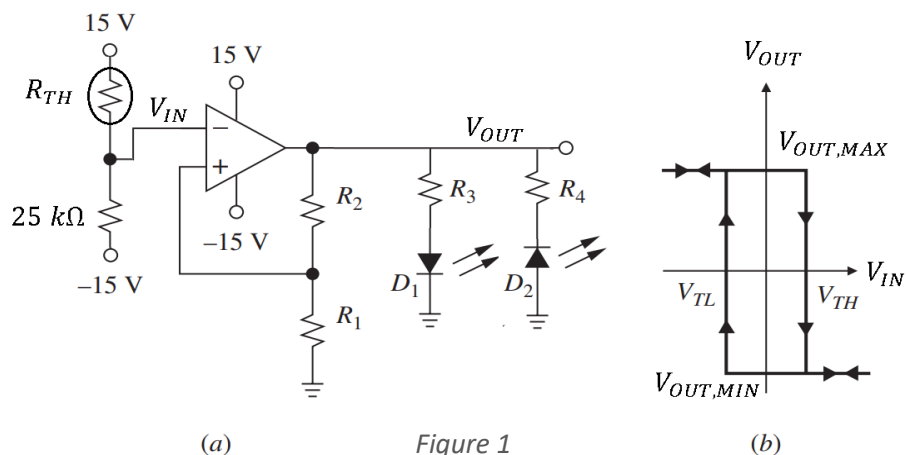- (a) Determine V_{TH} and V_{TL} for your roll number. [0.5 Marks]
- (b) Determine R_1 and R_2 for above V_{TH} and V_{TL} . [1.5 Marks]
- (c) Determine R_3 and R_4 as per instructions (3) and (4). [1.5 Marks]
- (d) Calculate T_{MAX} and T_{MIN} . [1.5 Marks]



Solution

1 a) Sample solution for roll number last digit '5'.

$$V_{TH} = 1.5 \text{ V} \quad \text{--- 0.25 Marks}$$

$$V_{TL} = -1.5 \text{ V} \quad \text{--- 0.25 Marks}$$

Students will choose based on their roll no.

$$b) \quad V_{TH} = \frac{13 R_1}{R_1 + R_2} \text{ V} \quad \text{--- ① --- 0.25 Marks}$$

$$V_{TL} = \frac{-13 R_1}{R_1 + R_2} \text{ V} \quad \text{--- ② --- 0.25 Marks}$$

from ①

$$1.5 = \frac{13 R_1}{R_1 + R_2}$$

$$1.5 R_1 + 1.5 R_2 = 13 R_1$$

$$1.5 R_2 = 11.5 R_1$$

Students can choose any value

$$\text{Let } R_1 = 1.5 \text{ k}\Omega \quad \text{--- 0.5 Marks}$$

$$R_2 = 11.5 \text{ k}\Omega \quad \text{--- 0.5 Marks}$$

c) for D_1 to pass safe current

$$1 \text{ mA} \leq \frac{12 - 1}{R_3} \leq 5 \text{ mA} \quad \text{--- 0.5 Marks}$$

$$1 \text{ mA} \leq \frac{12}{R_3} \leq 5 \text{ mA}$$

$$2.4 \text{ k}\Omega \leq R_3 \leq 12 \text{ k}\Omega \quad \text{--- 0.25 Marks}$$

for D_2 to pass safe current

$$1 \text{ mA} \leq \frac{-2 - (-13)}{R_4} < 5 \text{ mA} \quad \text{--- 0.5 Marks}$$

$$2.2 \text{ k}\Omega \leq R_4 < 11 \text{ k}\Omega \quad \text{--- 0.25 Marks}$$

4) Finding T_{\max} , As T increases R_{TH} decreases and V_{IN} increases, at $T=T_{\max}$, $V_{IN} = V_{TH}$

For $V_{TH} = 1.5V$

$$V_{TH} = 15 - \frac{30 R_{TH}}{25K + R_{TH}} \quad - 0.25 \text{ Marks}$$

Answer depends
on student
roll no.

$$1.5 = 15 - \frac{30 R_{TH}}{25K + R_{TH}}$$

$$R_{TH} = 20.45 K\Omega$$

$$20.45 K\Omega = 25K\Omega e^{4000\left(\frac{1}{T} - \frac{1}{298}\right)}$$

$$4000\left(\frac{1}{T} - \frac{1}{298}\right) = \ln \frac{20.45}{25}$$

$$T_{\max} = 302.52 K \quad - 0.5 \text{ Marks}$$

Finding T_{\min} , As T decreases R_{TH} increases and V_{IN} decreases, at $T=T_{\min}$, $V_{IN} = -V_{TH}$

For $V_{TH} = -1.5V$

$$V_{TH} = 15 - \frac{30 R_{TH}}{25K + R_{TH}}$$

$$-1.5 = 15 - \frac{30 R_{TH}}{25K + R_{TH}} \quad - 0.25 \text{ Marks}$$

$$R_{TH} = 30.55 K\Omega$$

$$30.55 K\Omega = 25K\Omega e^{4000\left(\frac{1}{T} - \frac{1}{298}\right)}$$

$$4000\left(\frac{1}{T} - \frac{1}{298}\right) = \ln \frac{25}{30.55}$$

$$T_{\min} = 293.6 K \quad - 0.5 \text{ Marks}$$

Q2: For the circuit shown in Figure 2(a), Op-Amps are dual supply Op-Amps and turn on voltages for D_1 and D_2 are equal to 0.7V .

- Derive an expression for V_{OUT} when $V_{IN} > 0$. [1 Marks]
- Derive an expression for V_{OUT} when $V_{IN} < 0$. [1 Marks]
- To achieve relation $V_{OUT} = A|V_{IN}|$, where A represents slope in Figure 2(b), what should be the relation between R_1 , R_2 and R_3 . [1 Marks]
- Consider condition for R_1, R_2, R_3 and R_4 as $1k\Omega \leq R_1, R_2, R_3, R_4 \leq 10k\Omega$, design the full wave rectifier for $A=3$. [2 Marks]


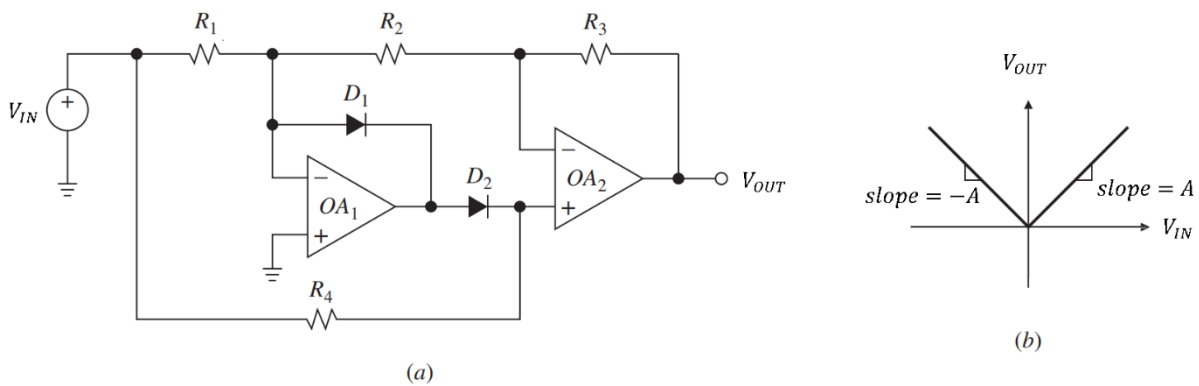


Figure 2

Solution

1 a) For $V_{IN} > 0$

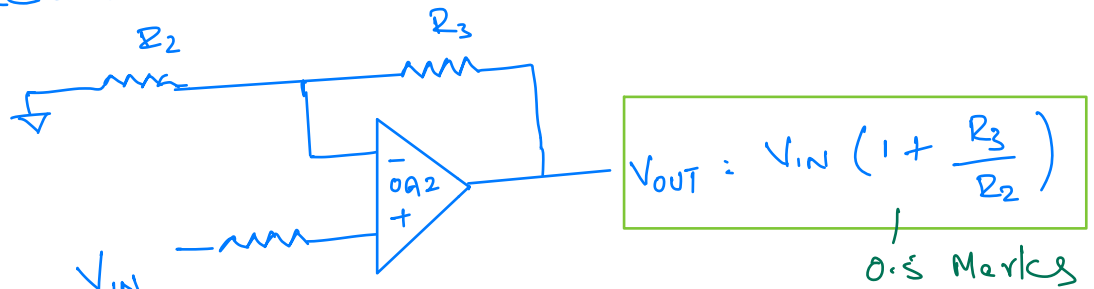D_1 turns ON and OA_1 is in negative feedback, D_2 is OFF — 0.5 Marks



b) For $V_{IN} < 0$

D_1 turns OFF and D_2 turns ON
 OA_1 is in -ve feedback through $D_2 - OA_2 - R_3 - R_2$ — 0.5 Marks

$$\frac{V_{IN} - 0}{R_1} = \frac{0 - V_{OUT}}{R_2 + R_3}$$

$$V_{OUT} = -\left(\frac{R_2 + R_3}{R_1}\right) V_{IN} \text{ — 0.5 Marks}$$

c) for $V_{out} = A V_{in}$

$$\left(1 + \frac{R_3}{R_2}\right) = \frac{R_2 + R_3}{R_1} \quad - 0.25 \text{ Marks}$$

$$\boxed{R_1 = R_2} \quad - 0.25 \text{ Marks}$$

$$1 + \frac{R_3}{R_2} = A$$

$$\boxed{R_3 = (A-1) R_2} \quad - 0.5 \text{ Marks}$$

d) for $A = 3$

Student can choose any value. let $R_1, R_2 = 3k\Omega$ — 1 Mark

$$R_3 = 6k\Omega \quad - 0.5 \text{ Marks}$$

R_4 has no constraint so R_4 can be anything — 0.25 Marks

$$\text{let } R_4 = 8k\Omega \quad - 0.25 \text{ Marks}$$