

EE204 Autumn 2023

Tutorial 10

Date 1 Nov 2023

Q1) Assume the 8-bit flash ADC, as shown in Fig. 1, has $V_{REF} = 2.560$ V.

(a) Find the total number of comparators, their voltage reference levels, and the maximum level tolerances allowed for a $\pm \frac{1}{2}$ LSB accuracy.

(b) Find $b_1 \dots b_8$ and the quantization error for $V_I = 0.5$ V, 1.054 V, and 2.543 V.

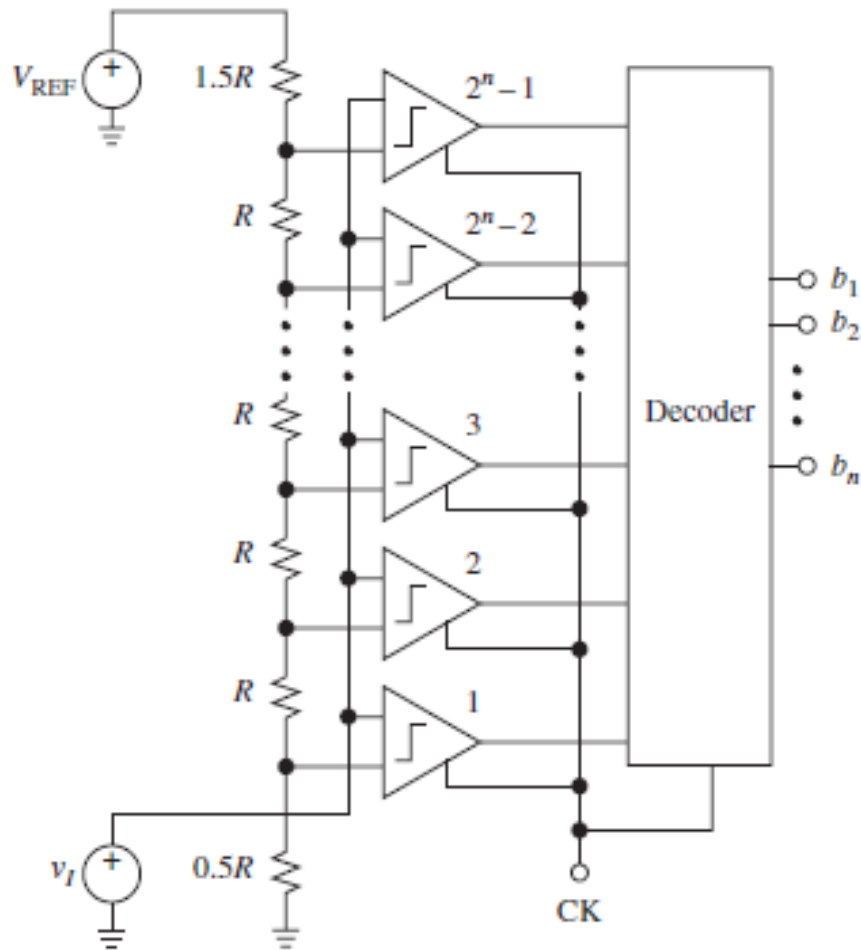


Figure 1

Q2) (a) Using a 0.5-nF capacitor C in the circuit of Fig. 2, find the value of R that results in an output pulse of 10- μ s duration. (b) If the 555 timer used in (a) is powered with $V_{CC} = 12$ V, and assuming that V_{TH} can be varied externally (i.e., it need not remain equal to $2/3 V_{CC}$), find its required value so that the pulse width is increased to 20 μ s, with other conditions the same as in (a).

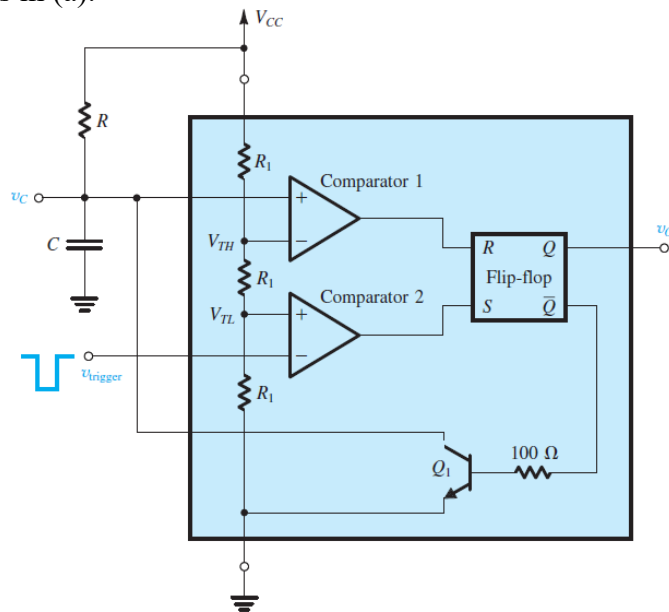


Figure 2

Q3) Using a 680-pF capacitor, design the astable circuit of Fig. 3 to obtain a square wave with a 20-kHz frequency and an 80% duty cycle. Specify the values of R_A and R_B .

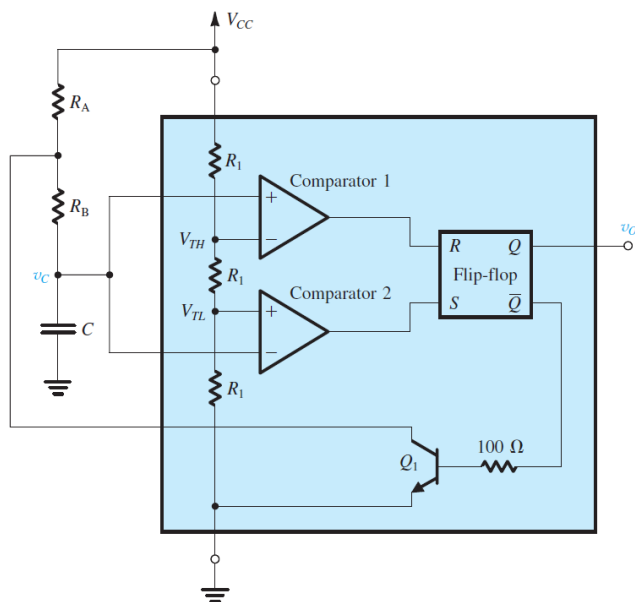


Figure 3

