

**Total Marks: 10****Submission Deadline: 11:59 p.m., 07-10-2023****Mode of submission: Scan your assignment and upload on Moodle as a single pdf file.**

Consider ideal op-amps for both questions.

**Q1:** The Circuit shown in Figure 1(a) uses a thermistor to indicate

- If temperature( $T$ ) is already below  $T_{MIN}$  or above  $T_{MAX}$  and
- will generate a falling edge or rising edge when temperature is going below  $T_{MIN}$  or going above  $T_{MAX}$ .

$D_1$  and  $D_2$  are LEDs (light emitting diodes).  $R_{TH}$  is the resistance of the thermistor of which the thermal characteristic is expressed as  $R_{TH}(T) = R_{TH}(T_0)e^{B(\frac{1}{T} - \frac{1}{T_0})}$ , where  $T$  is absolute temperature in Kelvin (K).  $T_0 = 298$  K ( $25^\circ\text{C}$ ),  $R_{TH}(T_0) = 25\text{k}\Omega$ ,  $B = 4000$  K.


- When the temperature rises above  $T_{MAX}$  then  $V_{IN}$  exceeds  $V_{TH}$  i.e.  $V_{IN} > V_{TH}$   $D_2$  should turn on(emitting light).
- When the temperature falls below  $T_{MIN}$  and  $V_{IN}$  is lower than  $V_{TL}$  i.e.  $V_{IN} < V_{TL}$   $D_1$  should turn on(emitting light).
- Op-Amp output saturates at  $\pm 13\text{V}$ .

Figure 1(b) shows the  $V_{OUT}$  vs  $V_{IN}$  hysteresis transfer characteristic for the circuit in Figure 1(a).

You will design the schmitt trigger as per following requirements

- (1) Choose  $R_1$  and  $R_2$  for your design according to limits:  $1\text{k}\Omega \leq R_1, R_2 \leq 25\text{k}\Omega$ .
- (2)  $V_{TH} = 1.x$  and  $V_{TL} = -1.x$ , where  $x$  is last digit of your roll number.
- (3) LED  $D_1$  has safe forward current between 1 mA and 5 mA and forward drop is 1V.
- (4) LED  $D_2$  has safe forward current between 1 mA and 5 mA and forward drop is 2V.

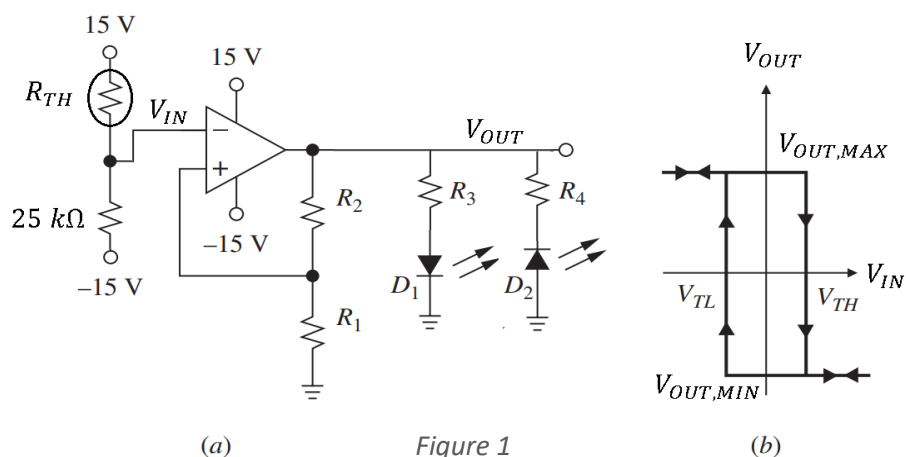- (a) Determine  $V_{TH}$  and  $V_{TL}$  for your roll number. [0.5 Marks]
- (b) Determine  $R_1$  and  $R_2$  for above  $V_{TH}$  and  $V_{TL}$ . [1.5 Marks]
- (c) Determine  $R_3$  and  $R_4$  as per instructions (3) and (4). [1.5 Marks]
- (d) Calculate  $T_{MAX}$  and  $T_{MIN}$ . [1.5 Marks]



**Q2:** For the circuit shown in Figure 2(a), Op-Amps are dual supply Op-Amps and turn on voltages for  $D_1$  and  $D_2$  are equal to 0.7V .

- Derive an expression for  $V_{OUT}$  when  $V_{IN} > 0$ . [1 Marks]
- Derive an expression for  $V_{OUT}$  when  $V_{IN} < 0$ . [1 Marks]
- To achieve relation  $V_{OUT} = A|V_{IN}|$ , where A represents slope in Figure 2(b), what should be the relation between  $R_1, R_2$  and  $R_3$ . [1 Marks]
- Consider condition for  $R_1, R_2, R_3$  and  $R_4$  as  $1k\Omega \leq R_1, R_2, R_3, R_4 \leq 10k\Omega$ , design the full wave rectifier for  $A=3$ . [2 Marks]

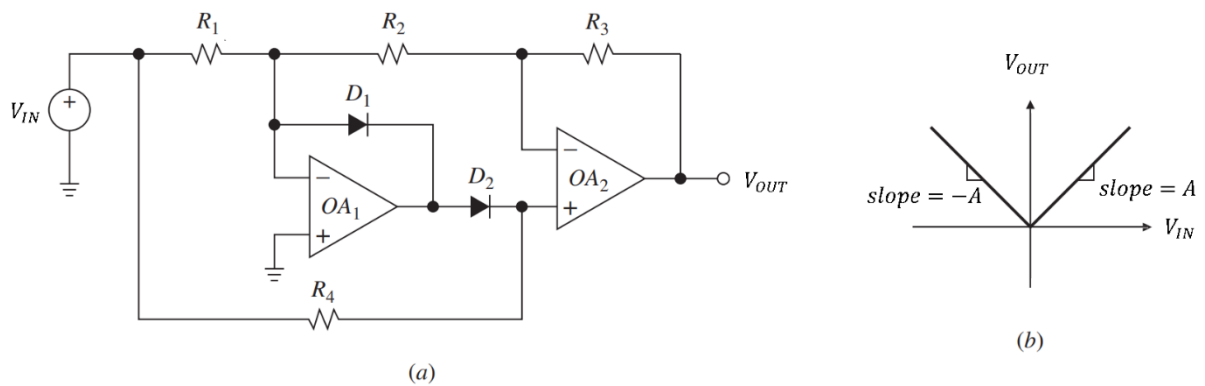


Figure 2