

EE204 : Analog Circuits
Dept of Electrical Engineering
IIT Bombay
Autumn Semester 2023

Assignment 1

Total Marks: 10

Submission Deadline: 11:59 p.m., 19-08-2023

Mode of Submission: Scan your assignment and upload on Moodle as a single pdf file.

1. For the circuit shown in Figure 1, use $A_v = 10^4$ for the OpAmp. Choose $10k\Omega < R_1 < 20k\Omega$, and $1k\Omega < R_2 < 5k\Omega$, such that the feedback factor $\beta = 0.1$.
 - (a) Calculate the $Gain = \frac{V_{out}}{V_{in}}$. [1 Mark]
 - (b) Calculate V_{out} for $V_{in} = 0.15V$. [1 Mark]
 - (c) Calculate the voltage at negative terminal of OpAmp for $V_{in} = 0.15V$. [1 Mark]

 


Figure 1: Circuit for Q1

2. For the circuit in Figure 2, use $W/L = 3\mu m/1\mu m$ for transistor M1. For M1 fabricated in 180nm CMOS technology, use $V_t = 0.4V$, and $\mu C_{ox} = 260\mu A/V^2$. Voltage limits for V_{GS} and V_{DS} are the following: $0 < V_{GS} < 1.8V$ and $0 < V_{DS} < 1.8V$.
- (a) Specify the range of V_{GS} and V_{DS} such that,
- (i) transistor M1 is in OFF region [0.5 Marks]
 - (ii) transistor M1 is in Ohmic region [0.5 Marks]
 - (iii) transistor M1 is in Saturation region [0.5 Marks]
- (b) Choose two values for V_{GS} and V_{DS} in Ohmic and Saturation regions of operation, calculate I_D and fill in the Table 1. [4 Marks]

Table 1

	Set1		Set2	
	$V_{GS}=...$		$V_{GS}=...$	
	V_{DS}	I_D	V_{DS}	I_D
Ohmic Region				
Saturation Region				

- (d) Sketch the plot of I_D vs. V_{DS} for all sets of V_{GS} . Mark the points calculated in Table 1 on the plot. [1.5 Marks]

 


Figure 2: Circuit for Q2