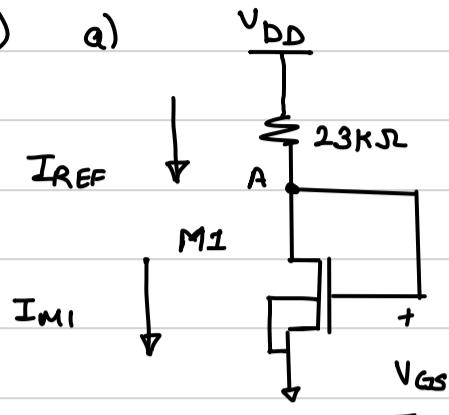


Assignment 2 Solution

Q1) a)



At point A,

$$I_{REF} = \frac{V_{DD} - V_{GS}}{23k\Omega} \quad - \textcircled{2} \quad (\text{0.5 marks})$$

$$I_{REF} = I_{M1} = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_t)^2$$

$$I_{M1} = I_{REF} = \frac{260\mu}{2} \times \left(\frac{W}{L}\right) [V_{GS} - V_t]^2 \quad - \textcircled{1} \quad (\text{0.5 marks})$$

$$\textcircled{1} = \textcircled{2}$$

$$\frac{1 - V_{GS}}{23k} = \frac{260\mu}{2} \left(\frac{W}{L}\right) (V_{GS} - 0.4)^2 \quad - \textcircled{3}$$

Solving equation $\textcircled{3}$, we get V_{GS} . two values of V_{GS} ,
(0.5 marks) for discarding a value that is $\leq V_t$

For example $\frac{W}{L} = \frac{4\mu\text{m}}{0.5\mu\text{m}}$

$V_{GS} = 0.622\text{V}$

b) $\lambda = 0.025\text{V}^{-1}$ for $L_2 = 1\mu\text{m}$

$$\frac{d\lambda}{dL} = -0.05 \text{ V}^{-1}/\mu\text{m}$$

For getting λ for $L_2 = 0.5\mu\text{m}$

$$\frac{0.025V^{-1} - \lambda}{1 - 0.5} = -0.05$$

$\lambda = 0.05 V^{-1}$ for length $L_2 = 0.5\mu m$

0.25 marks

case 1 : $L_2 = 1\mu m$

$$\frac{W_2}{L_2} = \frac{4\mu m}{0.5\mu m} = \frac{W_2}{1\mu m}$$

$$W_2 = 8\mu m$$

(i) For $V_{DS} < V_{GS} - V_t$

$$V_{DS} < 0.622 - 0.4$$

$$V_{DS} < 0.222 V$$

M₂ is in linear region

$$I_{out} = \frac{\mu_n C_{ox} W}{2L} \left(2(V_{GS} - V_t)V_{DS} - V_{DS}^2 \right)$$

0.25 marks

(ii) For $V_{DS} > V_{GS} - V_t$

$$V_{DS} > 0.222 V$$

M₂ is in saturation region

$$I_{out} = \frac{\mu_n C_{ox} W}{2L} \left(V_{GS} - V_t \right)^2 \left(1 + \lambda V_{DS} \right)$$

0.25 marks

$$\text{For } \begin{cases} V_{DS} = 0.18V \\ L = 1\mu\text{m} \end{cases} \quad I_{out} = 49.42 \mu\text{A}$$


$$V_{DS} = 0.5 \quad I_{out} = 51.89 \mu\text{A}$$

$$V_{DS} = 1V \quad I_{out} = 52.53 \mu\text{A}$$


$$\text{For } \begin{cases} V_{DS} = 0.18V \\ L = 0.5\mu\text{m} \end{cases} \quad I_{out} = 49.42 \mu\text{A}$$

$$V_{DS} = 0.5 \quad I_{out} = 52.53 \mu\text{A}$$
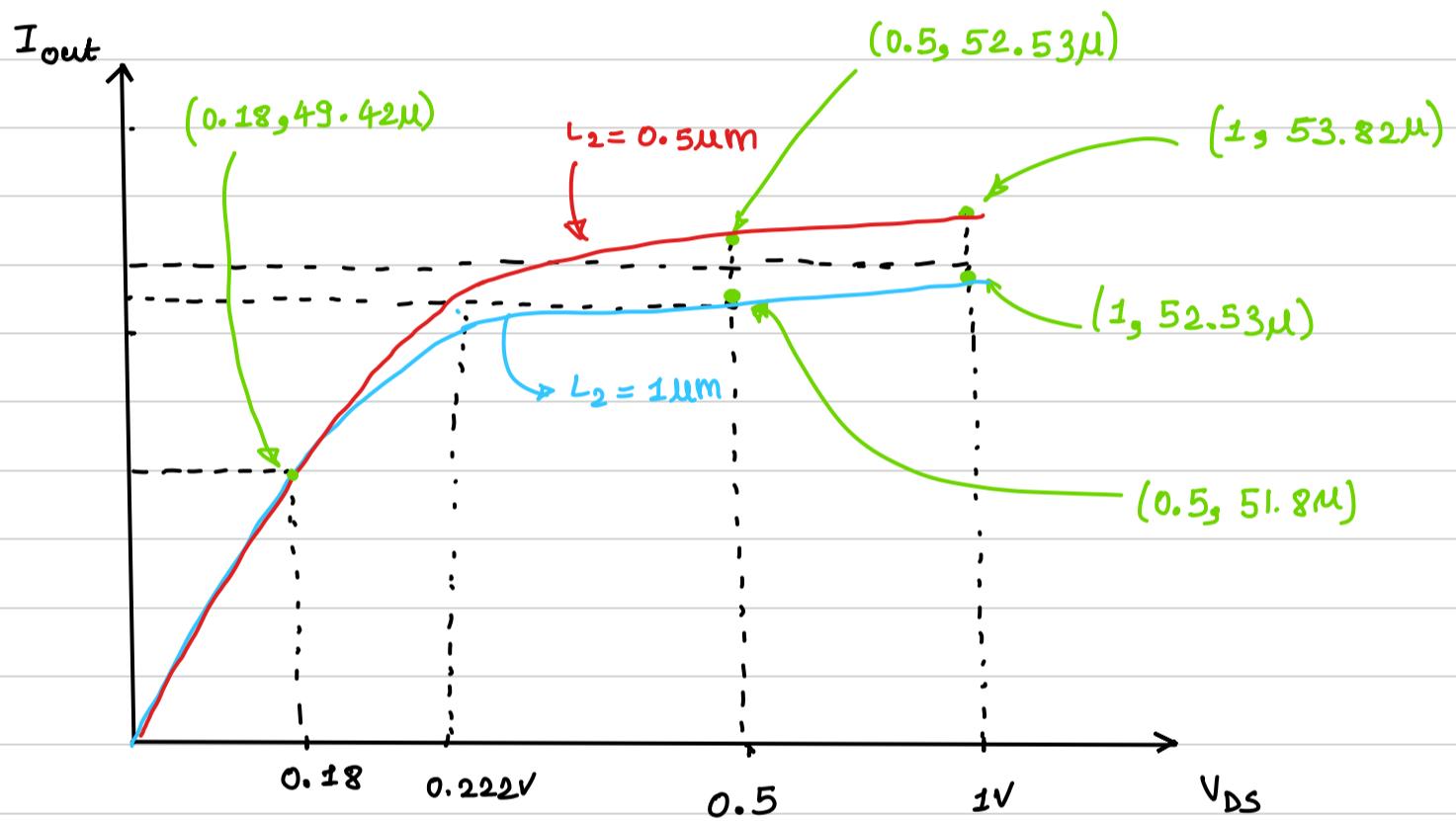
$$V_{DS} = 1V \quad I_{out} = 53.82 \mu\text{A}$$



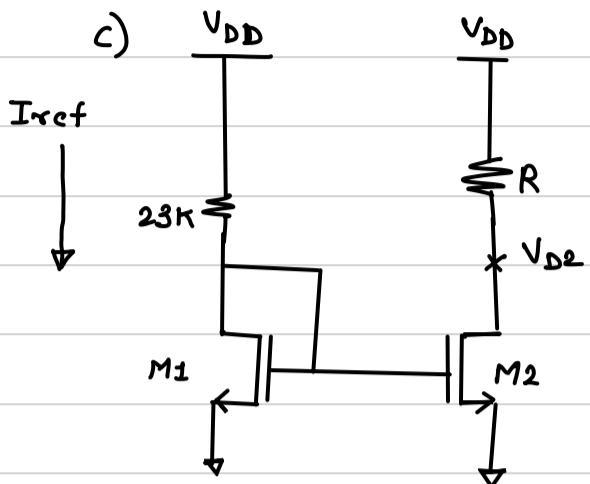- Take atleast 2 points in saturation and atleast 1 point in linear for both case - 0.5 marks
- 0.25 marks for plot .



$$I_{ref} = \frac{1.8 - V_{GS}}{23K}$$

$$= \frac{1.8 - 0.622}{23K}$$

$$= 51.21 \mu A$$

- 0.25 marks

case 1) $R = 20K$

Assuming M2 in saturation - 0.25 marks

$$V_{D2} = V_{DD} - I_{ref} R$$

$$= 1.8 - 51.21 \mu A \times (20K)$$

$$= 0.7758$$

since $V_{D2} > V_G - V_t$ - 0.25 marks

M2 is in saturation and $I_{out} = 51.21 \mu A$ -

0.25 marks 0.25 marks

case 2) $R = 40K$

Assuming M2 in saturation

$$V_{D2} = V_{DD} - I_{ref} R$$

$$= 1.8 - 51.21 \mu A \times 40K$$

$$= -0.248V$$

so our assumption is wrong
so M2 is in linear region

- 0.25 marks

$$I_{out} = \frac{V_{DD} - V_{DS}}{40K} \quad - \textcircled{1}$$

$$I_{out} = \frac{\mu_n C_{ox} W}{2L} \left(2(V_{GS} - V_t) V_{DS} - V_{DS}^2 \right) \quad - \textcircled{2}$$

$$\textcircled{1} = \textcircled{2}$$

$$\therefore \frac{V_{DD} - V_{DS}}{40K} = \frac{\mu_n C_{ox} W}{2L} \left(2(V_{GS} - V_t) V_{DS} - V_{DS}^2 \right) \quad - 0.25 \text{ marks}$$

$$\therefore 1.8 - V_{DS} = 41.6 \left(0.444 V_{DS} - V_{DS}^2 \right)$$

$$\therefore V_{DS} = 0.127$$


$$I_{out} = \frac{V_{DD} - V_{DS}}{40K}$$

$$= \frac{1.8 - 0.127}{40K}$$



$$= 41.825 \mu A$$

- 0.25 marks

Q2)

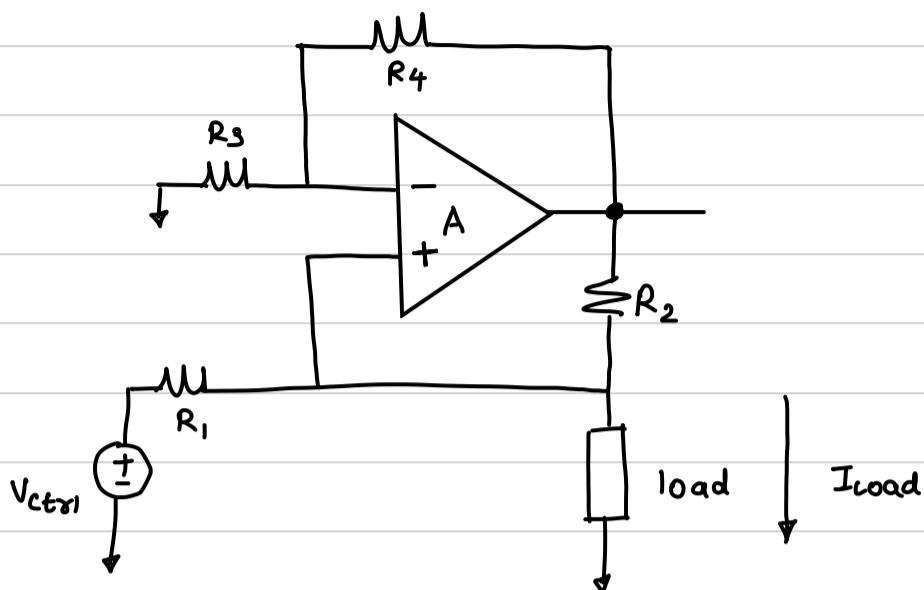

a)

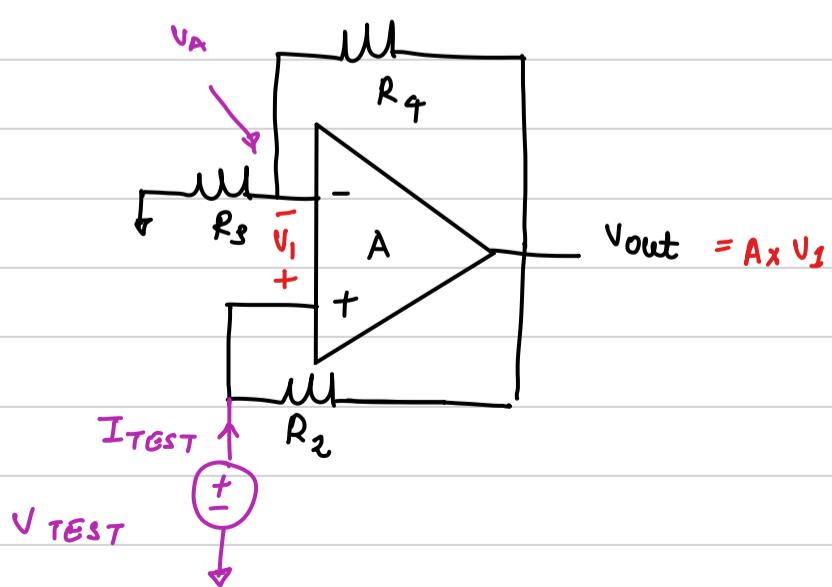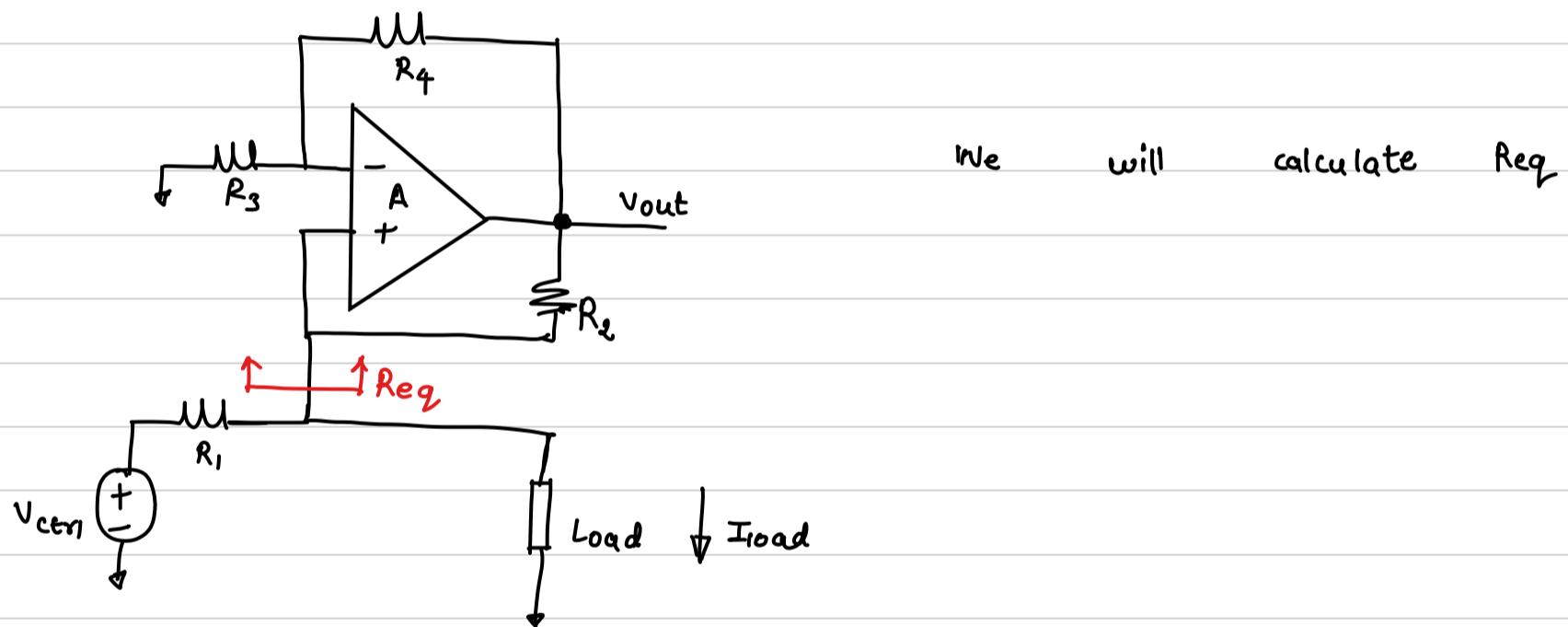

$$V_{out} = A \cdot V_1$$

0.25 marks

$$v_A = V_{out} \left(\frac{R_3}{R_3 + R_4} \right)$$

$$V_{out} = \left(1 + \frac{R_4}{R_3} \right) v_A$$

$$= \left(1 + \frac{R_4}{R_3} \right) (V_{TEST} - V_1) -$$

0.25 marks

$$\therefore AV_1 = \left(I + \frac{R_4}{R_3} \right) (V_{TEST} - V_1)$$

$$\therefore \left(A + \frac{R_4}{R_3} + 1 \right) V_1 = \left(1 + \frac{R_4}{R_3} \right) V_{TEST}$$

$$\therefore V_1 = \left(\frac{1 + R_4/R_3}{A + 1 + R_4/R_3} \right) V_{TEST}$$

$$I_{TEST} = \frac{V_{TEST} - AV_1}{R_2}$$

$$\therefore I_{TEST} = V_{TEST} - A \underbrace{\left(\frac{1 + \frac{R_4/R_3}{A+1+R_4/R_3}}{R_2} \right)}_{R_2} V_{TEST}$$

$$\therefore I_{TEST} = \frac{V_{TEST}}{R_2} \left(\frac{A+1 + \frac{R_4/R_3}{A+1+R_4/R_3} - A R_4/R_3 - A}{A+1 + \frac{R_4}{R_3}} \right)$$

$$= \frac{V_{TEST}}{R_2} \left(\frac{1 + (1-A) R_4/R_3}{1 + A + \frac{R_4}{R_3}} \right)$$

$$Req = R_2 \left(\frac{1 + A + R_4/R_3}{1 + (1-A) R_4/R_3} \right)$$

- 0.5 marks

$$Req = -R_1$$

- 0.25 marks

0.25 marks for calculating value of R_2

$$b) G_{out} = \frac{-R_4}{R_3} \times \frac{1}{R_2} + \frac{1}{R_1} = \frac{1}{R_1} \left(1 - \frac{R_4/R_3}{R_2/R_1} \right) \quad - 0.5 \text{ marks}$$

when no mismatch

$$R_4 \rightarrow R_{40}, R_3 \rightarrow R_{30} + \Delta R_3, R_2 \rightarrow R_{20} + \Delta R_2, R_1 \rightarrow R_{10}$$

also $\frac{R_{40}}{R_{30}} = \frac{R_{20}}{R_{10}}$ 0.25 marks

$$G_{out} = \frac{1}{R_1} \left(1 - \frac{\frac{R_{40}}{R_{30}} \times \frac{1}{z-a}}{\frac{R_{20}}{R_{10}} (1+b)} \right)$$

$$= \frac{1}{R_1} \left(1 - \frac{1}{(1-a)(1+b)} \right)$$

$$= \frac{1}{R_1} \left(1 - (1 - (b-a)) \right)$$

$$G_{out} = \frac{(b-a)}{R_1} \quad \text{0.5 marks}$$

$$R_{out} = \frac{R_1}{b-a}$$

$$b-a = \epsilon$$

$$0 - 0.05 < \epsilon < 0.04$$

- 0.5 marks

$$R_{out} = \frac{R_1}{\epsilon}$$

$$\epsilon = \frac{R_1}{R_{out}}$$

$$so, -0.05 < \frac{R_1}{R_{out}} < 0.04$$

$$so, -20 > \frac{R_{out}}{R_1}$$

and

$$R_{out} > 25R_1$$

0.25 marks

$$R_{out} < -20R_1$$



This is not possible because circuit may become unstable (0.25 marks)

so, worst case error occurs when

$$R_{out} = 25R_1$$

-0.25 marks

c) $I_{load} = \frac{V_{ctrl}}{R_1} \left(\frac{R_{out}}{R_{out} + R_L} \right)$

$$= \frac{V_{ctrl}}{R_1} \left(\frac{\frac{I}{I + \frac{R_L}{R_{out}}}}{R_{out}} \right)$$

- 0.5 marks

V_{ctrl} must be between V_{DD} and V_{SS} - 0.25 marks

0.25 marks for finding numerical value.