

---

**EE204: Analog Circuits****Dept of Electrical Engineering, IITB****Autumn Semester 2023**

---

**Assignment 6****Date: 29-10-2023**


---

**Total Marks: 10****Submission Deadline: 11:59 p.m., 05-11-2023****Mode of Submission: Scan your assignment and upload on Moodle as a single pdf file.**

---

**Q1:** Consider the 555 circuit of Figure 1. when the Threshold and the Trigger input terminals are joined together and connected to an input voltage  $V_{in}$ . Find the transfer characteristic  $V_{out}$  vs  $V_{in}$  with thresholds  $V_{TL} = \frac{1}{3} V_{CC}$  and  $V_{TH} = \frac{2}{3} V_{CC}$  and output levels of 0 and  $V_{CC}$ .

(2Marks)

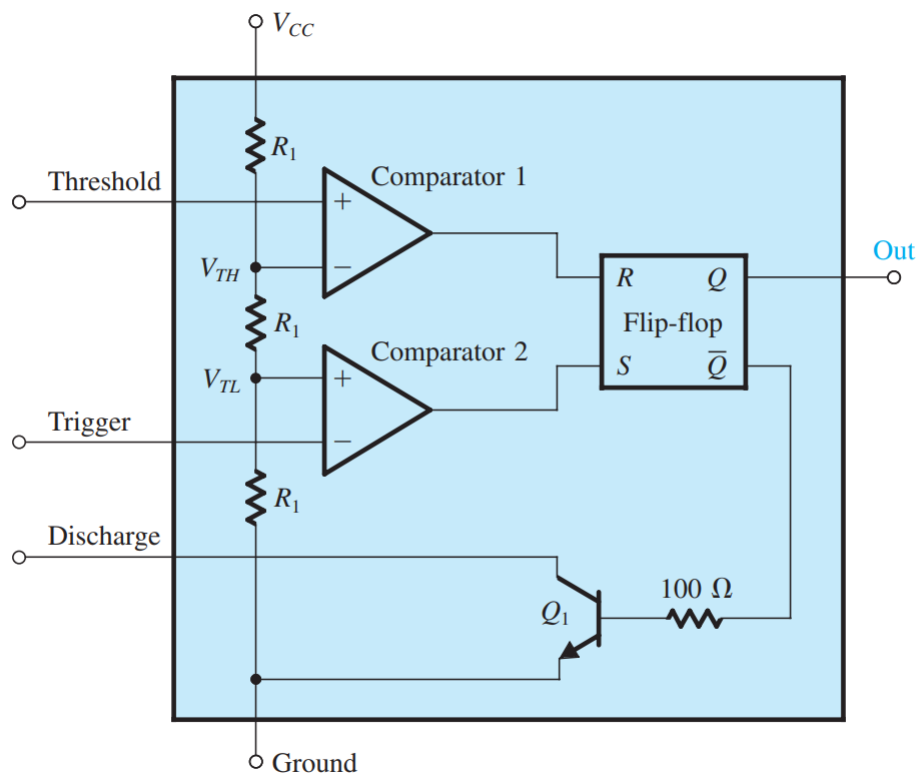
**Figure-1**

(a) Using a 0.5-nF capacitor C in the circuit of Fig. 2(a), find the value of R that results in an output pulse of 10- $\mu$ s duration. (1 Marks)




**Q3.**

**a.** A 4-bit flash ADC is shown in Figure 3.1(a). It is tested with a setup shown in Figure 3.2. The resulting reconstructed analog output is shown in Figure 3.1(b). Identify the problem and the most probable fault. (1 mark)

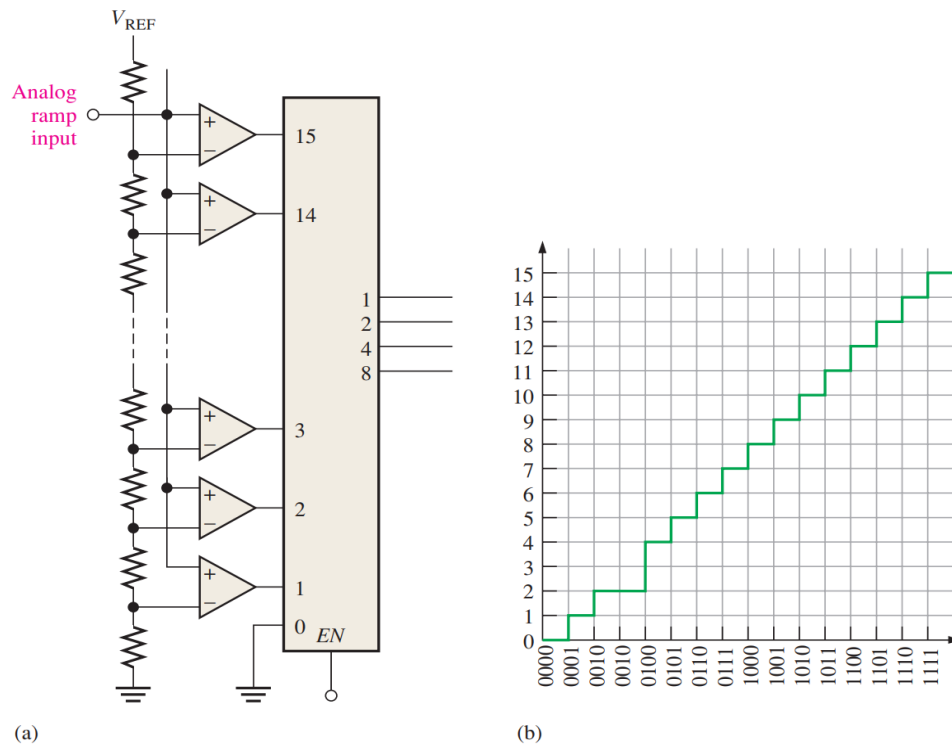

**Figure – 3.1**

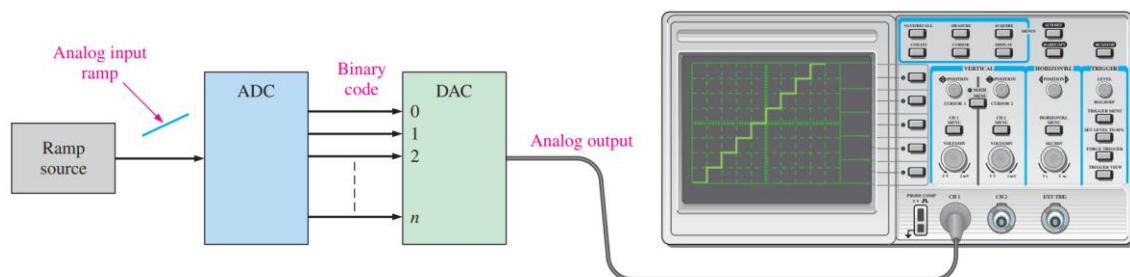

**Figure – 3.2**

**b.** A certain 8-bit ADC has a full-scale input of 2.55 V (i.e.,  $V_A = 2.55$  V produces a digital output of 11111111). It has a specified error of 0.1% F.S. Determine the maximum amount by which the output can differ from the analog input. (1 Marks)

**Q4.** The circuit shown in the Figure 4. works as a 2-bit analog to digital converter for  $0 \leq V_{in} \leq 3$  V .

Find the expression for

a) MSB output  $Y_1$  as a Boolean function of the inputs  $X_1, X_2, X_3$  (1.5 Marks)

b) LSB output  $Y_2$  as a Boolean function of the inputs  $X_1, X_2, X_3$ . (1.5 Marks)

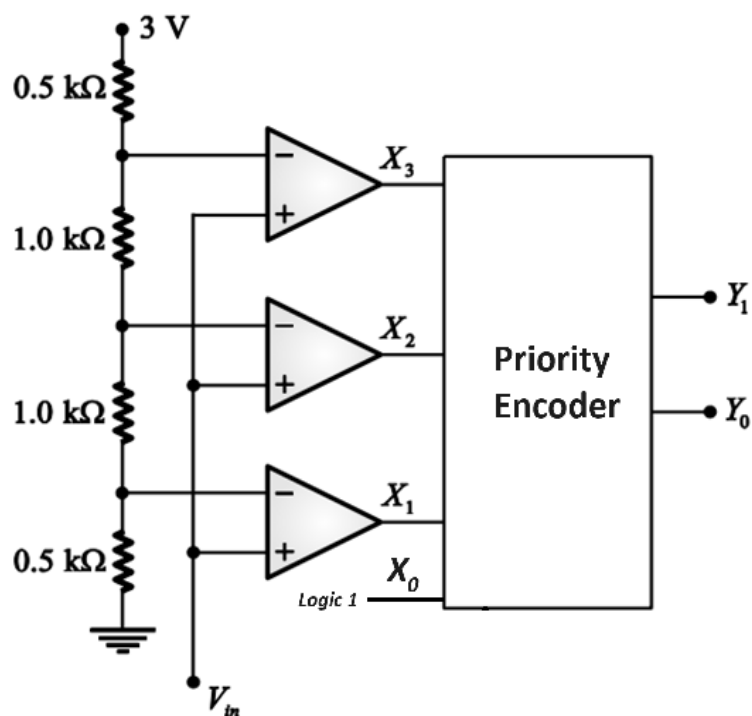


Figure 4