

Q1: For the circuit in Figure 1, transistor M₁ has W/L = 20um/1.8um. Use 180nm CMOS tech parameters: V_t = 0.4V, and $\mu C_{ox} = 260\mu A/V^2$.

- (a) For $V_1 = 0.80V$, calculate I_D and V_D .
- (b) Increase V_1 by 5mV, and recalculate I_D and V_D .
- (c) Calculate $(V_D(\text{part b}) - V_D(\text{part a})) / (V_1(\text{part b}) - V_1(\text{part a})) = \Delta V_D / \Delta V_1$. Is the absolute value of the ratio greater than 1?

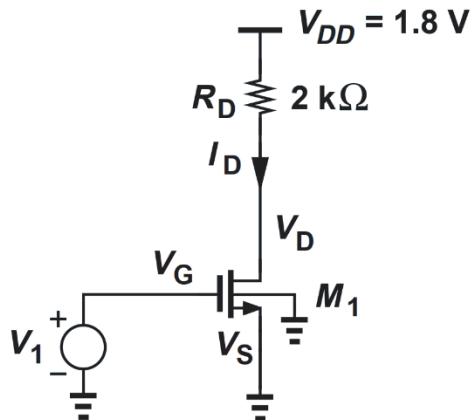


Figure 1

Q2: For the circuit in Figure 2, V_{DD} = 5V. Photodiode sensitivity is 0.5A/W (Ampere/Watt). Op-Amp output saturates at 3.5V high and 1.5V low.

- (a) If $R_1 = 1k\Omega$, what is the maximum intensity of light the circuit can sense?
- (b) If V_{out} can be measured with a resolution of 5mV, what is the minimum change in light intensity that can be detected?

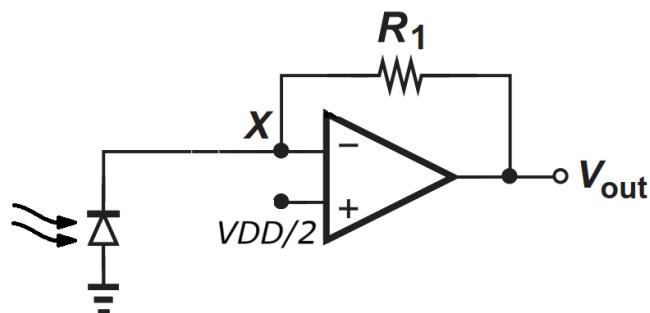


Figure 2

Q3: For the circuits in Figure 3, Op-Amps have finite open loop gain A_0 . Find expressions for $A_V = V_{out}/V_{in}$ in terms of R_1 , R_2 and open loop gain A_0 . Verify that they reduce to standard inverting and non-inverting gains when $A_0 \rightarrow \infty$.

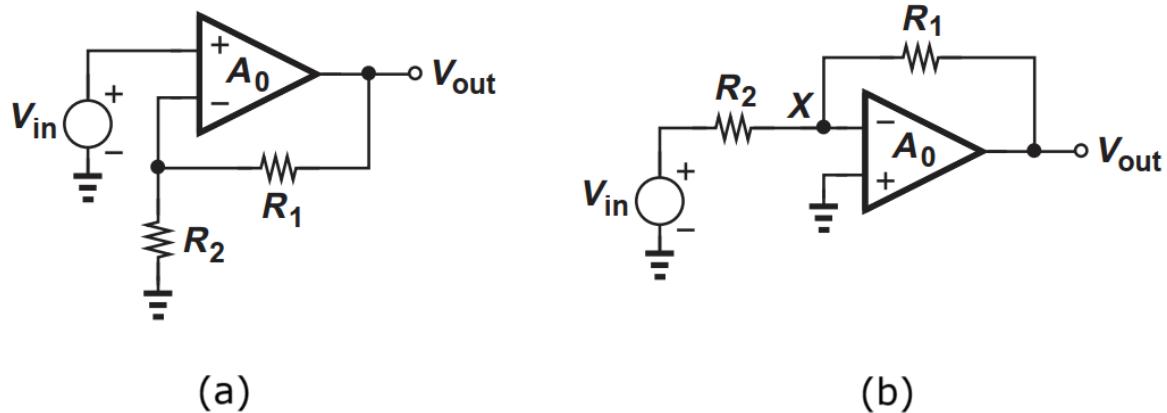


Figure 3

Q4: For the Howland Current Source in Figure 4, $VDD = 5V$, $VSS = 0V$ and $Vcntrl = 2V$. Op-Amp output saturates at 4V.

- (a) Find the values of R_1 , R_2 , R_3 , and R_4 such that $I_{OUT} = 1mA$ for $R_L = 2k\Omega$.
- (b) For the above design, what is the maximum value of R_L such that the Op-Amp does not saturate?

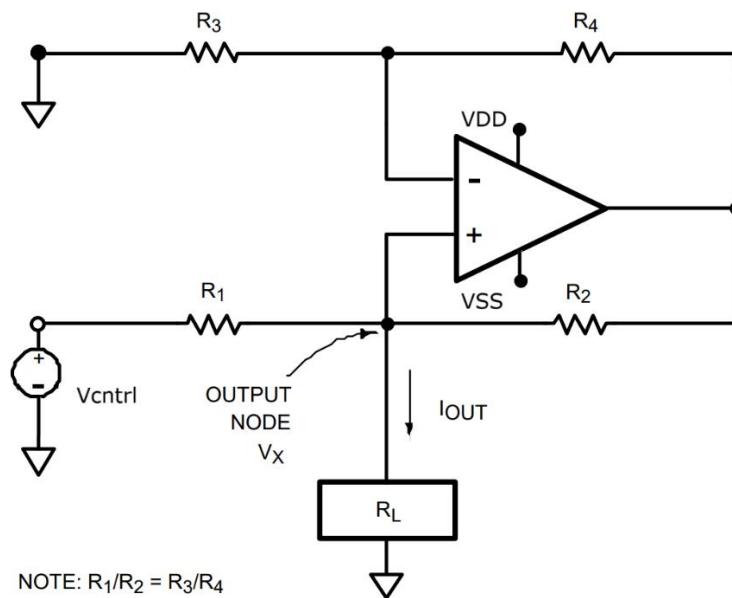


Figure 4

Q5: For the Modified Howland Current Source in Figure 5, $VDD = 5V$, $VSS = 0V$ and $Vcntrl = 2V$. Op-Amp output saturates at 4V.

- (a) Find the values of R_1 , R_2 , R_3 , R_4 , and R_5 such that $I_{OUT} = 1mA$ for $R_L = 2k\Omega$.
- (b) For the above design, what is the maximum value of R_L such that the Op-Amp does not saturate?


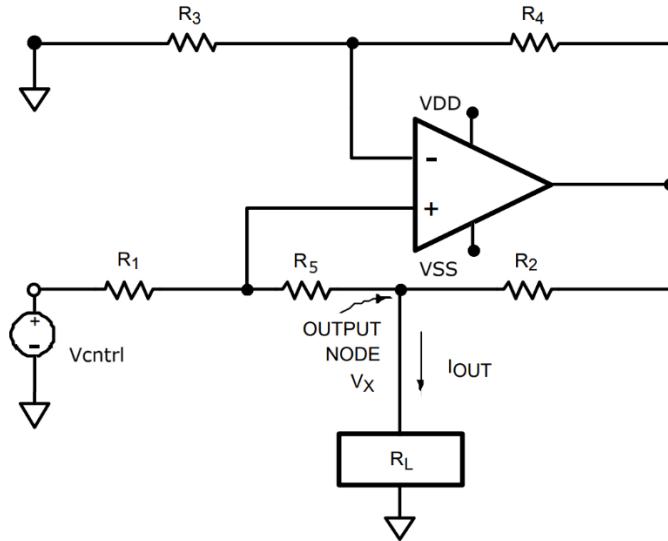


Figure 5

EE204 : Analog Circuits

Tutorial 3 Solutions

Q1 Q1: Solution

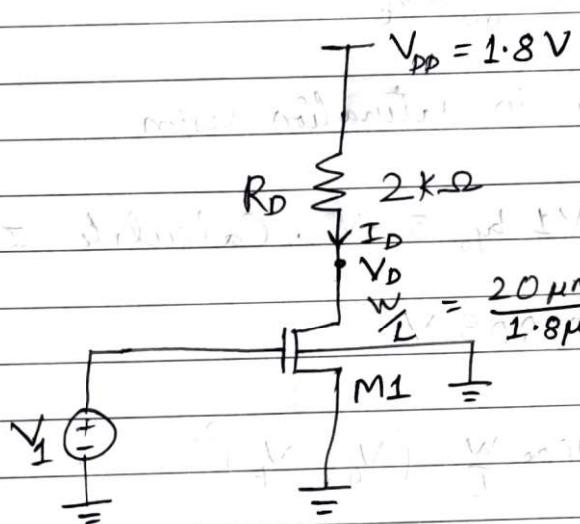

$$V_t = 0.4V, \mu C_{ox} = 260 \mu A/V^2.$$

(a) For $V_1 = 0.8V$, calculate I_D & V_D .

~~Assuming in saturation region for M1.~~

$$I_D = \frac{1}{2} \mu n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$V_{GS} = \frac{1}{2} \times 260 \times \frac{20}{1.8} (0.8 - 0.4)^2 \mu A$$

$$= 231.11 \mu A = 0.231 mA$$

$$V_D = V_{DD} - I_D R_D = 1.8 - 0.231 \times 2 = 1.338V$$

~~After reading the notes, I have understood the circuit~~

Let's verify our assumption of operation in saturation region for M1.

$$V_{DS} = 1.338 \text{ V}$$

$$V_{GS} - V_t = 0.8 - 0.4 = 0.4 \text{ V}$$

$$\therefore V_{DS} > V_{GS} - V_t$$

$\therefore M1$ is in saturation region

(b) Increase V_1 by 5 mV. Calculate I_D & V_D

$$V_1 = 0.805 \text{ V}$$

$$I_D = \frac{1}{2} \mu C_o x \frac{W}{L} (V_{GS} - V_t)^2$$

$$= \frac{1}{2} \times 260 \times \frac{20}{1.8} (0.805 - 0.4)^2 \mu\text{A}$$

$$= 236.9 \mu\text{A} \approx 0.237 \text{ mA}$$

$$V_D = V_{DD} - I_D R_D = 1.8 - 0.237 \times 2 = 1.326 \text{ V}$$

(c) Calculate $\frac{\Delta V_D}{\Delta V_1}$


$$\frac{\Delta V_D}{\Delta V_1} = \frac{1.326 - 1.338}{0.805 - 0.8} = \frac{-0.012 \text{ V}}{0.005 \text{ V}}$$

$$= \frac{-12 \text{ mV}}{5 \text{ mV}} = -2.4$$

Absolute value $\left| \frac{\Delta V_D}{\Delta V_1} \right| = |-2.4| = 2.4 > 1$


This is a rudimentary demo of transistor as amplifier

Q:2 Solution

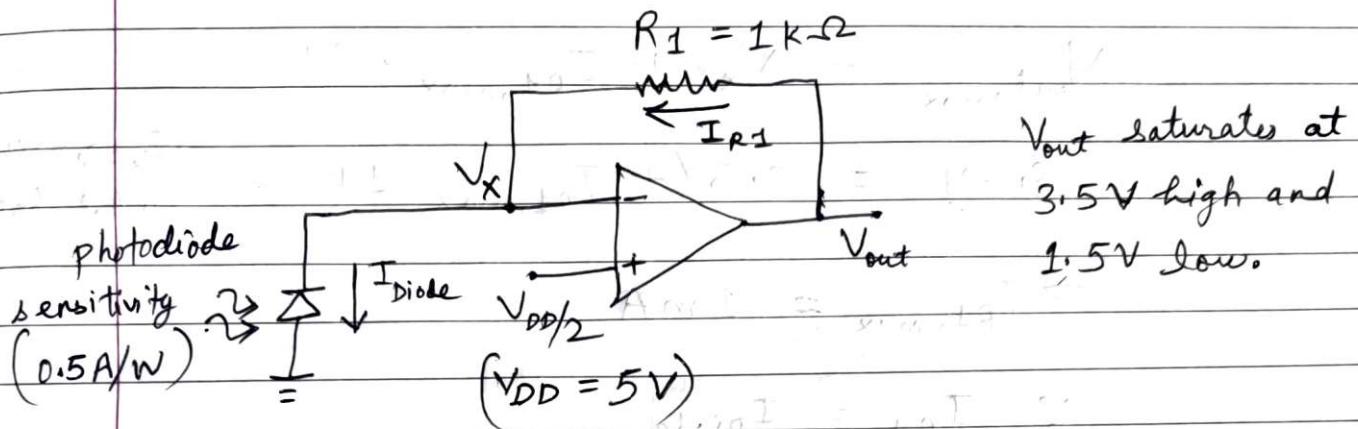

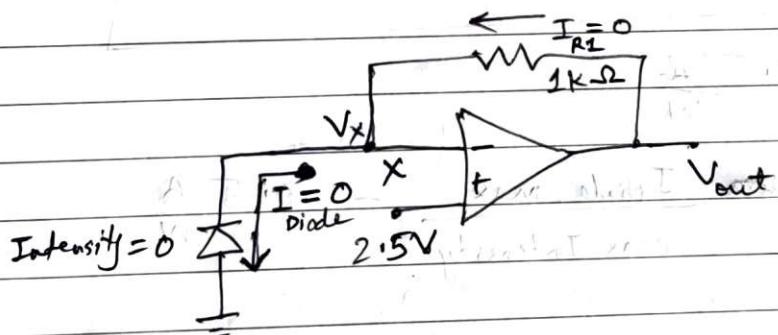(a) What is the max intensity of light the circuit can sense?

Solution: When intensity = 0, photodiode current = 0.



By virtual short $V_x = 2.5\text{ V}$

$$V_{\text{out}} = V_x + I_{R1} \cdot R_1$$

$$= 2.5 + 0$$

$$V_{\text{out}} = 2.5\text{ V}$$

For a photodiode $I_{\text{diode}} \propto \text{Intensity of light}$

Max intensity ~~sets~~ corresponds to max current without opamp saturation.

Opamp saturates at 3.5V. Therefore

$$V_{out, max} = V_x + I_{R1, max} \cdot R_1$$

$$3.5V = 2.5V + I_{R1, max} \cdot 1k\Omega$$

$V_x = 2.5V$ by
Virtual short

$$\Rightarrow I_{R1, max} = 1mA$$

$$\therefore I_{R1} = I_{diode}$$

$$\therefore I_{diode, max} = I_{R1, max} = 1mA$$

$$\text{Photodiode Sensitivity} = \frac{I_{diode}}{\text{Incident light Intensity}}$$

$$\therefore \frac{I_{diode, max}}{\text{max Intensity}} = 0.5 \frac{A}{W}$$

$$\text{Max Intensity} = \frac{I_{diode max}}{0.5 A/W}$$

$$\text{Max Intensity} = 2mW$$

Therefore, maximum intensity of light the circuit can sense before op-amp output going to saturation is 2mW.

~~Solution~~

(b) If V_{out} can be measured with a resolution of 5mV , what is the minimum change in light intensity that can be detected?

Sol'n :

$$\Delta V_{out, \min} = 5\text{mV}$$

[min. V_{out} change
that can be measured]

$$V_{out} = V_x + I_{R1} \cdot R_1$$

$$V_{out} = V_x + I_{diode} \cdot R_1$$

[$\because I_{R1} = I_{diode}$]

$$V_{out} = V_x + \text{Light Intensity} \times \text{Sensitivity} \cdot R_1$$

Let Light Intensity = P_{light}

& Sensitivity = S

$$V_{out} = V_x + P_{light} \cdot S \cdot R_1$$

$$\Delta V_{out} = \Delta P_{light} \cdot S \cdot R_1$$

$\left. \begin{array}{l} (\because V_x = 2.5\text{V} \\ \text{constant}) \\ S \& R_1 \text{ are} \\ \text{constant} \end{array} \right\}$


~~Therefore,~~
Minimum change in light Intensity that can be detected

$$\Delta P_{light, \min} = \frac{\Delta V_{out, \min}}{S \cdot R_1} = \frac{5\text{mV}}{0.5\text{A} \cdot 1\text{k}\Omega}$$

$$\Delta P_{light, \min} = 10\text{ }\mu\text{W}$$


Q3: Solution

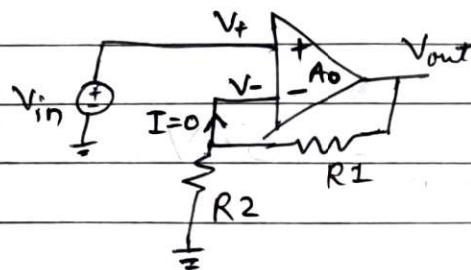(a) Express, $A_v = \frac{V_{out}}{V_{in}}$ in terms of R_1, R_2 & A_o for following circuit.



~~(By virtual short)~~

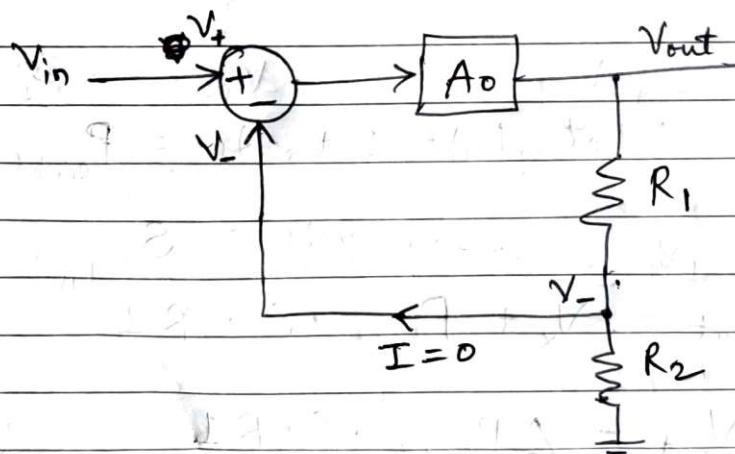~~Solution:~~ Redrawing the above circuit as below.



$$V_- = \frac{V_{out} \cdot R_2}{R_1 + R_2}$$

[Using voltage division]

$$(V_+ - V_-) A_o = V_{out}$$

$$V_+ - \left(V_{in} - \frac{V_{out} R_2}{R_1 + R_2} \right) A_o = V_{out}$$

[After substituting for
V₊ and V₋]

$$\frac{V_{in} A_o - V_{out} R_2 A_o}{R_1 + R_2} = V_{out}$$

$$V_{out} \left[1 + \frac{R_2 A_o}{R_1 + R_2} \right] = V_{in} A_o$$

$$\frac{V_{out}}{V_{in}} = \frac{A_o}{1 + \frac{R_2 A_o}{R_1 + R_2}}$$


Let $\frac{R_2}{R_1 + R_2} = \beta$ (feedback factor)

$$A_v = \frac{V_{out}}{V_{in}} = \frac{A_o}{1 + \beta A_o}$$


if $A_o \rightarrow \infty$, $\beta A_o \gg 1$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{A_o}{\beta A_o} = \frac{1}{\beta} = \frac{R_1 + R_2}{R_2} = 1 + \frac{R_1}{R_2}$$

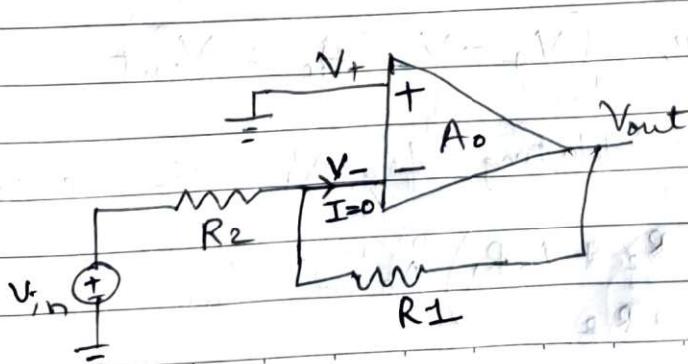(b) Express $A_v = V_{out}/V_{in}$, in terms of R_1 , R_2 & A_o for following circuit



Redrawing the above circuit as below

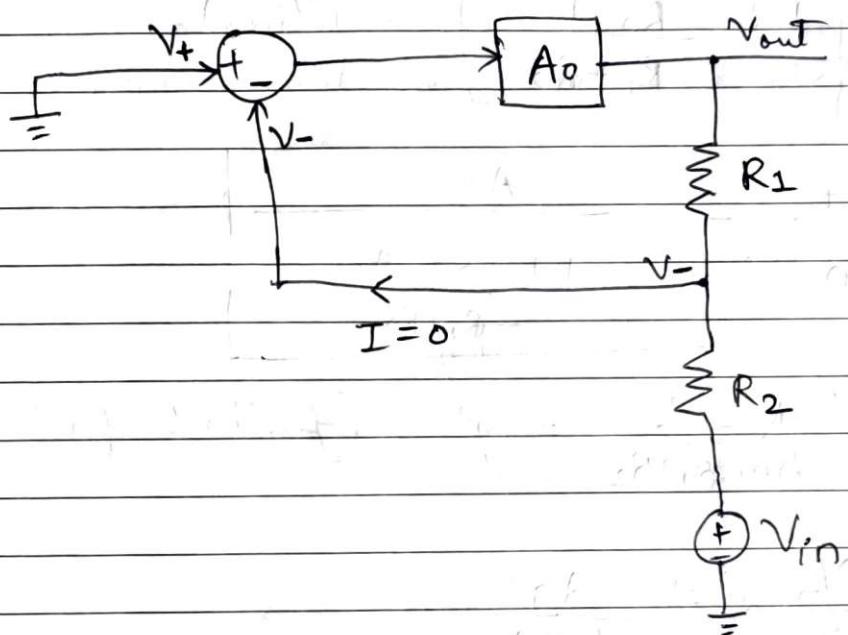

Equating Currents through R_1 & R_2

$$\frac{V_{out} - V_-}{R_1} = \frac{V_- - V_{in}}{R_2}$$

$$V_{out} R_2 - V_- \cdot R_2 = V_- \cdot R_1 - V_{in} R_1$$

$$V_{out} R_2 + V_{in} R_1 = V_- \cdot R_1 + V_- \cdot R_2$$

$$V_- = \frac{V_{out} R_2 + V_{in} R_1}{R_1 + R_2}$$

Now, $(V_+ - V_-)A_o = V_{out}$

Substituting for V_+ & V_- we get

$$0 - \left(\frac{V_{out} R_2 + V_{in} R_1}{R_1 + R_2} \right) A_o = V_{out}$$

$$V_{out} \left(1 + \frac{R_2 A_o}{R_1 + R_2}\right) = -\frac{V_{in} R_1 A_o}{R_1 + R_2}$$


$$A_v = \frac{V_{out}}{V_{in}} = \frac{-\left(\frac{R_1 A_o}{R_1 + R_2}\right)}{\left(\frac{R_1 + R_2 + R_2 A_o}{R_1 + R_2}\right)}$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{-R_1 A_o}{R_1 + R_2 + R_2 A_o}$$

If $A_o \rightarrow \infty \Rightarrow R_2 A_o \gg R_1 \& R_2$

$$\therefore A_v = \frac{V_{out}}{V_{in}} = \frac{-R_1 A_o}{R_2 A_o} = -\frac{R_1}{R_2}$$

Q4: Solution

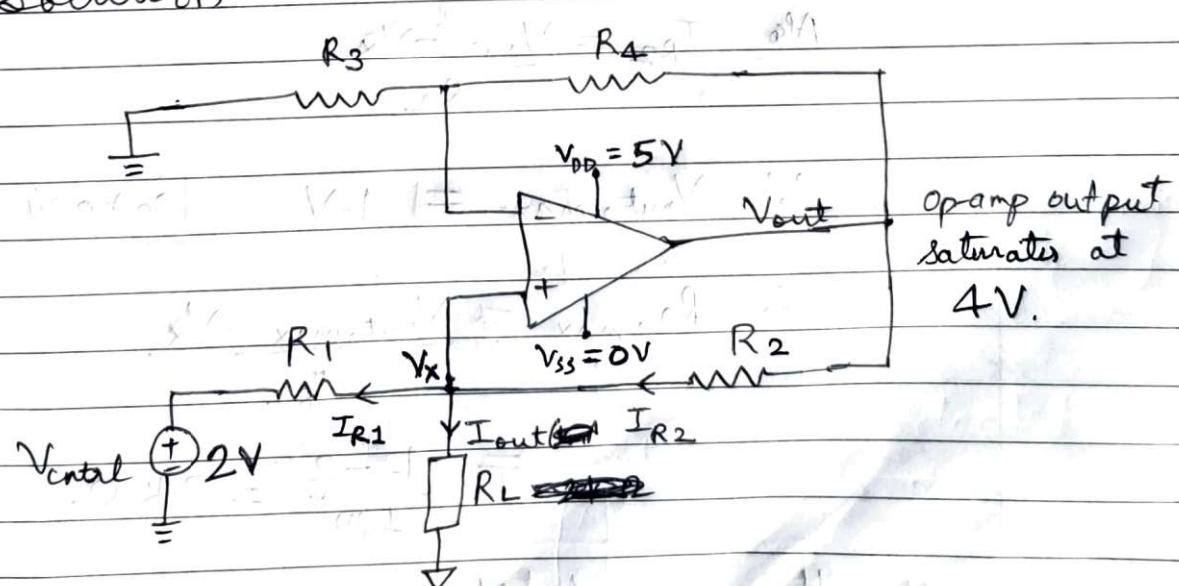

(a) $I_{out} = 1 \text{ mA}$, $R_L = 2 \text{ k}\Omega$

Design the circuit and choose R_1, R_2, R_3 and R_4 for required $I_{out} = 1 \text{ mA}$ and given $R_L = 2 \text{ k}\Omega$.
Opamp should ~~not~~ be not saturated.

Ø

Solution :-

$$I_{out} = \frac{V_{ctrl}}{R_1}$$

$$\Rightarrow R_1 = \frac{V_{ctrl}}{I_{out}} = \frac{2 \text{ V}}{1 \text{ mA}} = 2 \text{ k}\Omega$$

$$V_x = I_{out} R_L = 1 \text{ mA} \cdot 2 \text{ k}\Omega = 2 \text{ V}$$

$$I_{R1} = \frac{V_x - V_{ctrl}}{R_1} = \frac{2 - 2}{R_1} = 0$$

$$\therefore I_{R2} = I_{R1} + I_{out} = 1 \text{ mA}$$

$$\text{Also } I_{R2} = \frac{V_{out} - V_x}{R_2}$$

$$\therefore V_{out, max} = 4 \text{ V}$$

[OpAmp o/p saturates at 4 V]

$$\therefore R_{2, max} = \frac{V_{out, max} - V_x}{I_{R2}}$$

$$= \frac{4 - 2}{1 \text{ m}} = 2 \text{ k}\Omega$$

Hence, we should choose $R_2 < 2 \text{ k}\Omega$

Let us choose $R_2 = 1.5 \text{ k}\Omega$

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$


[Howland current source requirement]

~~$\frac{2 \text{ k}}{1.5 \text{ k}} = \frac{R_3}{R_4}$~~

Let us choose $R_3 = 2 \text{ k}\Omega$ and $R_4 = 1.5 \text{ k}\Omega$


So, now our design is
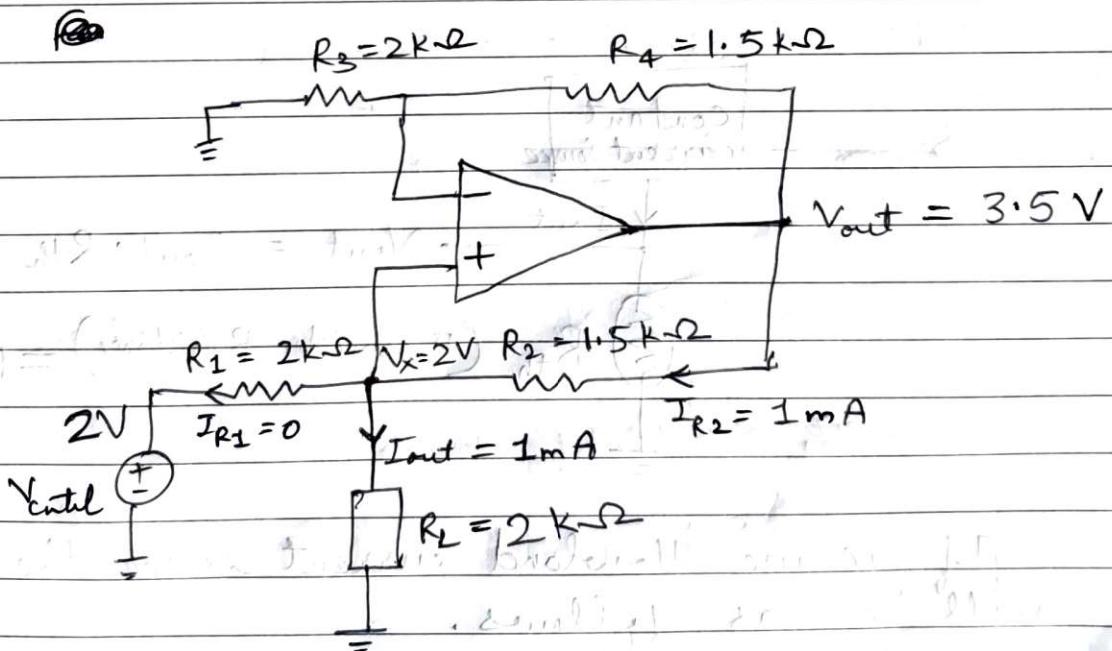
$$R_1 = 2 \text{ k}\Omega, R_2 = 1.5 \text{ k}\Omega, R_3 = 2 \text{ k}\Omega, R_4 = 1.5 \text{ k}\Omega$$



For our design $V_{out} = 3.5 \text{ V}$ (\because Op-Amp is not saturated and we have 0.5 V margin before op-amp saturates.)

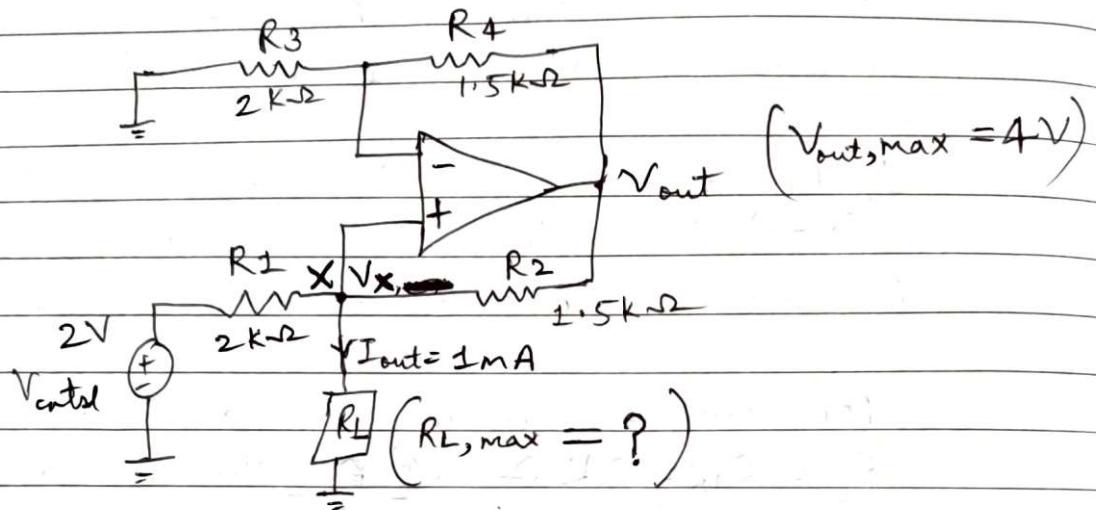(b) For the design in part (a), what is the maximum value of R_L such that op-amp output does not saturate? [opamp o/p is at the verge of saturation]



Writing KCL at node X.

$$\frac{V_x - V_{ctrl}}{R_1} + I_{out} = \frac{V_{out} - V_x}{R_2}$$

putting $V_x = I_{out} R_L$ we get

$$\frac{I_{out} \cdot R_L - V_{ctrl}}{R_1} + I_{out} = \frac{V_{out} - I_{out} \cdot R_L}{R_2}$$

when, $V_{out} = V_{out, \max} \Rightarrow R_L = R_{L, \max}$

$$\frac{I_{out} \cdot R_{L, \max} - V_{ctrl}}{R_1} + I_{out} = \frac{V_{out, \max} - I_{out} \cdot R_{L, \max}}{R_2}$$

Substituting $I_{out} = 1mA$, $V_{out1} = 2V$, $R_1 = 2k\Omega$,
 $R_2 = 1.5k\Omega$, ~~$V_{out, max}$~~ $= 4V$, we get,

$$\frac{1mA \cdot R_{L,max} - 2}{2k\Omega} + 1mA = \frac{4 - 1mA \cdot R_{L,max}}{1.5k\Omega}$$

$$\frac{1m \cdot R_{L,max} - 2 + 1mA \cdot 2K}{2K} = \frac{4 - 1m \cdot R_{L,max}}{1.5K}$$

$$\frac{1m \cdot R_{L,max} - 2 + 2}{2} = \frac{4 - 1m \cdot R_{L,max}}{1.5}$$

$$1.5(1m \cdot R_{L,max}) = 8 - 2m \cdot R_{L,max}$$

$$3.5m \cdot R_{L,max} = 8$$

$$R_{L,max} = \frac{8}{3.5m}$$

$$R_{L,max} = 2.286 k\Omega$$

**

Supplementary Material for Q4


For the design in part (a) ~~if we increase~~ if R_L (load resistance) is increased the opAmp output voltage V_{out} will increase.

~~B~~ R_L may increase if load is variable.


One example is R_L may be sensitive to temperature and hence may change.

Let us understand through an example.

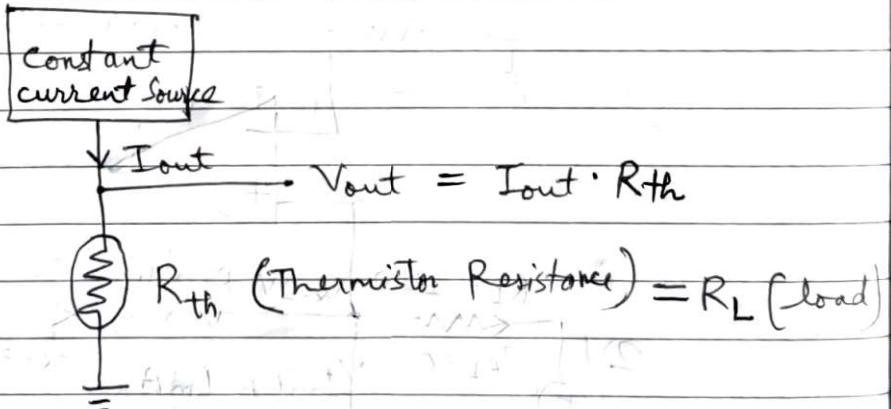We want to make a temperature sensor. ~~thermistor~~. We can pass a constant current through it and sense the voltage across thermistor.



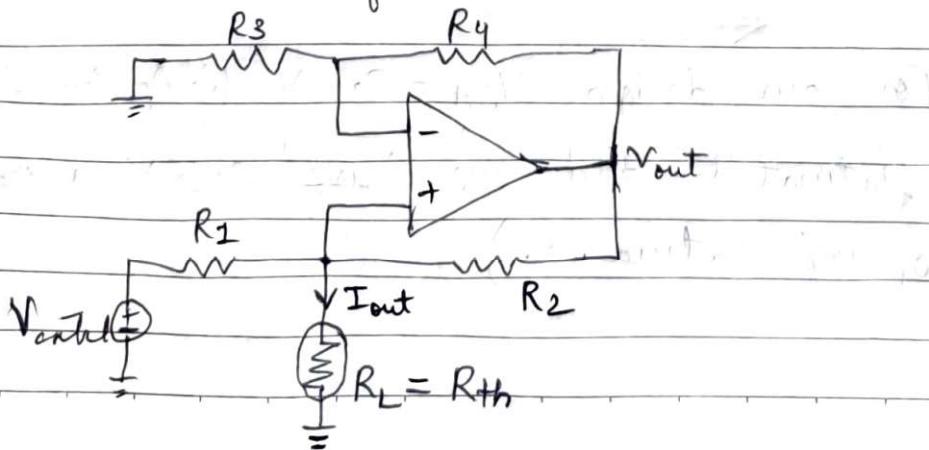If we use Howland current source the circuit will be as follows.



In part (a) we designed for $I_{out} = 1\text{mA}$ and $R_L = R_{th} = 2\text{k}\Omega$.

Let us say ~~$R_L = R_{th} = 2\text{k}\Omega$~~ corresponds to thermistor resistance at 25°C.


If we are using a Negative Temperature Coefficient (NTC) thermistor, the resistance, R_{th} , will increase when temperature reduces.

For our design in part (a) $V_{out} = 3.5\text{V}$ for $R_L = R_{th} = 2\text{k}\Omega$. [This is for our design choices of $R_1 = 2\text{k}\Omega$, $R_2 = 1.5\text{k}\Omega$, $R_3 = 2\text{k}\Omega$ & $R_4 = 1.5\text{k}\Omega$]

Now, ~~for now~~ in part (b) we find maximum R_L (i.e., how much R_L can be increased before op-Amp saturates). This, $R_{Lmax} = 2.286\text{k}\Omega$.

In our thermistor example, this corresponds to the maximum R_{th} value, that is the minimum temperature value (remember we are using negative coefficient thermistor) that can be sensed before op-Amp output saturates.

Q5: Solution

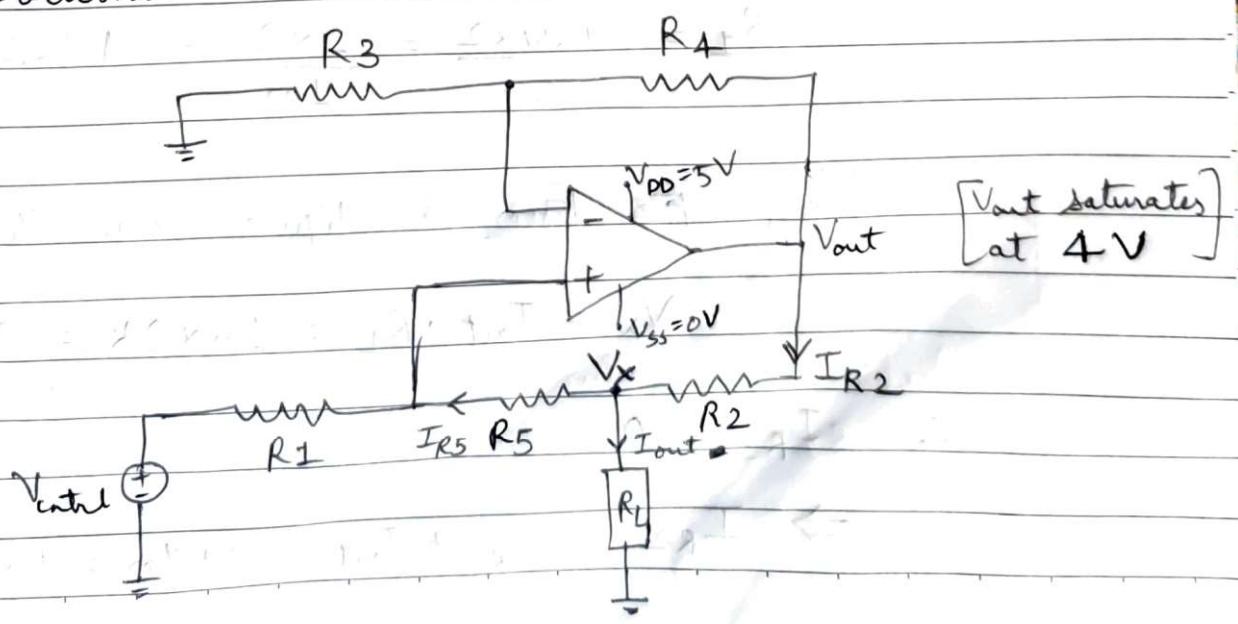

(a) $I_{out} = 1 \text{ mA}$, $R_L = 2 \text{ k}\Omega$.

Design the circuit and choose, R_1, R_2, R_3, R_4 and R_5 appropriately for $I_{out} = 1 \text{ mA}$ and $R_L = 2 \text{ k}\Omega$.
~~Opamp~~ Opamp should not be saturated output.

$$I_{out} = \frac{V_{control}}{R_1} \times \left(\frac{R_2 + R_5}{R_2} \right)$$

Design
Equations

$\underbrace{\qquad}_{\text{also known as}} \qquad \underbrace{\qquad}_{\text{Gain Factor}}$

$$\frac{R_4}{R_3} = \frac{R_2 + R_5}{R_1}$$

Let us choose the following,

$$\text{Gain factor} = \frac{R_2 + R_5}{R_2} = 2$$

$$\Rightarrow R_2 = R_5$$

Now,

$$\therefore I_{out} = \frac{V_{control} \times 2}{R_1}$$

$$R_1 = \frac{V_{control} \times 2}{I_{out}} = \frac{2 \times 2}{1 \text{ m}} = 4 \text{ k}\Omega$$

~~From the figure, using Ohm's Law.~~

$$V_x = I_{out} \cdot R_L = 1 \text{ m} \times 2 \text{ k} = 2 \text{ V}$$

$$\therefore I_{R5} = 0$$

$$\Rightarrow I_{R2} = I_{R5} + I_{out} = 0 + 1 \text{ m} = 1 \text{ mA}$$

$$\text{Now, } V_{\text{out}} = V_x + I_{R2} \cdot R_2$$

$$\Rightarrow R_{2,\text{max}} = \frac{V_{\text{out,max}} - V_x}{I_{R2}}$$

$V_{\text{out,max}} = 4 \text{ V}$
as opamp o/p saturates at 4 V

$$= \frac{4 - 2}{1 \text{ mA}} = 2 \text{ k}\Omega$$


∴ we choose $R_2 < 2 \text{ k}\Omega$.

Let us choose $R_2 = 1.5 \text{ k}\Omega$.

$$\Rightarrow R_5 = R_2 = 1.5 \text{ k}\Omega$$


$$\text{Now, } \frac{R_4}{R_3} = \frac{R_2 + R_5}{R_1} = \frac{1.5 + 1.5}{4} = \frac{3}{4}$$

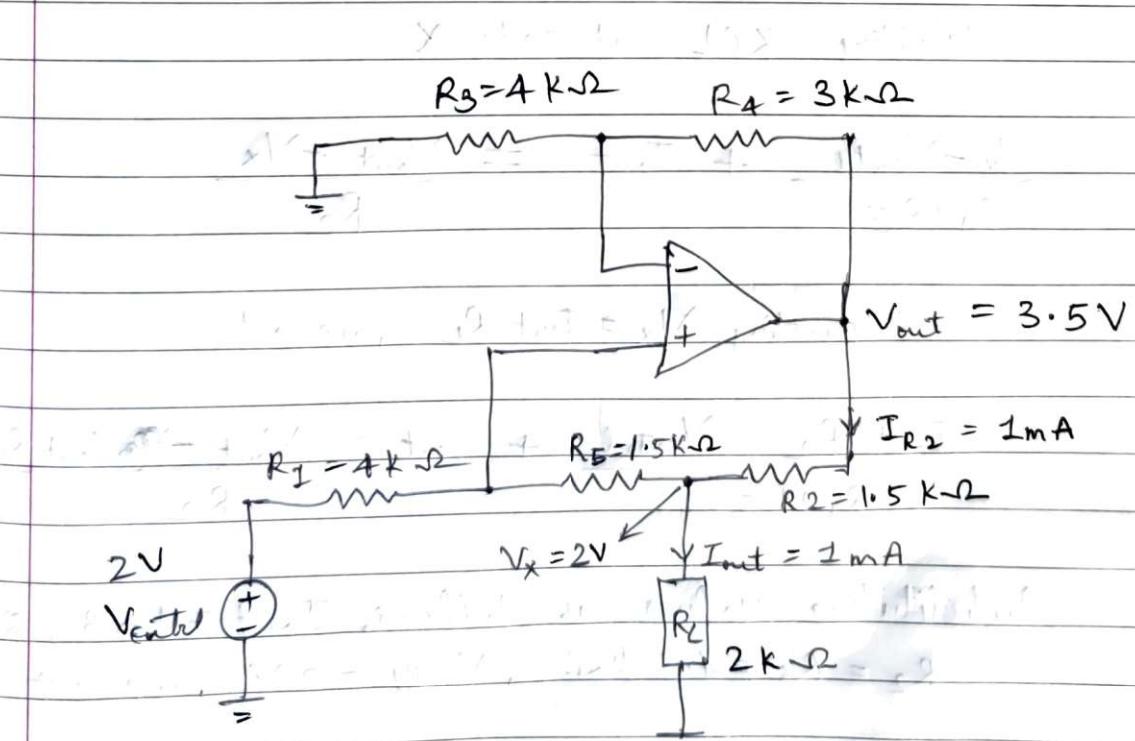Let us choose $R_4 = 3 \text{ k}\Omega$, $R_3 = 4 \text{ k}\Omega$
So, now our designed circuit is as below.



For our design $V_{\text{out}} = 3.5 \text{ V}$ (opamp is not saturated)
and we have 0.5 V margin before opamp saturates)

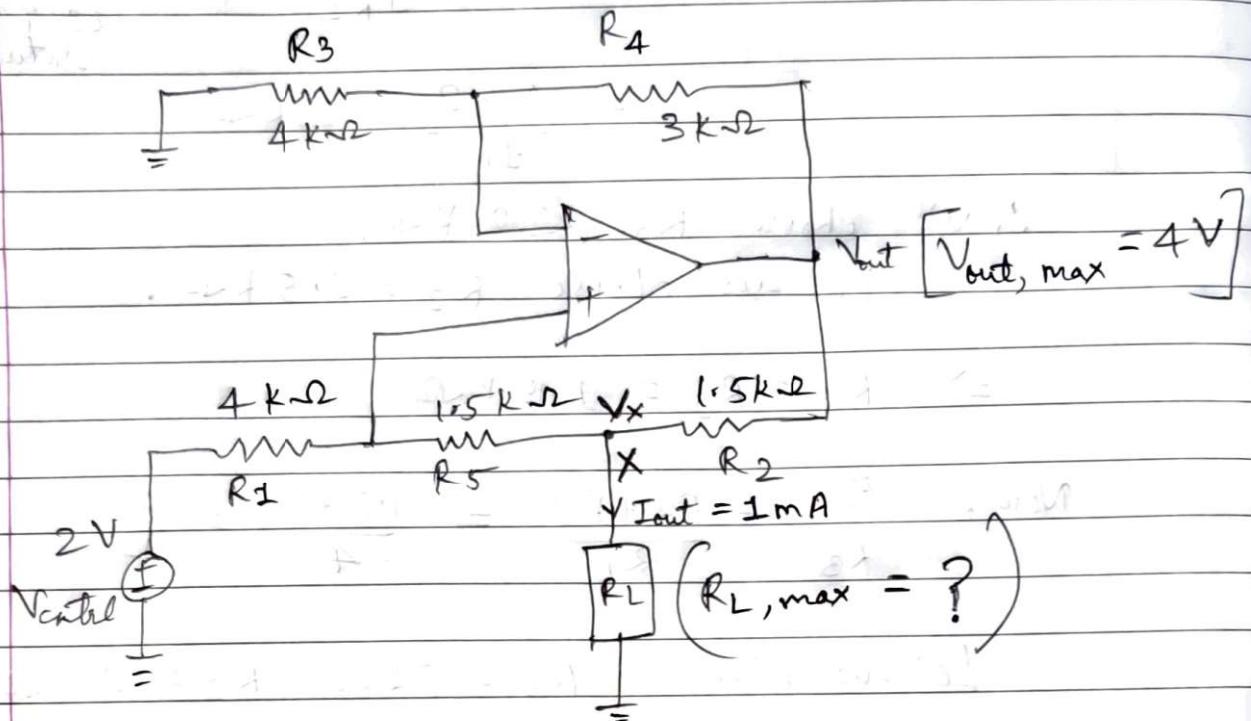(b) For the design in part (a), what is the maximum value of R_L such that op-amp is at verge of saturation?



Writing KCL at node X

$$\frac{V_x - V_{cathode}}{R_1 + R_5} + I_{out} = \frac{V_{out} - V_x}{R_2}$$

putting $V_x = I_{out} R_L$, we get

$$\frac{I_{out} R_L - V_{cathode}}{R_1 + R_5} + I_{out} = \frac{V_{out} - I_{out} \cdot R_L}{R_2}$$

Substituting values as follows. $I_{out} = 1mA$, $R_1 = 4k\Omega$

$R_2 = R_5 = 1.5k\Omega$, $V_{cathode} = 2V$, we get

$$\frac{1\text{mA} \cdot R_L - 2}{4\text{k}\Omega + 1.5\text{k}\Omega} + 1\text{mA} = \frac{V_{out} - 1\text{mA} \cdot R_L}{1.5\text{k}\Omega}$$

$$\frac{1\text{mA} \cdot R_L - 2 + 5.5}{5.5} = \frac{V_{out} - 1\text{mA} \cdot R_L}{1.5}$$

when, $V_{out} = V_{out, max} \Rightarrow R_L = R_{L,max}$

$$\frac{1\text{mA} \cdot R_{L,max} - 2 + 5.5}{5.5} = \frac{V_{out,max} - 1\text{mA} \cdot R_L}{1.5}$$

put $V_{out,max} = 4\text{V}$. & simplify.

$$1.5(1\text{mA} \cdot R_{L,max} + 3.5) = 5.5(4 - 1\text{mA} \cdot R_{L,max})$$

$$(1.5 + 5.5)\text{mA} \cdot R_{L,max} = 5.5 \times 4 - 1.5 \times 3.5$$

$$7\text{mA} \cdot R_{L,max} = 16.75$$

$$R_{L,max} = \frac{16.75}{7\text{mA}}$$

$$= \frac{16.75}{7} \text{k}\Omega$$

$$R_{L,max} = 2.393 \text{k}\Omega$$