
EE204: Analog Circuits


Dept. of Electrical Engineering, IIT Bombay

Autumn Semester 2023

11-10-2023

Tutorial 7

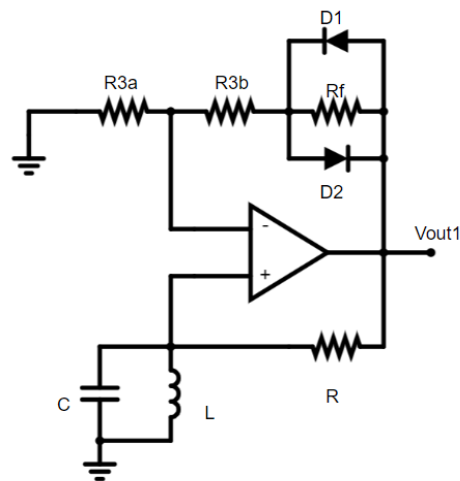
Q-1. Consider the oscillator circuit given below:



- Determine the loop gain $A(s)\beta(s)$, and find the frequency of oscillations.
- Find the condition on R_{3a} , R_{3b} and R_f for sustained oscillations.

Q-2.

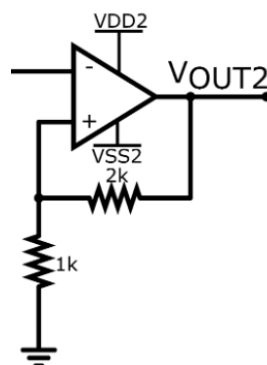
Consider the sine wave with an amplitude of 5V as the input to the Schmitt trigger circuit shown below:



Sketch the waveforms V_{out1} and V_{out2} and determine the duty cycles of the outputs if

- $V_{DD2}=15V$, $V_{SS2}=-15V$
- $V_{DD2}=15V$, $V_{SS2}=0V$

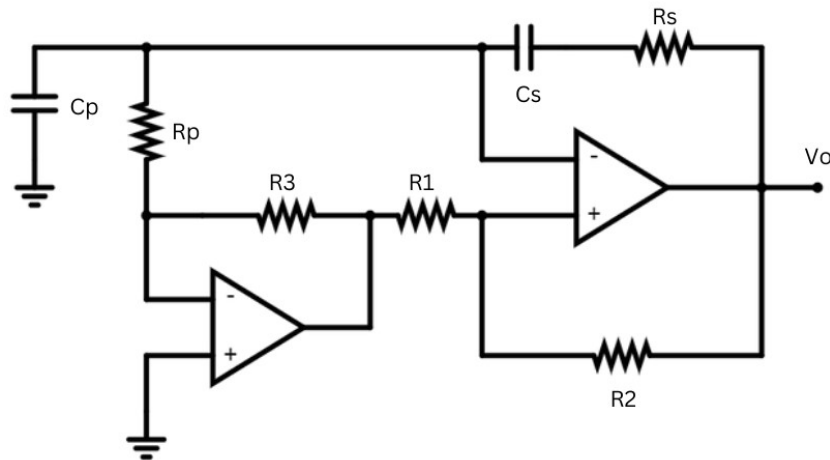Q3. Consider the oscillator circuit shown below:



- Evaluate the loop gain and show that the Barkhausen's condition for this circuit is:

$$(R_2/R_1)(1 + R_3/R_p) = R_s/R_p + C_p/C_s$$
- Verify that if we let $R_2/R_1 = C_p/C_s$, this condition simplifies to $R_3 = (R_1/R_2)R_s$.

Q1.

$$a. \quad A(s) = \left(1 + \frac{R_f + R_{3b}}{R_{3a}} \right) = \frac{V_o}{V_i}$$

$$\begin{aligned} \beta(s) &= \frac{V_f}{V_o} = \frac{\frac{1}{R}}{\frac{1}{R} + \frac{1}{sL} + sC} \\ &= \frac{\frac{1}{R} \cdot sL \cdot R}{sL \cdot R + R + sL} \times \frac{1}{LC \cdot R} \\ &= \frac{s \cdot \frac{1}{RC}}{s + s \cdot \frac{1}{RC} + \frac{1}{LC}} \end{aligned}$$

$$\therefore \text{loop gain } A(s) \cdot \beta(s) = \frac{s \cdot \frac{1}{RC} \cdot \left(1 + \frac{R_f + R_{3b}}{R_{3a}} \right)}{s + \frac{s}{RC} + \frac{1}{LC}}$$

$$b. \quad s = j\omega$$

$$A(j\omega) \beta(j\omega) = \frac{j \frac{\omega}{RC}}{(-\omega^2 + \frac{1}{LC}) + j \frac{\omega}{RC}} \cdot \left(1 + \frac{R_f + R_{3b}}{R_{3a}} \right)$$

for phase 0°

$$\omega_0^2 = \frac{1}{LC} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$


$$\text{for } |A(j\omega) \beta(j\omega)| \geq 1$$

$$\Rightarrow 1 + \frac{R_f + R_{3b}}{R_{3a}} \geq 1$$

$$\Rightarrow \frac{R_f + R_{3b}}{R_{3a}} \geq 0 \rightarrow \text{condition for sustained oscillations.}$$

Q3. $A(s) \cdot \beta(s)$

$$A(s) = \frac{V_f}{V_o}$$

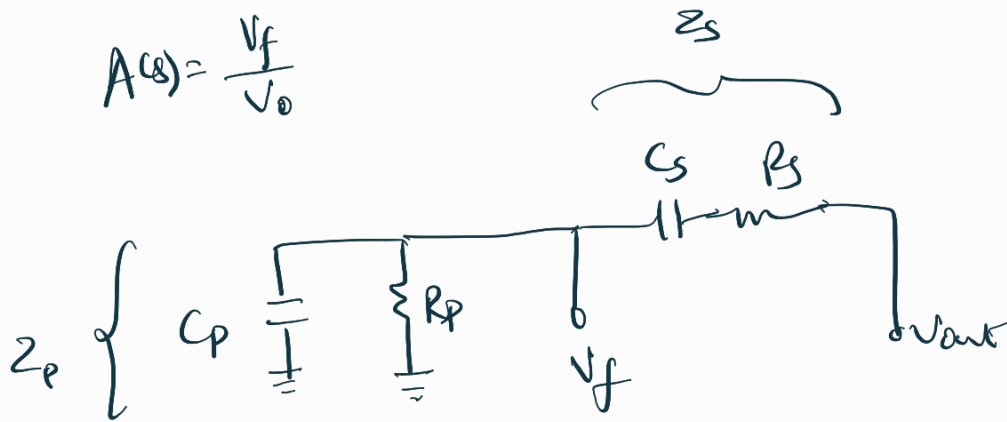

$$Z_p = \frac{R_p \cdot \frac{1}{sC_p}}{R_p + \frac{1}{sC_p}}$$

$$Z_s = R_s + \frac{1}{sC_s}$$

$$V_f = \frac{Z_p}{Z_s + Z_p} \cdot V_{out}$$

$$\beta(s) = \frac{V_f(s)}{V_{out}} = \frac{\frac{R_p}{sC_p}}{sR_pC_p + 1} \times \frac{1}{\frac{R_p}{1 + sR_pC_p} + R_s + \frac{1}{sC_s}}$$

$$= \frac{R_p}{(1 + sR_pC_p)} \times \frac{1}{\frac{R_p \cdot s \cdot C_s + R_s(1 + sR_pC_p) \cdot sC_s + (1 + sR_pC_p)}{(1 + sR_pC_p) \cdot sC_s}}$$


$$= \frac{s R_p C_s}{s^2 R_s R_p C_s C_p + s (C_s R_p + R_s C_s + R_p C_p) + 1}$$

$$= \frac{j\omega \cdot R_p C_s}{(1 - \omega^2 R_s R_p C_s C_p) + j\omega (C_s R_p + R_s C_s + R_p C_p)}$$

$$\omega_0 = \frac{1}{\sqrt{R_s R_p C_s C_p}}$$

$$\text{at } \omega_0 = \frac{1}{\frac{C_s R_p + R_s C_s + R_p C_p}{R_p C_s}} = \frac{1}{1 + \frac{R_s}{R_p} + \frac{C_p}{C_s}}$$

$$A(s) = \frac{V_o}{V_{in}}$$

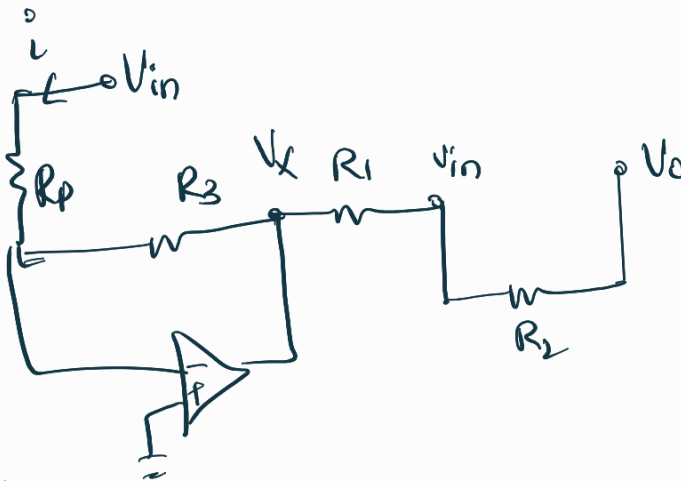

$$I = \frac{V_{in}}{R_p}$$

$$0 - \left(\frac{V_{in}}{R_p} \right) \cdot R_3 = V_x$$

$$V_{in} - V_x = \left(V_o + \frac{V_{in}}{R_p} \cdot R_3 \right) \cdot \frac{R_1}{R_1 + R_2}$$

$$\Rightarrow V_o = \left(V_{in} + V_{in} \cdot R_2 \right) \left(\frac{1}{1 + \frac{R_2}{R_1}} \right) - V_{in} \cdot R_2$$

$$V_{in} = \left(V_o + \frac{V_o}{R_p} \right) \cdot \left(\frac{R_3}{1 + R_2/R_1} \right) = V_o \cdot \frac{R_3}{R_p}$$

$$V_{in} \left(1 + \frac{R_3}{R_p} \right) \cdot \left(1 + \frac{R_2}{R_1} \right) - V_o \left(\frac{R_3}{R_p} \right) = V_o$$

$$\Rightarrow \frac{V_o}{V_{in}} = 1 + \frac{R_2}{R_1} \left(1 + \frac{R_3}{R_p} \right)$$

$$\Rightarrow A \cdot \beta = 1$$

$$\Rightarrow \left[1 + \frac{R_2}{R_1} \left(1 + \frac{R_3}{R_p} \right) \right] \left[\frac{1}{1 + \frac{R_3}{R_p} + \frac{C_p}{C_s}} \right] = 1$$

$$\Rightarrow \frac{R_2}{R_1} \left(1 + \frac{R_3}{R_p} \right) = \frac{R_3}{R_p} + \frac{C_p}{C_s}$$

b.


$$\frac{R_3}{R_p} \cdot \frac{R_2}{R_1} = \frac{R_3}{R_p}$$

$$R_3 = \left(\frac{R_1}{R_2} \right) \cdot R_s$$

Q2. If initially high

$$V_{HTR} = V_f = V_{out} \left(\frac{1k}{2k} \right)$$

$$= V_{DD}$$

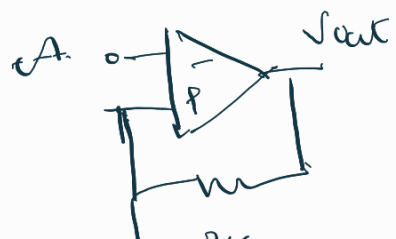

If $V_{in} \geq V_{HT}$
then O/P goes low.

When V_o is low

$$V_{LT} = V_+ = V_{SS} \left(\frac{1}{1+2} \right) = \frac{V_{SS}}{3}$$

When $V_{in} \leq V_{LT}$

then V_{out} goes high



$$V_o = A(V_+ - V_-)$$


if V_o is V_{DD}

$$V_+ = \frac{V_{DD}}{3}$$

if V_o is V_{SS}

$$V_+ = \frac{V_{SS}}{3}$$

a.

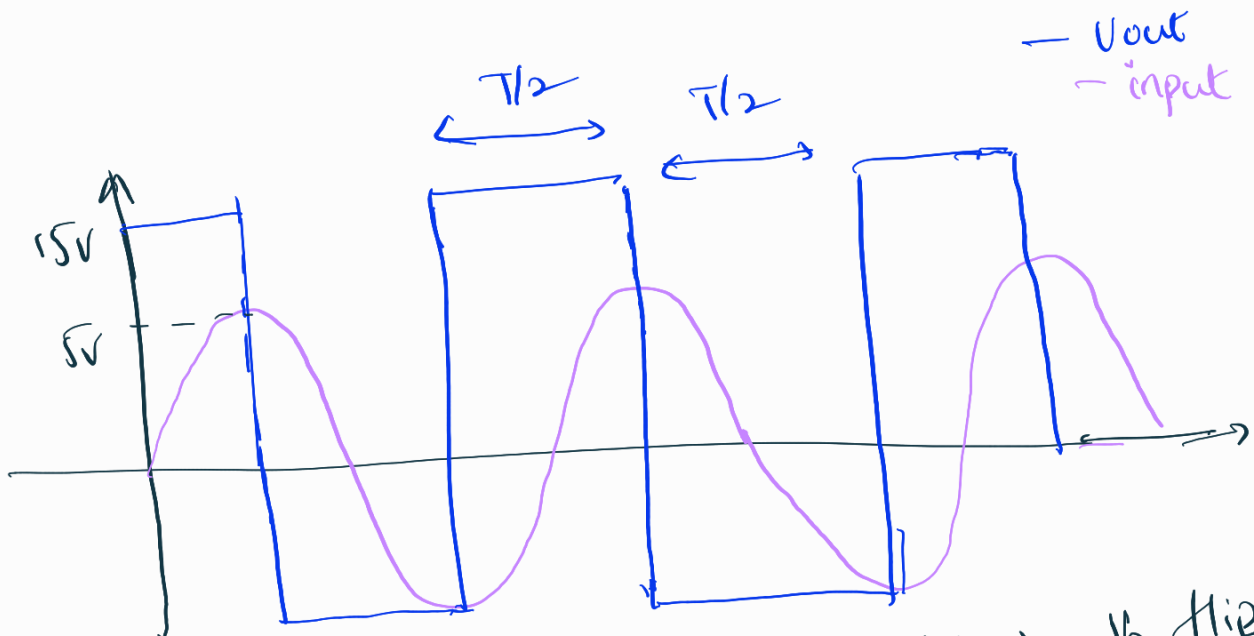


Starting V_o is high, when $V_{ip} \geq V_+ \left(\frac{V_{DD}}{3} \right)$ V_o flips
then when $V_{ip} \leq V_+ \left(\frac{V_{SS}}{3} \right)$ V_o flips again

duty cycle: $\frac{T/2}{T/2 + T/2} = 0.5$

b.



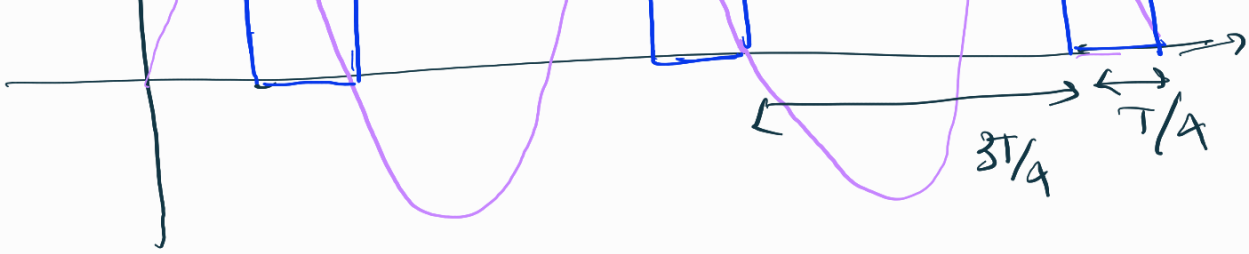

When o/p is low, $V_x = V_{SS}/3$
 if $V_{ip} \leq \frac{V_{SS}}{3}$, it becomes high again
 $V_{ip} \leq 0$

then when $V_{ip} \geq \frac{V_{DD}}{3}$ o/p becomes low again

duty cycle $\frac{\frac{3T}{4}}{\frac{3T}{4} + \frac{T}{4}} = 0.75$

