
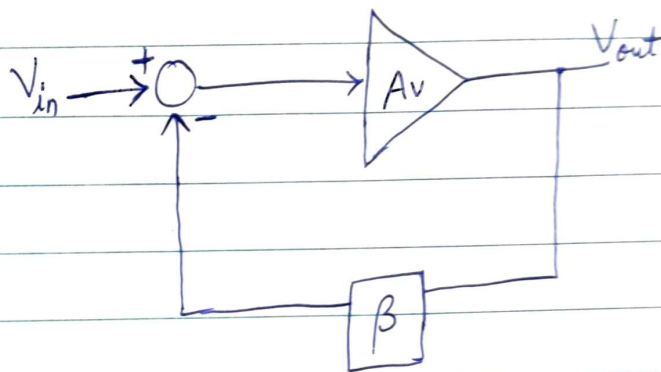


EE 204 : Analog Circuits

Assignment 1 : Solution

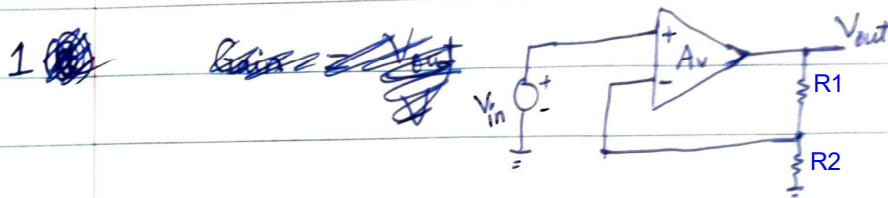

$$\text{Gain} = \frac{V_{out}}{V_{in}} = \frac{A_v}{1 + A_v \beta}$$

$$\text{where, } \beta = \frac{R_2}{R_1 + R_2}$$

$$(a) \quad \text{Gain} = \frac{A_v}{1 + A_v \beta} = \frac{10^4}{1 + 10^4 \times 0.1} = \boxed{9.99} \quad [1 \text{ mark}]$$

~~[1 mark]~~

OR

$$\text{Gain} = \frac{A_v}{1 + A_v \beta} \approx \frac{1}{\beta} \quad (\because A_v \beta \gg 1) = \frac{1}{0.1} = \boxed{10} \quad [1 \text{ Mark}]$$

$$(b) \quad V_{out} = \text{Gain} \times V_{in}$$

$$= 9.99 \times 0.15$$

$$= \boxed{1.4985 \text{ V}} \quad [1 \text{ mark}]$$

OR

$$V_{out} = \text{Gain} \times V_{in}$$

$$= 10 \times 0.15$$

$$= \boxed{1.5 \text{ V}}$$

[1 Mark]

$$(c) \quad \text{Voltage at (-)ve terminal} = \beta \times V_{out}$$

$$= 0.1 \times 1.4985$$

$$= \boxed{0.14985 \text{ V}}$$

[1 mark]

OR


$$\text{Voltage at (-)ve terminal} = \beta \times V_{out}$$

$$= 0.1 \times 1.5$$

$$= \boxed{0.15 \text{ V}}$$

[1 Mark]

2

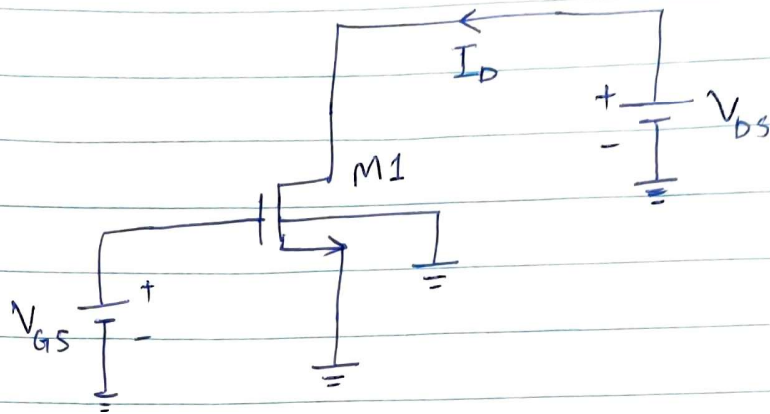

$$\left(\frac{W}{L}\right)_{M1} = \frac{3\mu\text{m}}{1\mu\text{m}}$$

$$V_t = 0.4\text{V}$$

$$\mu C_{ox} = 260\mu\text{A/V}^2$$

$$0 < V_{GS} < 1.8\text{V}$$

$$0 < V_{DS} < 1.8\text{V}$$

(a)

$$(i) \quad V_{GS} < 0.4\text{V}, \quad 0 < V_{DS} < 1.8\text{V} \quad [0.5\text{ Marks}]$$

~~(i)~~

$$(ii) \quad 0.4 < V_{GS} < 1.8\text{V}, \quad 0 < V_{DS} < V_{GS} - V_t \quad [0.5\text{ Marks}]$$

$$(iii) \quad 0.4 < V_{GS} < 1.8\text{V}, \quad V_{DS} > V_{GS} - V_t \quad [0.5\text{ Marks}]$$

$$(b) \quad I_D \Big|_{\text{ohmic region}} = \mu C_{ox} \frac{W}{L} \left[(V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$I_D \Big|_{\text{saturation region}} = \frac{1}{2} \mu C_{ox} \frac{W}{L} [V_{GS} - V_t]^2$$

[0.5] Marks of each correct calculation

2(b) Sample Calculations :-

Set 1 : $V_{GS} = 0.6 \text{ V}$

Ohmic region calculations :-

$$V_{DS} < V_{GS} - V_t$$

$$V_{DS} < 0.6 - 0.4 \text{ V}$$

$$V_{DS} < 0.2 \text{ V}$$

[0.5 Marks] point 1 : $V_{DS} = 0.15 \text{ V}$

Q

$$\begin{aligned} I_D &= \mu C_{ox} \frac{W}{L} \left[(V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right] \\ &= 260 \times 3 \times \left[(0.6 - 0.4) \times 0.15 - \frac{0.15^2}{2} \right] \mu\text{A} \\ &= 14.625 \mu\text{A} \end{aligned}$$

[0.5 Marks] point 2 : $V_{DS} = 0.08 \text{ V}$

$$\begin{aligned} I_D &= \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right] \\ &= 260 \times 3 \times \left[(0.6 - 0.4) \times 0.08 - \frac{0.08^2}{2} \right] \mu\text{A} \\ &= 9.984 \mu\text{A} \end{aligned}$$

Saturation Region Calculations :-

$$V_{DS} > V_{GS} - V_t$$

$$V_{DS} > 0.6 - 0.4 \text{ V}$$

$$V_{DS} > 0.2 \text{ V}$$

[0.5 Marks] point 1 : $V_{DS} = 0.4 \text{ V}$

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$= \frac{1}{2} \times 260 \times 3 \times (0.6 - 0.4)^2 \mu\text{A}$$

$$= 15.6 \mu\text{A}$$

[0.5 Marks] point 2 : $V_{DS} = 0.8 \text{ V}$

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$= \frac{1}{2} \times 260 \times 3 \times (0.6 - 0.4)^2 \mu\text{A}$$


$$= 15.6 \mu\text{A}$$

Similarly for Set 2 there will be 4 points [0.5 Marks] for each calculation.

Then fill in the Table.

	Set 1		Set 2	
	$V_{GS} = 0.6 \text{ V}$		$V_{GS} =$	
	V_{DS} (in V)	I_D (in μA)	V_{DS} (in V)	I_D (in μA)
Ohmic	0.08	9.984		
	0.15	14.625		
Saturation	0.4	15.6		
	0.8	15.6		

(c)

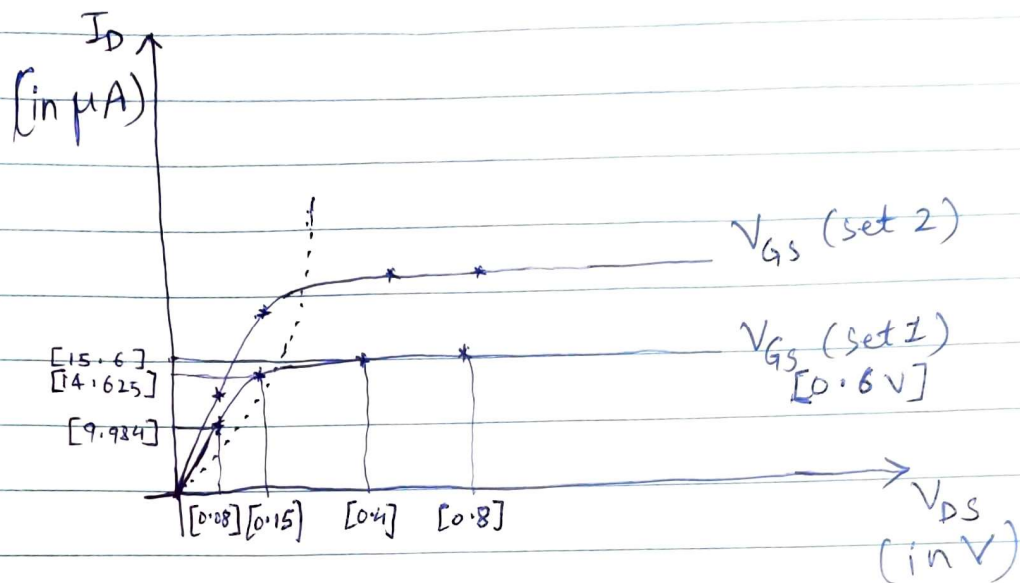

Correct sketch [1 Mark]

points on graph [0.5 Marks]

Note: Values on graph in \mathbb{R} & \mathbb{Q} brackets are only sample calculations of part (b).