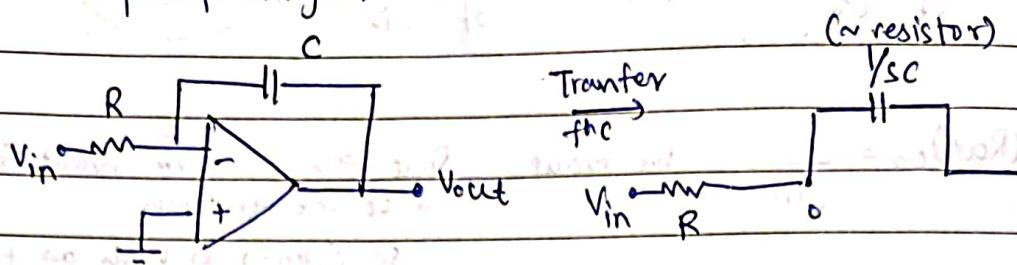


BODE PLOTS


For an op-amp integrator



$$\frac{V_{in} - 0}{R} = 0 - V_{out} \Rightarrow V_{out} = \left(-\frac{1}{RCs} \right) V_{in}$$


$$H(jw) = \frac{-1}{RCjw} \Rightarrow |H(jw)| = \frac{1}{RCw}$$

$$20 \log(|H(jw)|) = -20 \log(RCw) = -20 \log\left(\frac{w}{Y_{RC}}\right)$$

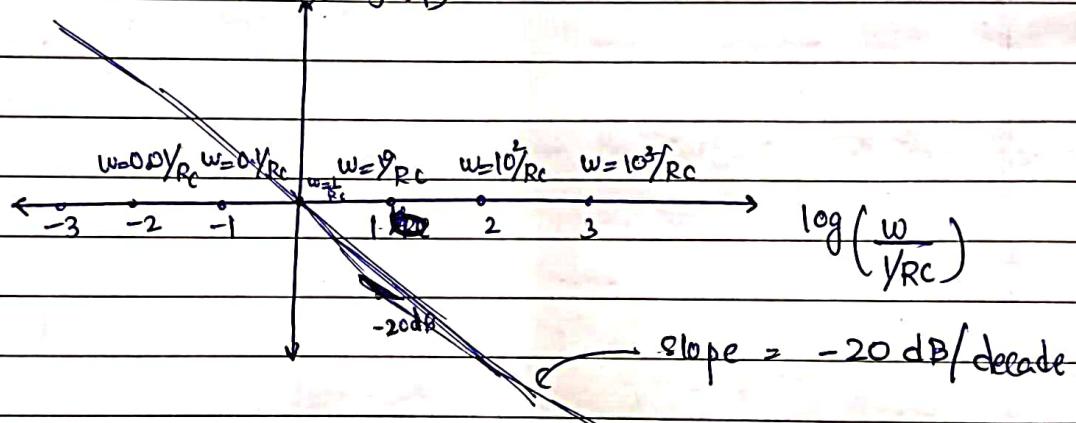


$$H(jw) = \frac{H_0}{1+jw/a} \quad |H(jw)| = 20 \log|H_0| - 20 \log|1+jw/a|$$

$$20 \log |H(jw)| = 20 \log |H_0| + \cancel{20 \log|1+jw/a|} + 20 \log \left| \frac{1}{1+jw/a} \right|$$

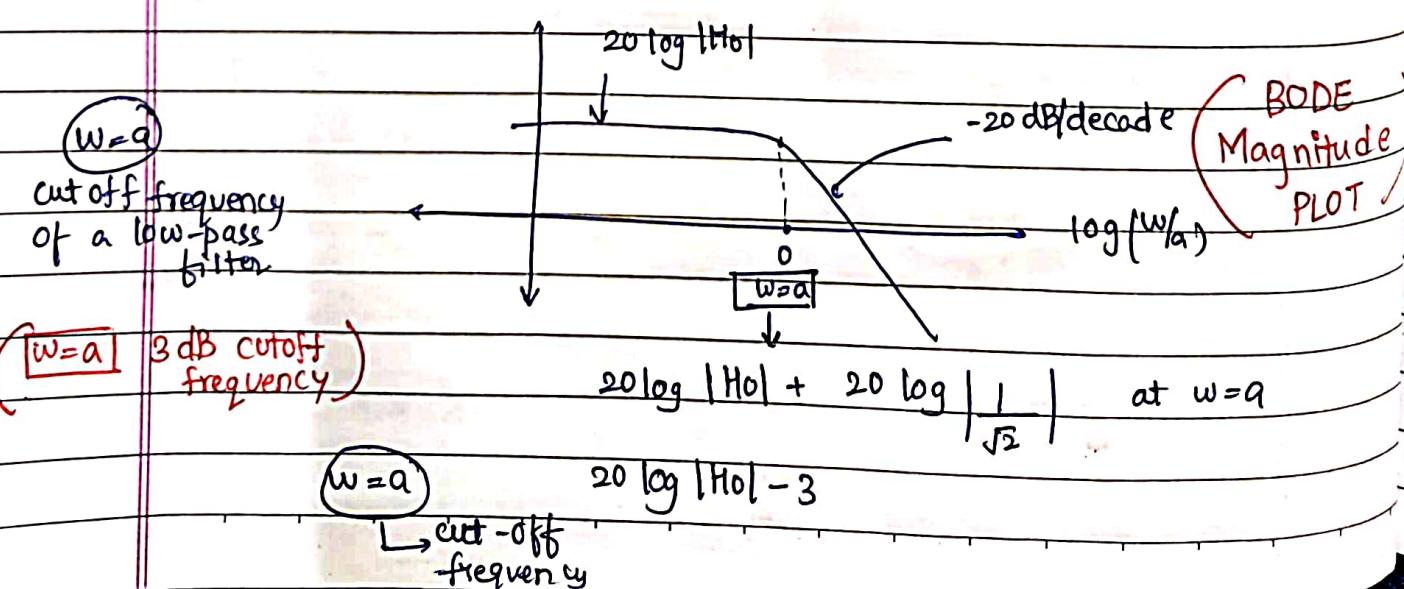

OP-AMP IC Analysis

Date _____
Page _____

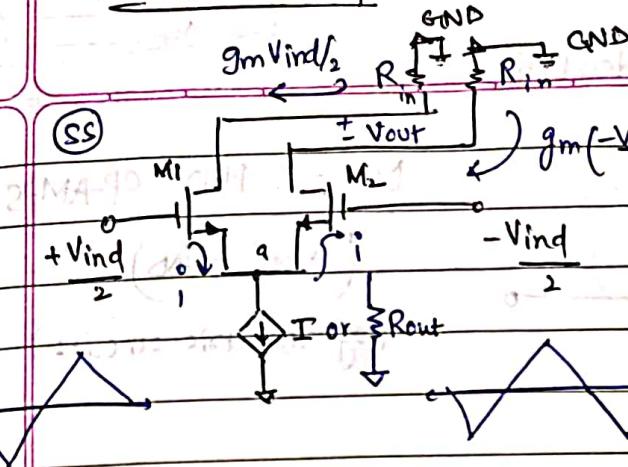

$g_m V_{ind}/2 \rightarrow$ The voltage at node 'a' won't change


2 symmetric transistors & resistors

→ This is a small-signal model. ⇒ (a) is a common-node

→ if $(V_{gs})_1$ and $(V_{gs})_2$ have opposite polarities

$s_1 \rightarrow a \rightarrow s_2$ s_1 and s_2 are same.

⇒ superposition:- For node 'a' →

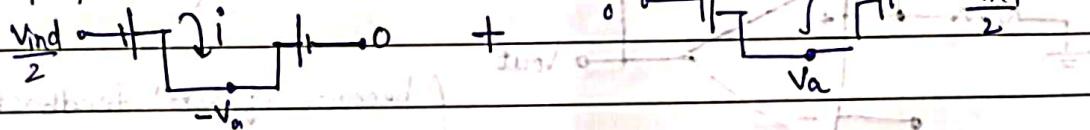

→ current changes its dirn, Va changes its polarity


→ superpose :- $V_a = 0$

$$V_{out} = g_m \left(2 \cdot V_{ind} \right) \rightarrow g_m V_{ind}$$

→ In Common-Mode $\rightarrow i \neq 0$ through R_{out}

$$V_{out} = -(g_m V_{id}) \cdot R_{in} \rightarrow \text{CS Amplifier}$$

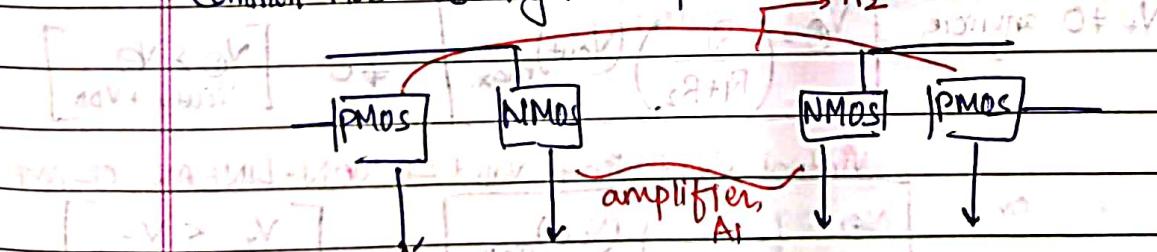→ Common Mode as high as possible $\rightarrow A_2$




currents from A_1 & A_2 are added up

More Op-Amp Non-idealities

Date _____
Page _____

Any internal/external noise

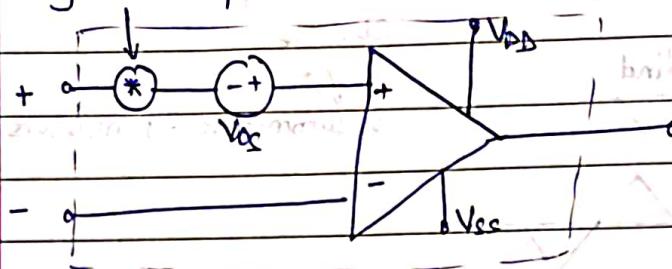

DUAL-SUPPLY OP-AMPS


$$(V_{SS} = -V_{DD})$$

(symmetric circuits)

V_{offset} → reason for putting it is due [represents all internal
to all 'internal mismatches']

DC; \sim few mV. (best)

Familiar Config. but with +ve feedback

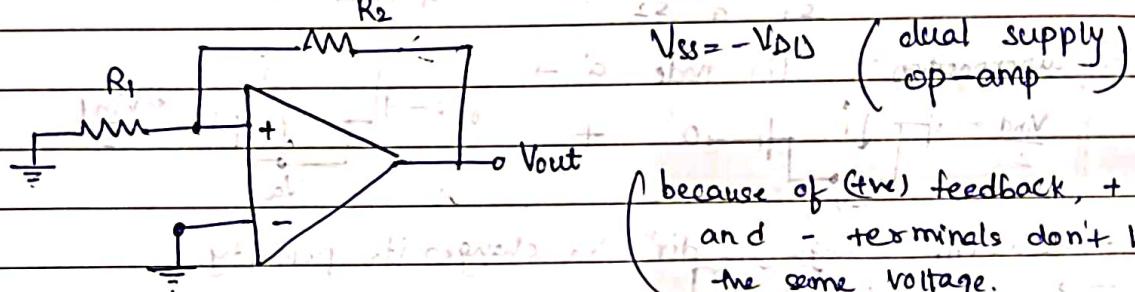

$$V_{SS} = -V_{DD} \quad (\text{dual supply})$$

because of (ve) feedback, + and - terminals don't have the same voltage.

$V_+ \uparrow \rightarrow V_{out} \uparrow \rightarrow$ more I flows $\rightarrow V_+ \uparrow$

if output slightly increases \rightarrow it keeps on increasing.

clamped to

$$V_{out} = (V_{out})_{\max.} \text{ or } (V_{out})_{\min.}$$

depends on NOISE the noise both create a -ve noise regenerative loop.

$V_+ \neq 0$ anymore

$$V_+ = \left(\frac{R_1}{R_1 + R_2} \right) (V_{out})_{\max.}$$

$\neq 0$

$$\begin{cases} V_+ > V_ \\ V_{out} = +V_{DD} \end{cases}$$


Virtual short isn't valid \Rightarrow NON-LINEAR OP-AMP

Or

$$V_+ = \left(\frac{R_1}{R_1 + R_2} \right) (V_{out})_{\min.}$$

$$\begin{cases} V_+ < V_- \\ V_{out} = -V_{DD} \end{cases}$$

(Comparator)

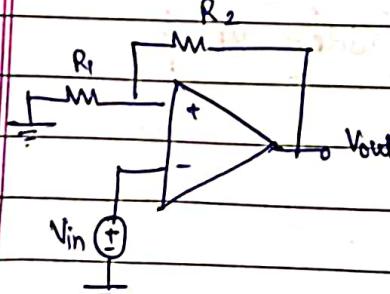

SCHMIDT TRIGGER

(Hysteresis Window)

$$(V_{out})_{\min.} \left(\frac{R_1}{R_1 + R_2} \right)$$

$$\left(\frac{R_1}{R_1 + R_2} \right) V_{out} \max.$$

V_{in}

very -ve

input is heavily (-ve) $V_{in} < V_f$ as V_+ is either $\left(\frac{R_1}{R_1+R_2}\right)(V_{DD})$ or $\left(\frac{R_1}{R_1+R_2}\right)(-V_{DD})$

$$\text{when, } V_{in} = \left(+ \left(\frac{R_1}{R_1+R_2} \right) V_{DD} \right)^+ \rightarrow V \rightarrow V_+ \\ \Rightarrow V_{out} = (V_{out})_{\min}$$

When they are equal \rightarrow op-amp gain becomes $\infty \rightarrow$ slight change in input causes a change in V_{out} .


Hysteresis Window

uncertainty

if the input is b/w $\left(\frac{R_1}{R_1+R_2}\right)V_{DD}$ and $\left(\frac{R_1}{R_1+R_2}\right)V_{DD}$,

we don't know what V_{out} is.

SCHMITT TRIGGER APPLICATIONS

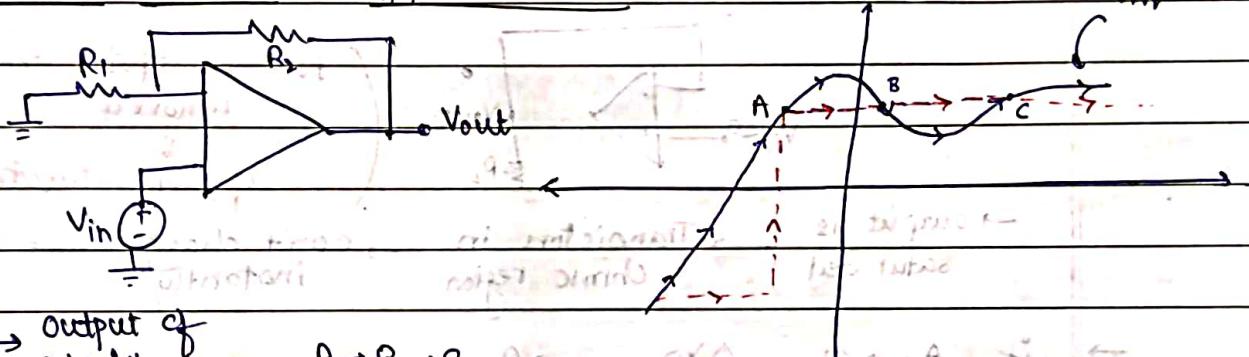

NOISE fluctuations etc. \rightarrow Output of Schmitt trigger doesn't change.

A \rightarrow B \rightarrow C
Here the input reduces but output remains same.

Hysteresis window \rightarrow b/w the window of noise.


1) shape output

2) Reduce fluctuations.

NON-LINEAR ELEMENTS

DIODE

(rectifiers)

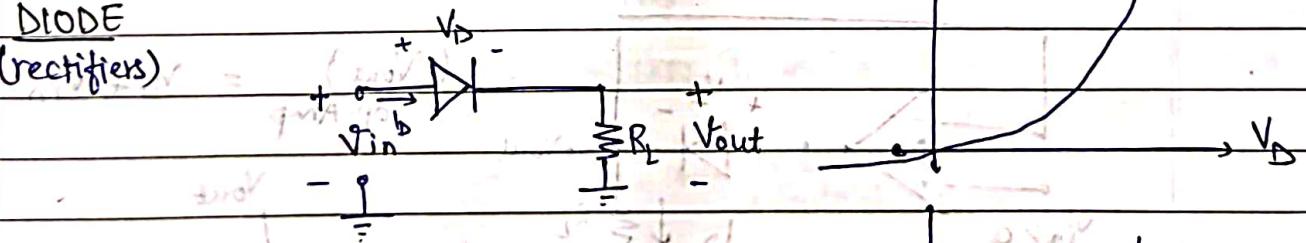

pass +ve & block -ve,

but $V_D \neq 0$

some part of input signal isn't transmitted

when diode is on,

$$V_{out} = V_{in}$$


$$\Rightarrow \left(\frac{\Delta V_{out}}{\Delta V_{in}} = 1 \right)$$

$$V_{out} = V_{in}$$

slope = 1

$$V_{in}$$

(Dual Supply Op-Amp)

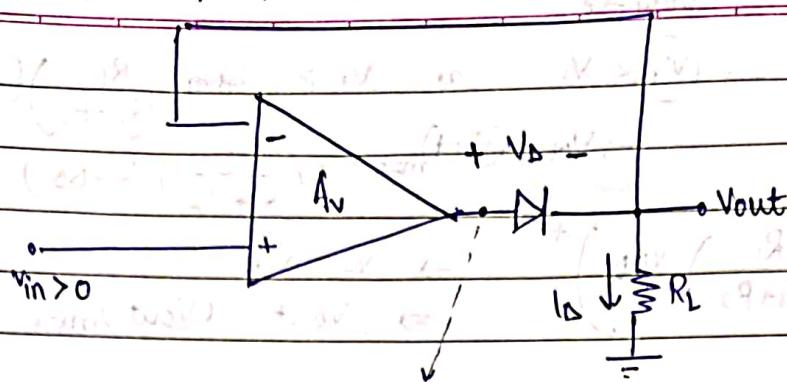


Here, $(\Delta V_{in} - R_L \Delta I_D) A_v - \Delta V_D = R_L (\Delta I_D)$

so, $\Delta I_D R_L (1 + A_v) = A_v \Delta V_{in} - \Delta V_D$

$$(\Delta I_D) R_L = \frac{\Delta V_{in} \times A_v}{(1 + A_v)} - \frac{\Delta V_D}{(1 + A_v)}$$

small signal equation.

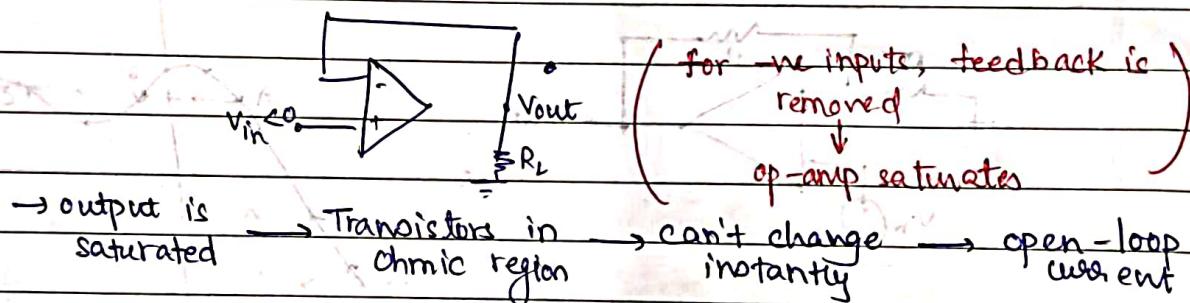
if $I=0 \rightarrow$ diode is broken (input is -ve) \rightarrow output = 0



→ if $A_v \rightarrow \infty$ $\frac{\Delta V_D}{(1 + A_v)} \rightarrow 0$


loop-gain = A_v , $b=1$

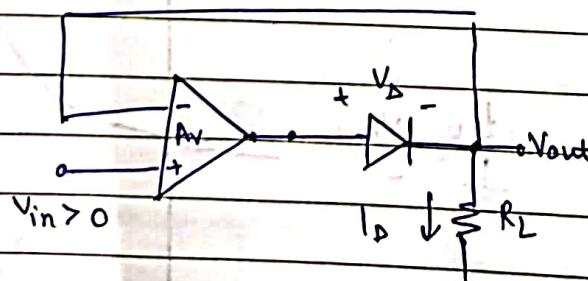Simple Half-wave Rectifier using Diode And Op-Amp in the Feedback




$$\frac{(V_{out})_{op-Amp}}{V_{in}} = V_D + V_{in}$$

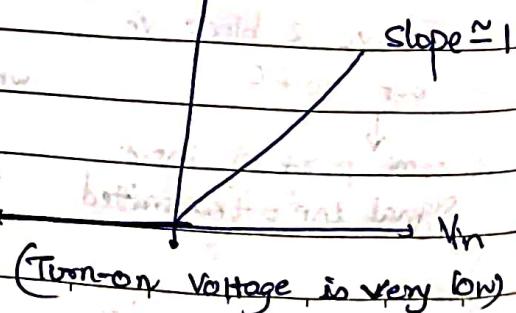Output of op-amp follows V_{in} with an additional V_D



→ (energy-harvesting)

Date _____
Page _____

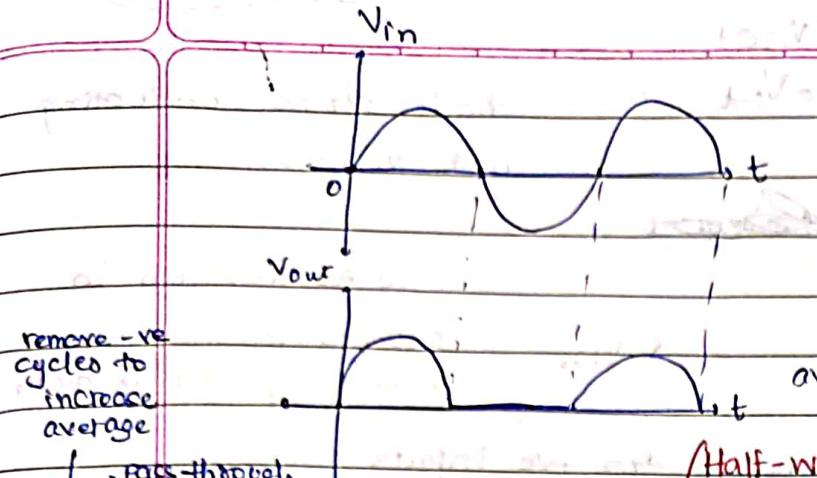

we don't need to know V_D explicitly if $A_v \rightarrow \infty$.

effective turn-on voltage $\rightarrow 0$

remove -ve cycles to increase average


↳ pass-through low-pass filter & generate DC.

→ When $V_{in} < 0$

(Half-wave) rectifier

For -ve input \rightarrow output $\rightarrow 0$

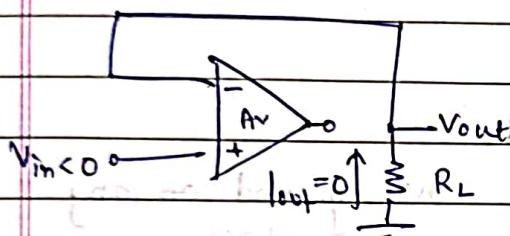DIODE IS OFF
diode will be off ($I = 0$)
(as $I < 0$)



Op-Amp gets saturated \rightarrow Speed limitation

(No Feedback)

Transistors ON \rightarrow OFF

HIGH FREQ. \rightarrow OP-AMP not the best choice

If the frequency of sine wave is very high \rightarrow waveform distorts

parasitic capacitance of diode

Transistors in op-amp

INVERTING OP-AMP BASED

SIMPLE HALF-WAVE RECTIFIER (FULL)


$N_{in} < 0 : D \text{ is ON}$

$$V_{out} = -\left(\frac{R_2}{R_1}\right) V_{in}$$

$V_{in} > 0 : D \text{ is OFF}$

Problem:

R_2 is load

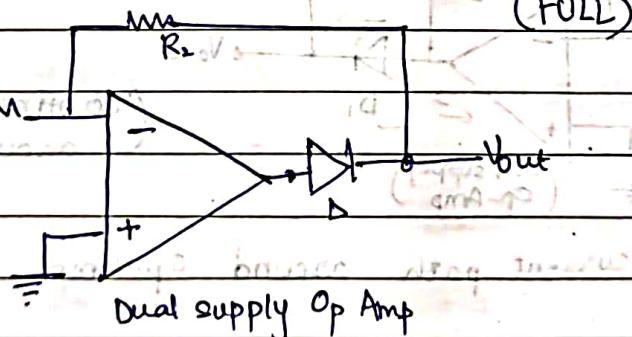

$V_{in} < 0 : V_{out} > 0$ I: Right to left in $R_2 \Rightarrow$ I from diode in

diode

D is ON \leftarrow D can conduct

$$V_{in} < 0 : V_{out} = -\left(\frac{R_2}{R_1}\right) V_{in}$$

$$V_{in} > 0 : V_{out} = 0 V_{in}$$

when diode is off, Op Amp is in

load \rightarrow connected b/w output & virtual ground

OPEN-LOOP

can't connect directly from output to ground \rightarrow path from V_{in} to GND.


voltage across R_2
connected to
virtual GND
 $V_{out} - V_O$ ($V_O = 0$)

Date _____
Page _____

$$\text{slope} = -\frac{(R_2)}{(R_1)}$$

$$= \frac{V_{R_2}}{R_2} = V_{out}$$

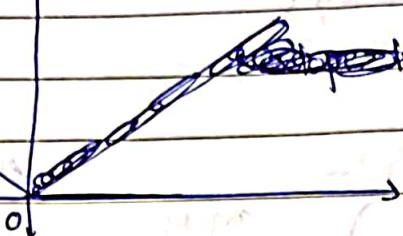diode stops conducting
with $V_{in} < 0$.



DUAL Version is
always possible by
changing dir^n of diode

→ we can change the conduct for +ve inputs.
dir^n of diode

→ as no current in op-amp, no current in $R_2 \Rightarrow V_{out} = 0$.




conducts in
this dir^n
only

Limitations → 1) R_2 is the load,

not ground on any
place

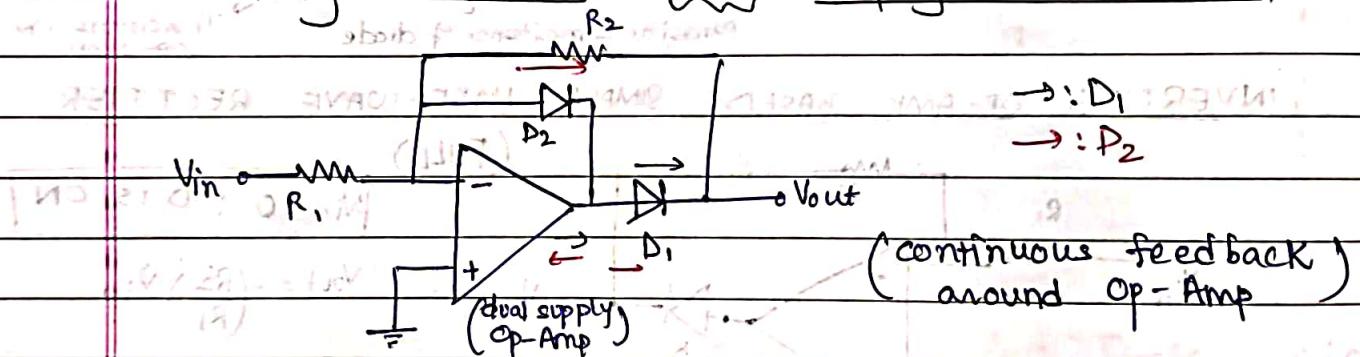2) Speed limitation.

Overcoming Limitations :- MORE clamping diodes in HWR.




bidirectional - current path around Op-Amp

both can't
be ON at
the same
time

$V_{in} < 0 : D_1 \rightarrow \text{ON}, D_2 \rightarrow \text{OFF}, V_{out} = -\left(\frac{R_2}{R_1}\right) V_{in} > 0$

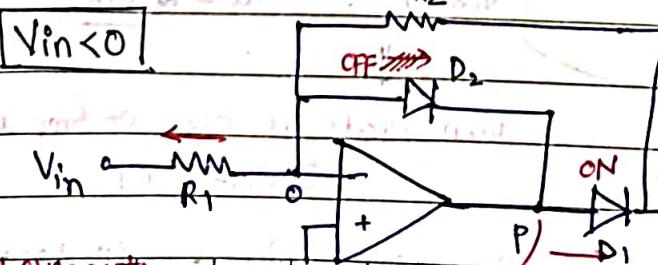$V_{in} > 0 : D_1 \rightarrow \text{OFF}, D_2 \rightarrow \text{ON}, V_{out} = 0$



$V_{out} > 0$


at P, $V = V_{out} + V_D > 0$

D_2 can't conduct

$\text{all currents flowing out} = (V_{on})_{D_1} + V_{out} (> 0)$

(TURN OFF) $I_{D_2} = 0$

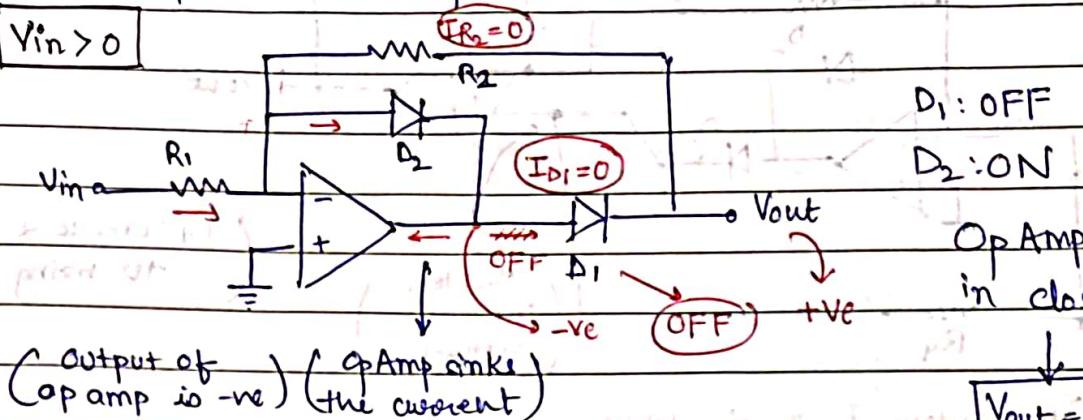D_2 : Keep feedback loop 'active' when D_1 is OFF.



FULL-WAVE RECTIFIER (FWR)

HWR: waste of energy

FWR

$$V_{out} = |V_{in}|$$

V_{in}



(-ve cycle \Rightarrow +ve cycle)

\rightarrow (Circuit \rightarrow gives you absolute value of the input as output)

V_{out}

$$V_{out} = K_2 (-V_{in}) + K_1 (+V_{in})$$


$m = -a$

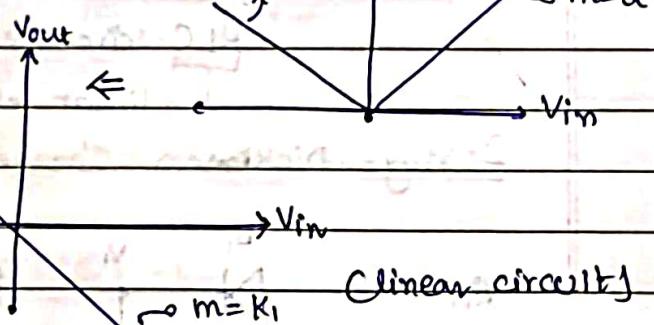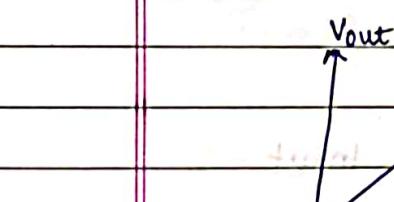

L.C. such that slope remains 'a' always. (Opp. polarity, same magnitudes)

Dependent on a

For output voltage V_{out} , V_{in}

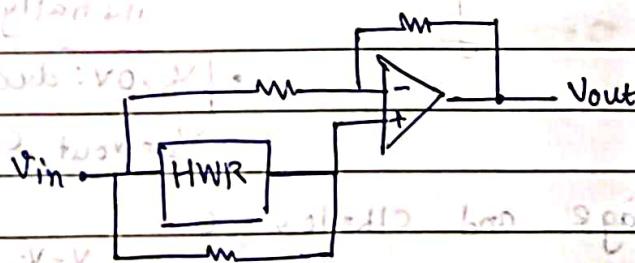


HWR + Non-inverting Amplifier

($R_4 \rightarrow$ Why?)

(combining the two parts)


(Dual Supply Op-Amps)

Date _____
Page _____

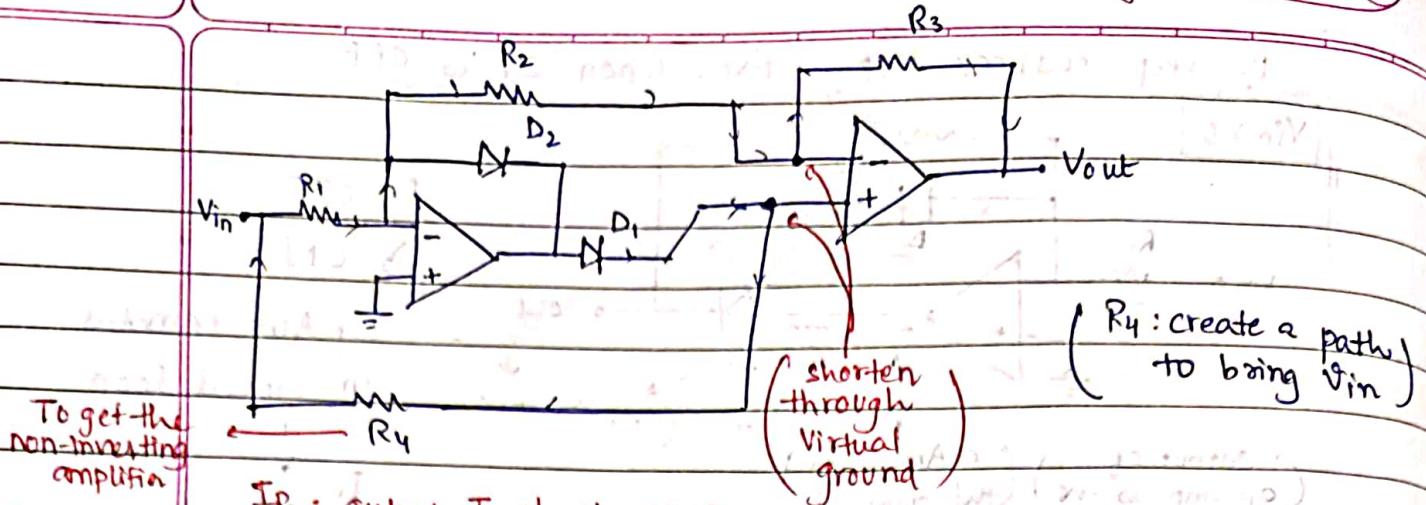

$$\rightarrow \text{Vin} > 0 : D_1 \rightarrow \text{ON}, D_2 \rightarrow \text{OFF} \Rightarrow V_{\text{out}} = \left(1 + \frac{R_3}{R_2}\right) \text{Vin} \quad (\text{Vin} > 0)$$
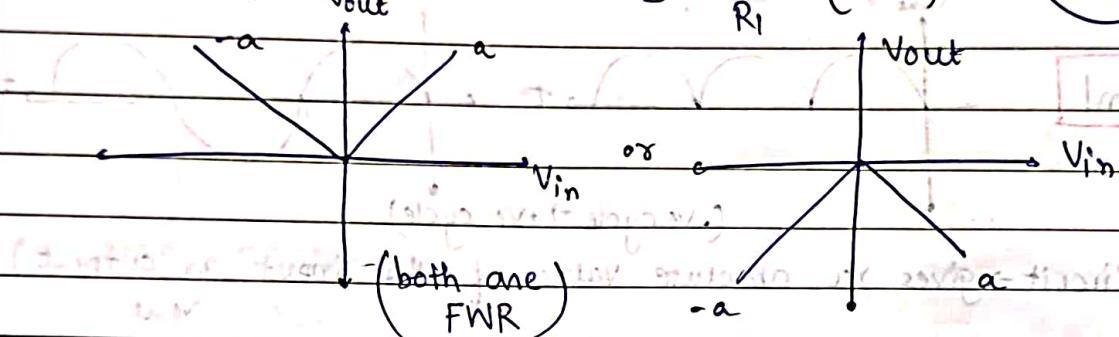
$$\text{Vin} < 0 : D_1 \rightarrow \text{OFF}, D_2 \rightarrow \text{ON} \Rightarrow \frac{R_3 + R_2}{R_1} (-\text{Vin}) \quad (\text{check})$$




DC to DC conversion using Diode-Capacitor Network

RLC circuits

linear elements

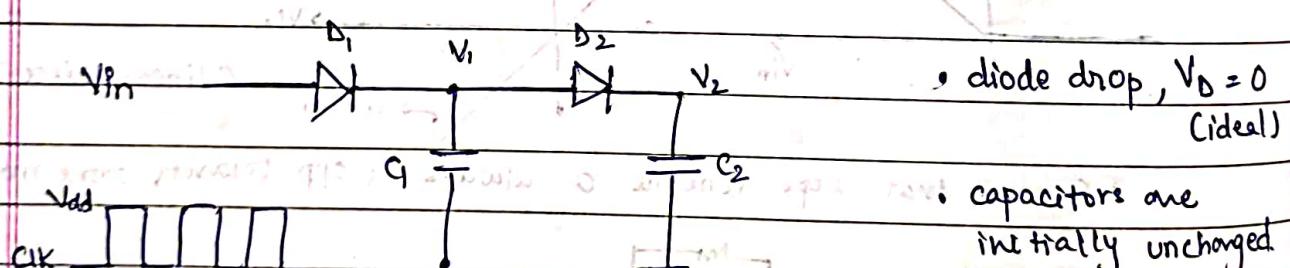2-stage Dickson Charge Pump with DC Input




\rightarrow Vin is a low DC Voltage and $\text{CLK} = \text{low} = 0$


$\rightarrow V_1 = V_2 = V_{\text{in}}$

Q across each capacitor, $Q_1 = Q_2 = C_c V_{\text{in}}$

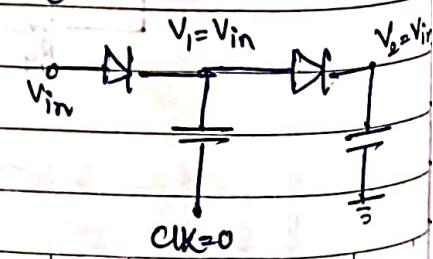Total charge $Q_{T-\text{low-CLK}} = 2C_c V_{\text{in}}$





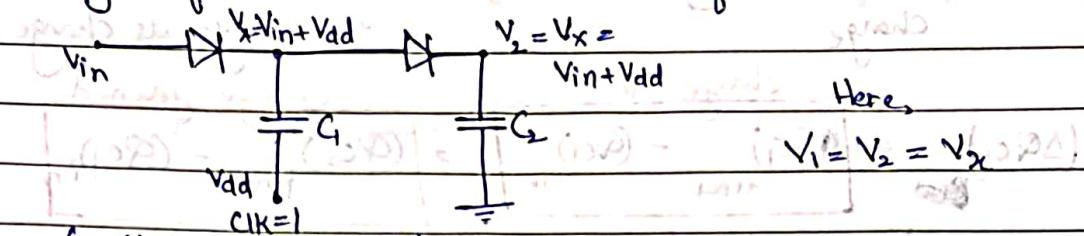charge of $+V_{DD}$ at the node of $C_1 \rightarrow$ so $V_1 = V_{in} + V_{dd}$





(a little after rising edge)

$(T \rightarrow 0)$

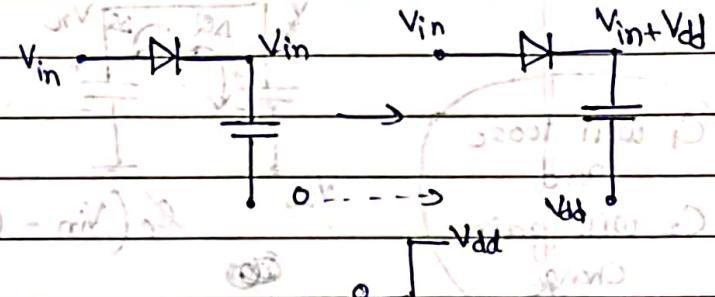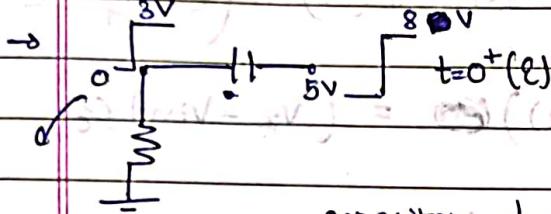


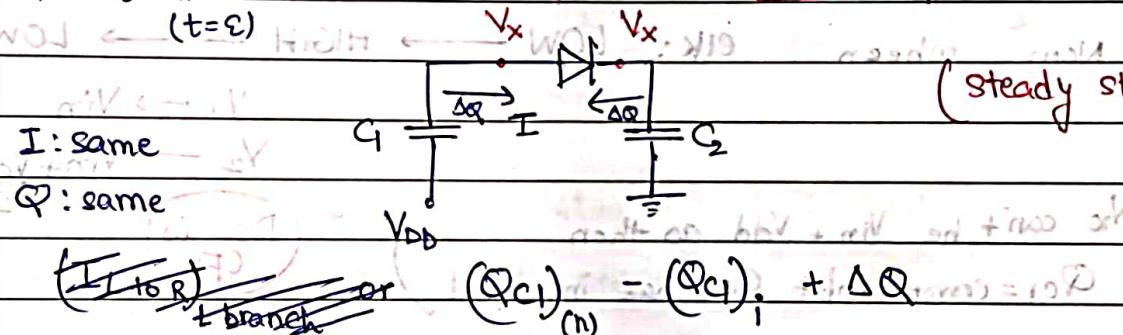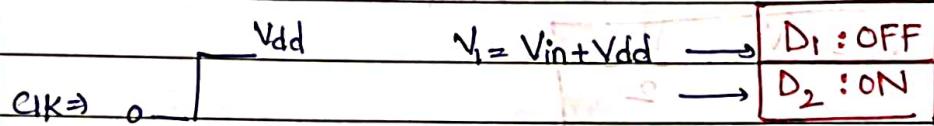capacitor doesn't allow voltage difference across it to change




Huge current flows b/w two capacitors.

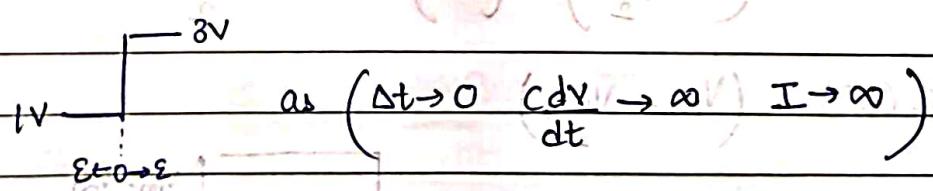impulsive current $\Rightarrow (\Delta Q)$ change in charge in $t \rightarrow 0$.



$V_{C1} = V_{C2} = V_{in}$ (initially)

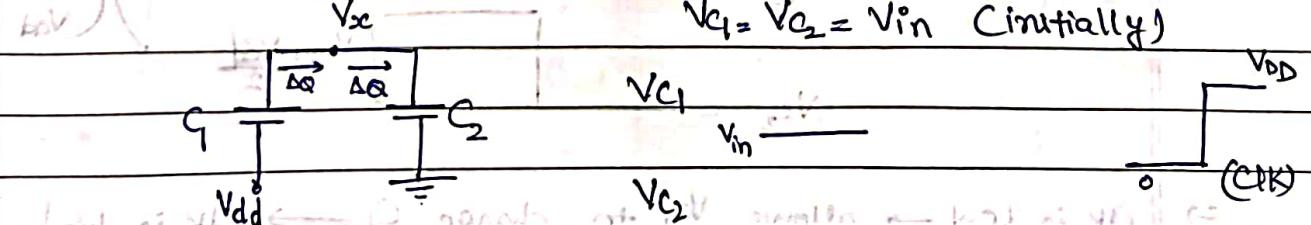


both can't be $V_{in} + V_{dd}$ as
both can't be someing current.

(CHARGE CONSERVATION)

Date _____
Page _____

if one capacitor changes its charge → the other one also has to change its charge.
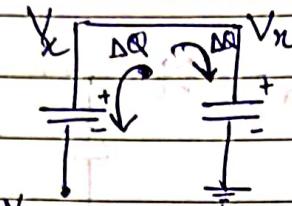
$$(\Delta Q_{C_1})_{\text{lost}} = (Q_{C_1})_{\text{final}} - (Q_{C_1})_{\text{in}} = (\Delta Q_{C_2})_{\text{gained}} = (Q_{C_2})_{\text{final}} - (Q_{C_2})_{\text{in}}$$



C_1 will loose and
 C_2 will gain charge.

CHARGE CONSERVATION

$$((C_1)_f - (C_1)_{in}) (-1) = ((C_2)_f - (C_2)_{in})$$

$$C_C (V_{in} - (V_x - V_{dd})) = (V_x - V_{in}) C_C$$

$$-V_{in} + V_{dd} + V_{in} = V_x - V_{in}$$

$$2V_x = 2V_{in} + V_{dd}$$

$$V_x = \frac{V_{in} + V_{dd}}{2}$$

Now, when CLK : LOW → HIGH → LOW

(other phase)

$$V_1 \rightarrow V_{in}$$

$$V_2 \rightarrow V_{in} + V_{dd}$$

V_x can't be $V_{in} + V_{dd}$ as then


Q_{C_1} = constant but Q_{C_2} has increased

D_2 is OFF

$\frac{1}{C_1} \frac{1}{C_2}$ (polarity also may reverse)

$$V_{C_1(O^+)} = \left(V_{in} + \frac{V_{dd}}{2}\right) - (V_{dd}) = V_{in} - \frac{V_{dd}}{2}$$
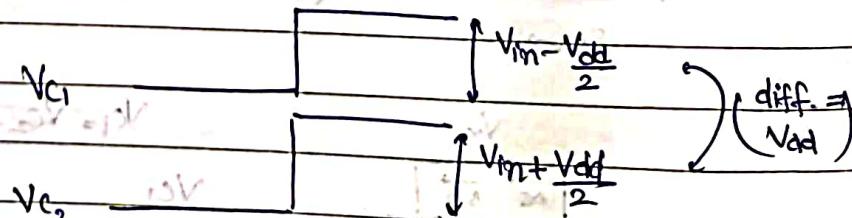
$$V_{C_2(O^+)} = \left(V_{in} + \frac{V_{dd}}{2}\right)$$



⇒ CLK is Low → allows V_{in} to charge C_1 → CLK is high

Transfers of charge to C_1

condition must be used if there
is a voltage drop also

→ After many cycles, V_x becomes so high that D_2 can never be ON.

$C_{1K} \rightarrow Q_2$ charges $V_{in} \rightarrow Q_1$ charges.

⇒ K-CYCLES

$$V_x = V_{in} + \left(\frac{V_{dd}}{2}\right) + \left(\frac{V_{dd}}{2^2}\right) + \dots + \frac{V_{dd}}{2^K}$$

$$\text{co. } V_x = V_{in} + V_{dd} \left(1 - \frac{1}{2^K}\right) \xrightarrow{K \rightarrow \infty} V_x = V_{in} + V_{dd}$$

2nd cycle

$$\frac{d}{dt}(V_{dd} - V_x + V_{in}) = (V_x - (V_{in} + V_{dd}/2)) \frac{d}{dt}$$

$$2V_x = 2V_{in} + V_{dd} + \frac{V_{dd}}{2} \Rightarrow V_x = V_{in} + \frac{V_{dd}}{2} + \frac{V_{dd}}{2^2}$$

$$\text{For } V_{in} \approx V_{dd} \Rightarrow V_x \approx 2V_{out} \quad \text{and so on.}$$

⇒ We can stack them such that V_x is a GND of next stage.

→ Use the circuit \rightarrow 1) NO supply needed

2) Instead of a clock, an AC signal can be used.

$$V_{in} = 0$$

CLK: min. value ≠ 0

Sine wave (AC) $\rightarrow (V_{in}=0 \text{ also}) \rightarrow \text{output (AC)}$


(which can go -ve)

(works here)


V_{out} \downarrow get a AC to DC converter \downarrow without any supply
 $-V_{out}$ \downarrow (DC output.)

OSCILLATORS

RLC circuit \rightarrow

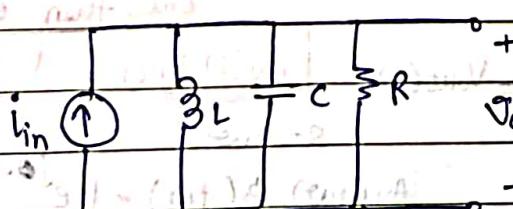

parallel - RLC

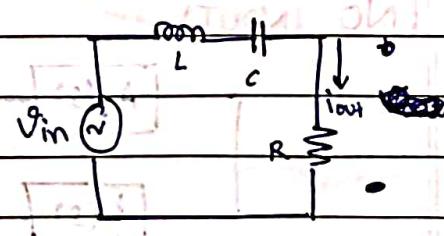

series - RLC

the only lossy element: **resistor**

(never can have a sustainable oscillation with a lossy element)


Parallel RLC: $R \rightarrow \infty$

Series RLC: $R \rightarrow 0$

$$I_C = C \frac{dV_C}{dt}$$

$$V_C = -L \frac{dI_C}{dt}$$

$$V_L = -V_C = L \frac{dI_C}{dt}$$

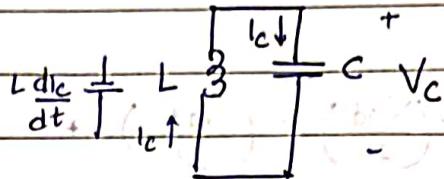


$$-V_C = L \frac{dI_C}{dt}$$

$$\Rightarrow ((\text{lossy } V + \text{lossy } V) - \frac{dV_C}{dt} = L \frac{d^2 I_C}{dt^2}) \text{ or}$$

$$I_C + LC \frac{d^2 I_C}{dt^2} = 0$$

resonance $V_C = \omega V_L$

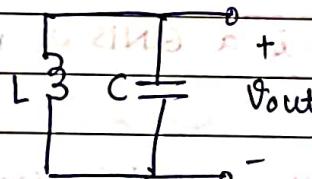
exchange of energy b/w inductor & capacitor



$$V_{out} = \int I_C dt \quad (\Delta\phi = -90^\circ)$$

$$I_C(t) = I_{cm} \sin(\omega_0 t)$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

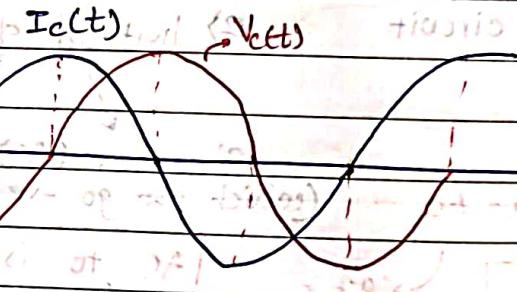

To compensate losses

Active elements to supply energy

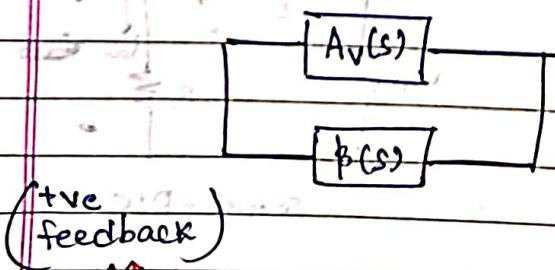Oscillation Based On Linear Feedback
(NO INPUT)



only then an oscillator

$$s = j\omega$$

$$A_V(j\omega) B(j\omega) = 1 - e^{j\omega T}$$

$$|T(j\omega)| = 1$$

$$\Im T(j\omega) = 0$$

(Barkhausen's Criteria)


if $A_{v(s)} \beta(s) > 0 \rightarrow$ non-linear

$\angle \theta \rightarrow$ oscillations decay down

Barkhausen's
Criteria \Rightarrow


$$|T(j\omega)| = 1 \quad \Im T(j\omega) = 0 \quad (T(j\omega): \text{loop gain})$$

Lossless Circuit

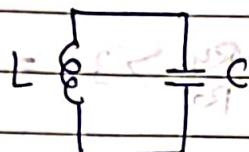

LC oscillator \rightarrow energy only transfers. NO LOSS

WIEN-BRIDGE OSCILLATOR

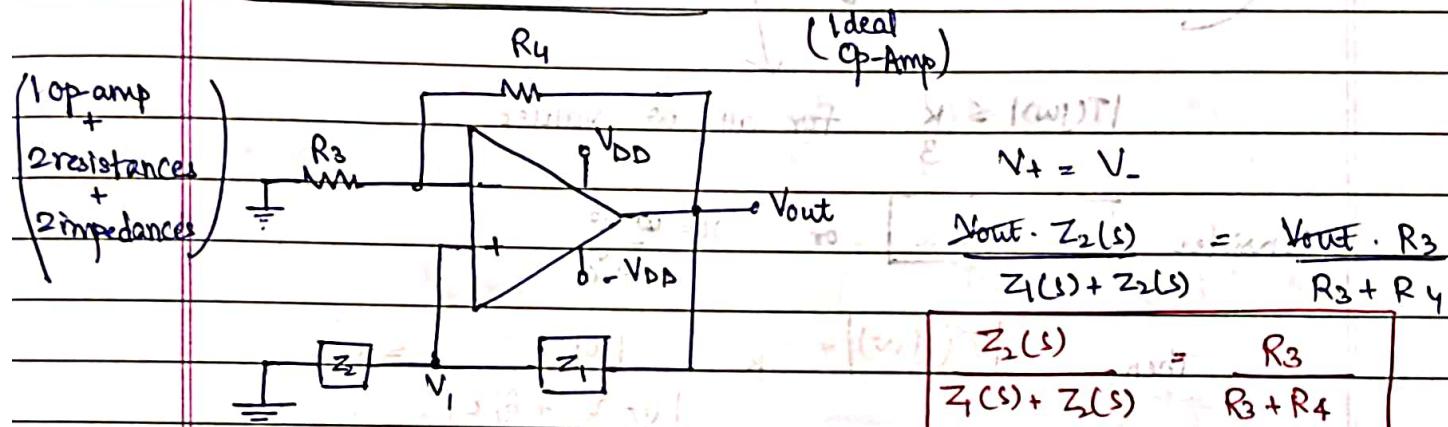

Z_1, Z_2 are made of R, C elements.

(simplest)

Z_1 : First-order series to open tve feedback at $s=0$.

inductors in CMOS are lossy \rightarrow E-friendly and not B-friendly




Z_1 : open \rightarrow series RC

Z_2 : close \rightarrow bias tve terminal at DC

be connected to the GND

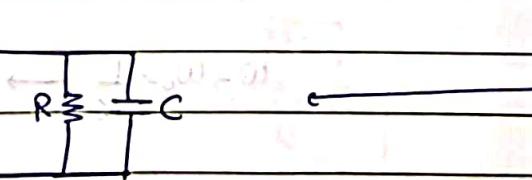Z_2 : First-order parallel R-C + bias tve terminal at DC



FOR
DC

$$V_i(s) = \frac{\left(\frac{R}{RCS+1}\right)}{\left(\frac{R}{RCS+1}\right) + \left(\frac{R+L}{SC}\right)}$$

$$V_{out} = \frac{RCS}{RCS + RCS(1+RCS) + RCS + 1}$$

$$V_i(s) = \frac{RCS}{R^2C^2S^2 + 3RCS + 1}$$

$$V_{out}(s)$$

$$V_{out}(s) = K \cdot V_i(s) \quad K = 1 + R_4$$

R_3

so,

$$\left(\frac{jRCw}{(1-R^2C^2w^2) + 3jRCw} \right) \times (K) = 1$$

Loop-Gain = 1

$$w = w_0 = \frac{1}{RC} \Rightarrow T(jw_0) = \frac{K}{3}$$

$$\text{Then, } \frac{K}{3} \geq 1 \Rightarrow K \geq 3 \Rightarrow 1 + \frac{R_4}{R_3} > 3 \Rightarrow \frac{R_4}{R_3} > 2$$

practical conditions

$|T(j\omega)| \leq \frac{K}{3}$ for all ω values

$$|T(jw)| \leq \frac{K}{3} \quad \text{for all } w \text{ values}$$


Consider $n = RCW$ or $n = \frac{w}{w_0}$

$$\text{Then, } (2) |T(jw)| = k \left(\frac{|x|}{\sqrt{(1-x^2) + 3jx}} \right) \leq 1.$$

$$|T(w)| = k|x|$$

$$|(1-x^2) + 3jx|$$

↳ always ≤ 1 .

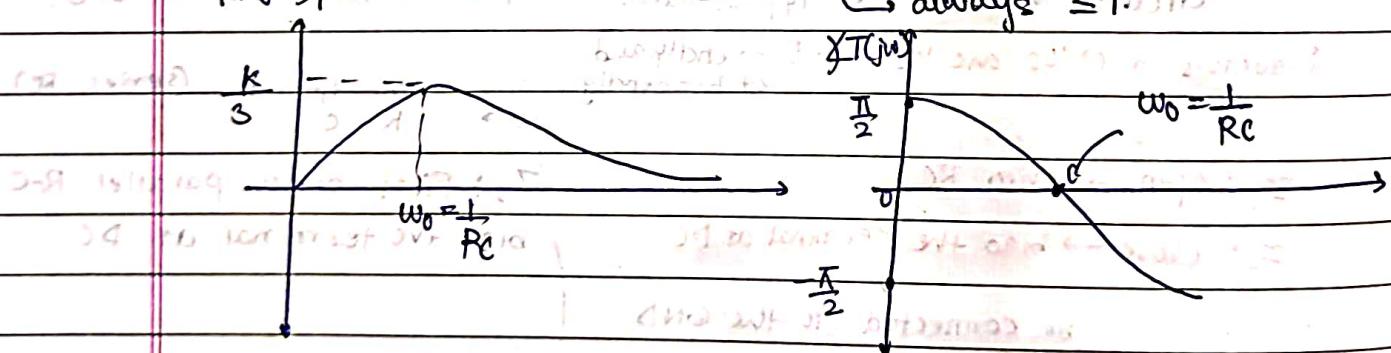

$\omega = \omega_0 = \frac{1}{RC} \rightarrow$ only frequency where the phase of loop-gain = 0

(Barkhausen's criteria)

e.g. - Target Value of oscillation frequency = 20 kHz (Barkhausen's criteria)

$$w_0 = 2\pi \times 20 \text{ kHz} \Rightarrow \frac{1}{RC} = 2\pi \times 20 \text{ kHz} \Rightarrow RC = 8 \mu\text{s}$$

$$1 + \frac{R_4}{R_3} = 3 \Rightarrow \frac{R_4}{R_3} = 2$$


start value

(has one-side ground)

$$R = 40\text{ k}\Omega \Rightarrow$$

$$C = 400\text{ pF}$$

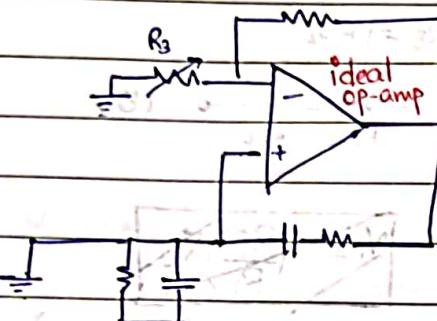$R_4 = 20\text{ k}\Omega \rightarrow$ start \rightarrow charge $R_3 = 10\text{ k}\Omega$ and then change until loop gain



unity-gain frequency of Op-Amp $\gg 20$ KHz

(magnitude of gain(loop) becomes ONE)

$$\frac{V_{id}(j\omega)}{V_{out}(j\omega)} = \frac{A(j\omega)}{1 + j\omega/\omega_p}$$

$$A(\omega_0) = 10^4$$

$$\text{Then, } |A(j\omega)| \approx A(\omega_0) \omega_p$$

$$20 \log 10^4 = 80 \text{ dB}$$

$$f_1 = 1 \text{ MHz}$$

$$(\log : \text{slope is -ve})$$

close to 20 dB/dec


$$\omega_i = 2\pi f_1$$

40 dB/dec

we assume that we have a transfer $f^n C$ with one pole.

Amplitude Control in Wien-Bridge Oscillator

\rightarrow amplitude of V_{out} - ?

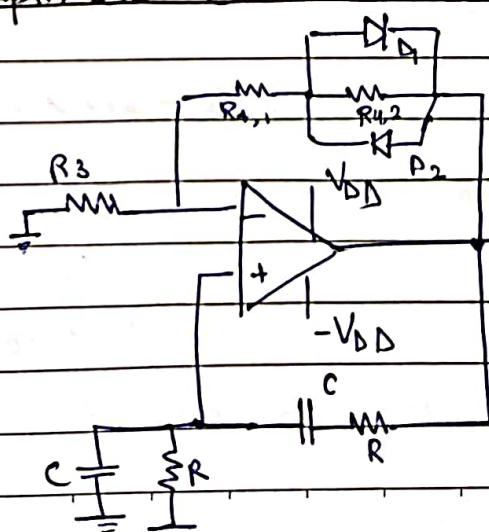

if $V_{R4,2} \approx V_{ON,D} \Rightarrow$

$$V_{out} \left(\frac{R_{42}}{R_3 + R_{41} + R_{42}} \right) V_{out,lim} \approx V_{ON,D}$$


so,

$$V_{out,lim} \approx V_{ON,D} \times \left(\frac{R_3 + R_{41} + R_{42}}{R_{42}} \right)$$

$\frac{R_{41}}{R_3} < 2 \rightarrow$ oscillation amplitude decays if diode is ON

Amplitude Controller Limiter circuit - (A)

Date _____
Page _____

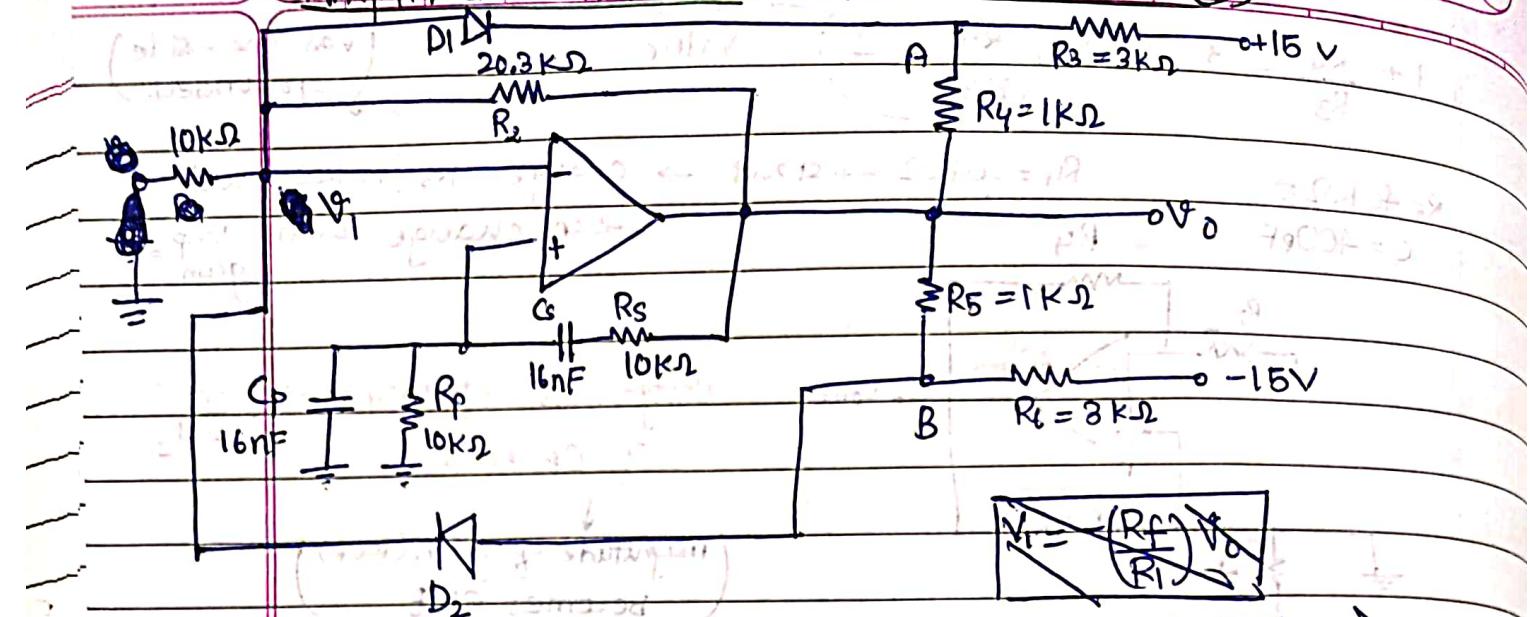

as we see in the limiter circuit, $L = \frac{V}{R_4} - V_D \left(1 + \frac{R_5}{R_6} \right)$

and $V_A = \frac{V}{R_5} + V_D \left(1 + \frac{R_5}{R_6} \right)$ values of V_A at which D_1 conducts (lower limit)

If $V_A > -(R_f/R_i)L$ $\Rightarrow V_A$ remains at $-V_D \Rightarrow i_{P3} = \text{constant}$.

\rightarrow at the peak of V_A , $V_b > V_A$ ($V_A = V_0/3$) $\hookrightarrow D_2$ conducts

Clamps the peak to a value det. by R_5, R_6, V_D, V_p , power supply

$$V_b = V_A + V_{D2} \quad \text{and} \quad \frac{V_0 - V_b}{R_5} = \frac{V_b + 15}{R_6} \quad V_0 = \left(1 + \frac{R_5}{R_6} \right) (V_A + V_{D2}) \quad \text{CLAMP}$$

\rightarrow -ve peak of $V_0 \rightarrow$ clamped by value that causes D_1 to conduct.

$$\hookrightarrow V_A = V_0 - V_D$$

saturation voltage or箇定電圧の範囲で動作する

\Leftarrow $V_A = V_0 - V_D$

$$V_0 = 15V \left(\frac{1}{3} + \frac{1}{3} \right) + 15V = 30V$$

$$(15V + 15V) \times \frac{1}{3} = 10V \approx \text{saturation voltage}$$

\Leftarrow $V_A = V_0 - V_D$