
EE204: Analog Circuits
Dept. of Electrical Engineering
IIT Bombay
Autumn Semester 2023

Assignment 3

Total Marks: 10

Submission Deadline: 11:59 p.m., 09-09-2023

Mode of Submission: Scan your assignment and upload on Moodle as a single pdf file.

Q-1. In the circuit shown in Fig. 1: $R_4 = R_2 = 10\text{K Ohm}$, $R_3 = R_1 = 5\text{K Ohm}$, $V_{dd} = 5\text{V}$, $V_{o_{min}} = 0\text{V}$, $V_{o_{max}} = 5\text{V}$ for all Op-Amps

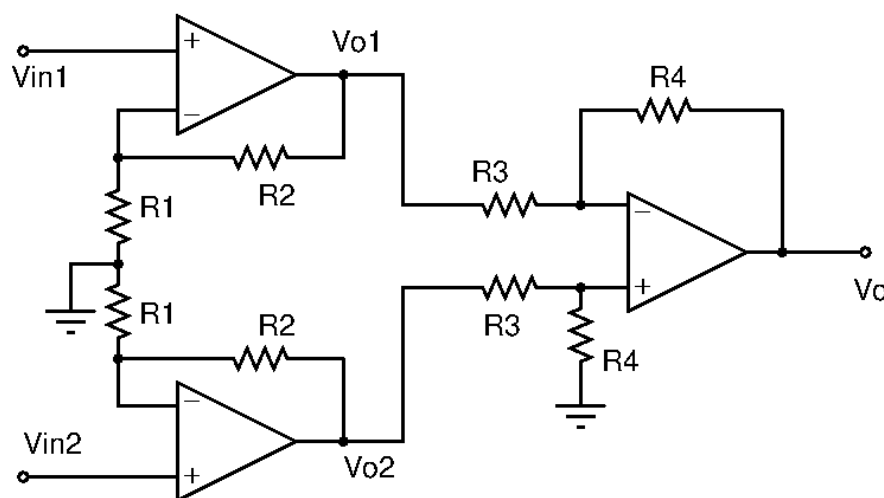


Fig. 1

- For the inputs: $V_{in1} = V_{cm} - V_{id} * \sin(\omega t)$, $V_{in2} = V_{cm} + V_{id} * \sin(\omega t)$, find expressions for outputs of all Op-Amps, i.e, V_{o1} , V_{o2} , V_o . (1.5 marks)
- Assuming the Op-Amps are ideal, given $V_{cm} = 1.8\text{V}$, $V_{id} = 0.3\text{V}$, plot all three Op-Amp output waveforms for at least two cycles. (1.5 marks)
- Assume the output of all Op-Amps saturates at 4V. Plot all three output waveforms once again for at least two cycles. Other parameters of Op-Amps and other elements remain unchanged. (1.5 marks)

Label all the voltage levels properly in the plots.

Q-2. In the circuit shown in Fig. 2, the NMOS is biased at $V_b = 0.8$ V, $V_{dd} = 1.8$ V, $W/L = 9/0.36$, $\mu_n C_{ox} = 260 \mu A/V^2$, $V_{TH} = 0.4$ V

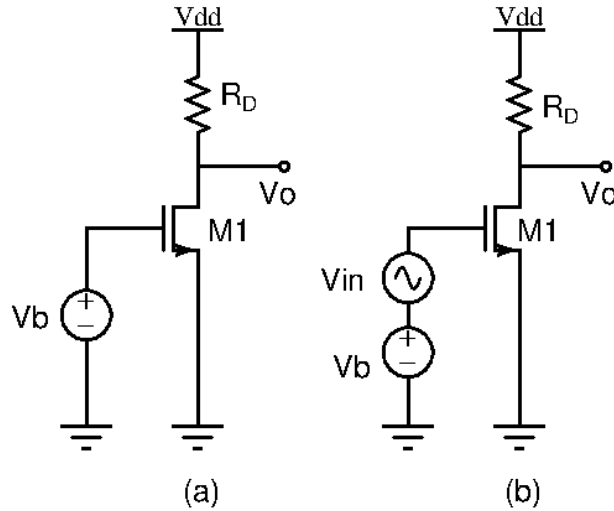


Fig. 2

- Find the biasing current I_D , and V_o for $R_D = 0.8$ K Ohm. Report the region of operation of M1. (0.5 marks)
- Draw the small signal model of the given circuit and find the small signal gain. (1 mark)
- A small signal with pk-pk input of 20mV is applied, as shown in Fig. 2b. Find the absolute value of incremental pk-pk output - input gain. Is the gain inverting or non-inverting? (2 marks)
- If R_D is increased by two times, calculate the new value of incremental gain for the same pk-pk input of 20mV. Find the maximum value of R_D , that can be used such that M1 stays in saturation. (2 marks)